



UNIVERSITI
TEKNOLOGI
MALAYSIA
www.utm.my

SECR1013 DIGITAL LOGIC

MODULE 7:
LATCHES & FLIP-FLOPS

FACULTY OF COMPUTING



Objectives:

- To introduce the various types of latches and flip-flop;
- To explain the characteristic of latches and flip-flop;
- To illustrate the timing diagram associated with each latches and flip-flop operations.

Topics Outline:

LATCH

- S-R Latch
- Gated S-R Latch
- Gated D Latch

FLIP-FLOPS

- S-R Flip-Flop
- J-K Flip-Flop
- D Flip-Flop
- T Flip-Flop




UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Introduction to Latch & Flip-Flop

Introduction

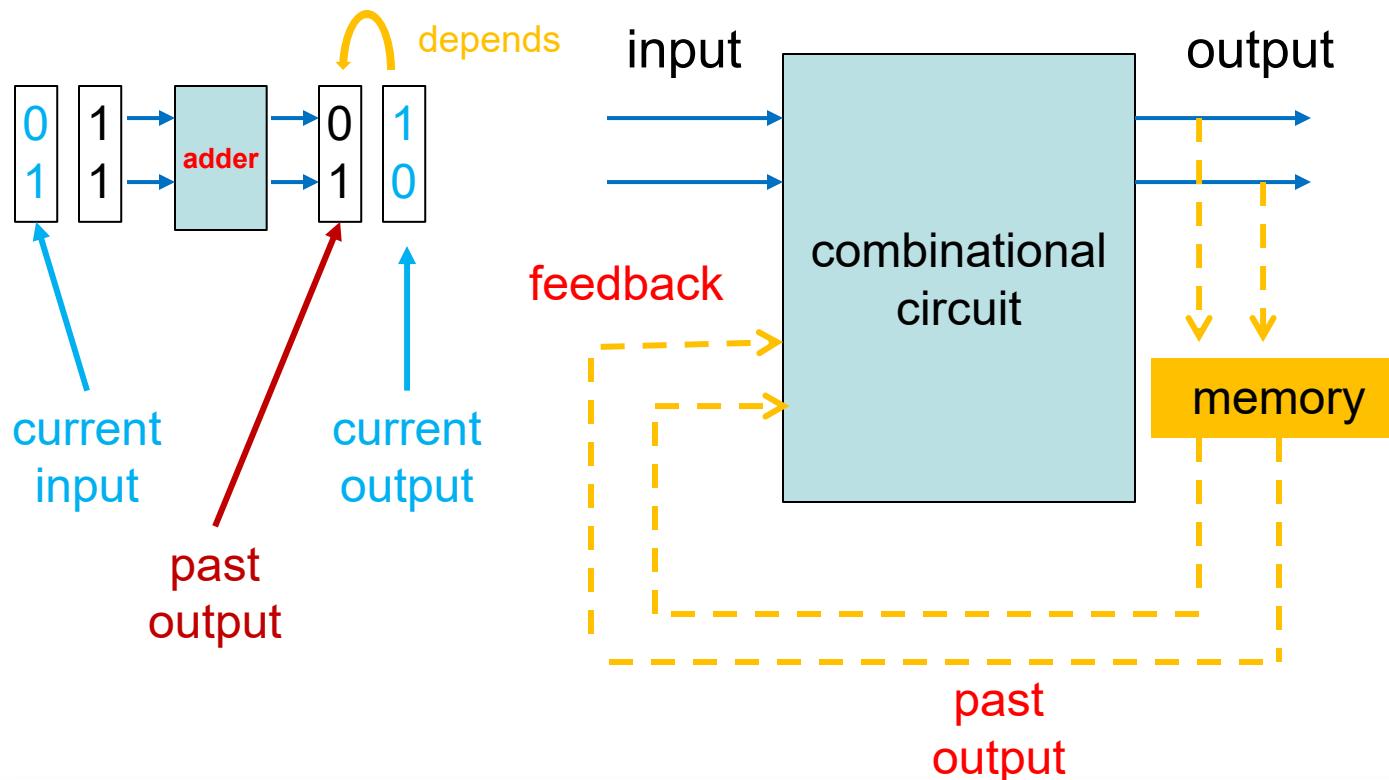- In **sequential circuits**, the current output depends on the current input as well as past output / outputs



Example of seq. circuits:

- flip flop
- counter
- register

counter
0 to 5

- | |
|----------|
| 0: 0 |
| 1: 0 + 1 |
| 2: 1 + 1 |
| 3: 2 + 1 |
| 4: 3 + 1 |
| 5: 4 + 1 |




WU

Sequential Vs Combinational Logic Circuit

unlock:

Combinational Logic Circuit:

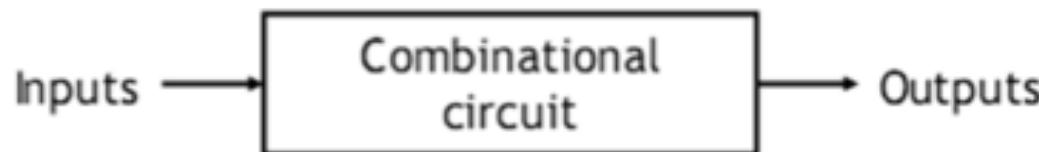

4 5 6 7




key sequence is NOT matter


- The output depend on the input
- It has no memory element
 - Therefore, it cannot memorize the previous output



Sequential Logic Circuit:

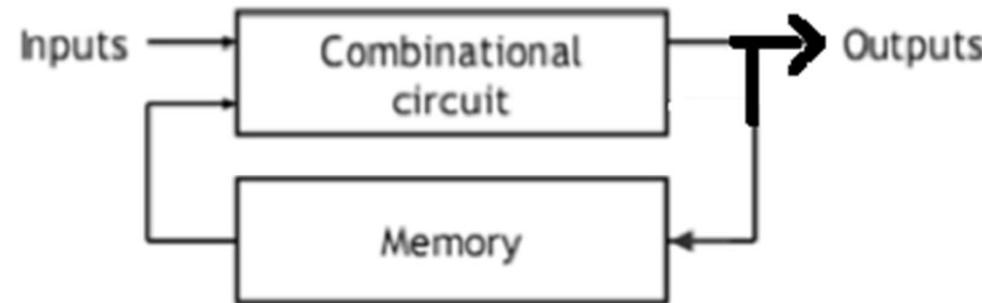

unlock:

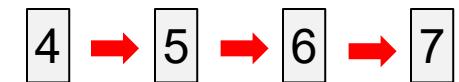


To unlock:
key sequence is MATTER

- It has memory element
- The output depend on the input, as well as the previous output from the feedback elements

Sequential Logic circuits can be divided into 3 main categories:

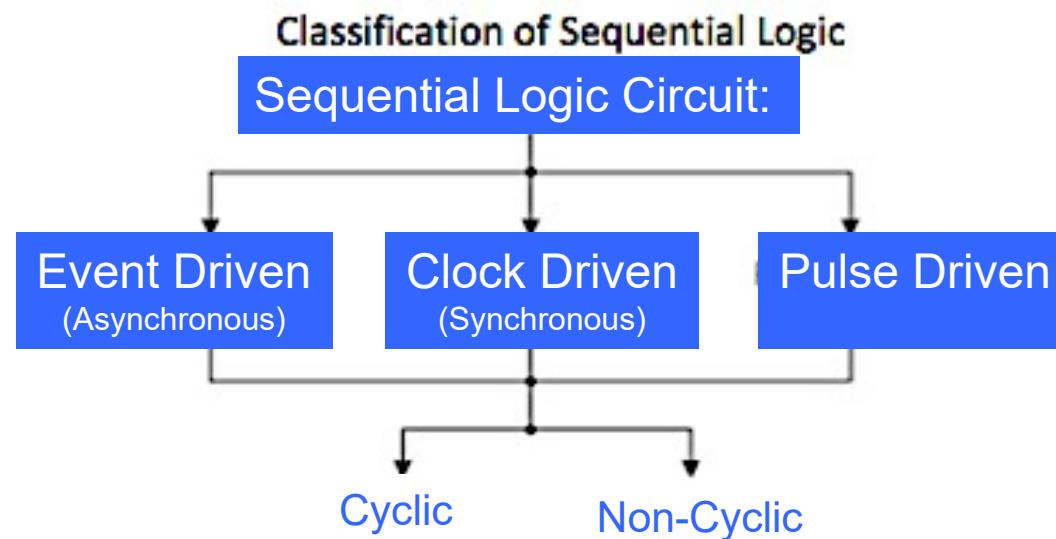1. Clock Driven - Synchronous Circuits that are synchronized to a specific clock signal.
2. Event Driven - Asynchronous Circuits that react or change state when an external event occurs.
3. Pulse Driven - Which is a Combination of Synchronous and Asynchronous.



Sequential logic circuits that return back to their original state once reset, i.e. circuits with loops or feedback paths are said to be "Cyclic" in nature.



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Latches

Latch

- Latch is a type of temporary storage device
- It has **two stable** states (bi-stable).
- Latch is level sensitive, or level-triggered.
 - are dependent on the voltage level applied (0/1), not on any signal transition.
- Type of Latch :
 - i) **S-R**
 - ii) **Gated S-R**
 - iii) **Gated D**

LOW

HIGH

INFO :

A **bi-stable** state is one with *two-stable* output states.


S → Set

R → Reset


D → Data

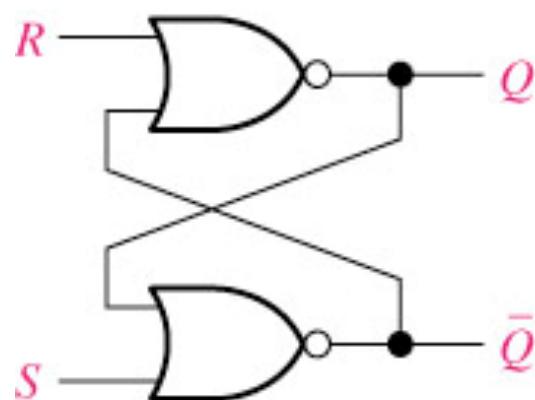(i) S-R Latch

- The output of each gate is connected to an input of the opposite data.
- This produces a **regenerative feedback**.




(a) Active-HIGH input S-R latch

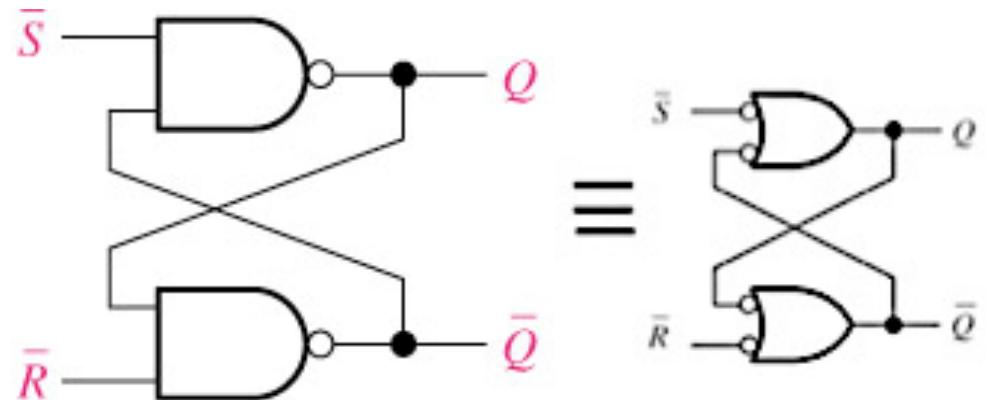


(b) Active-LOW input \bar{S} - \bar{R} latch

S-R Latch: Logic symbol

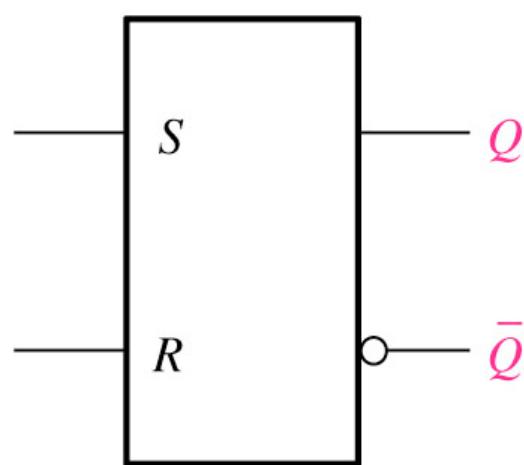


(a) Active-HIGH input
S-R latch

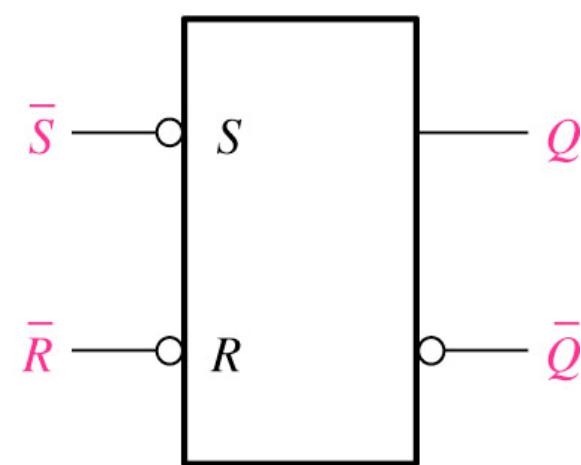

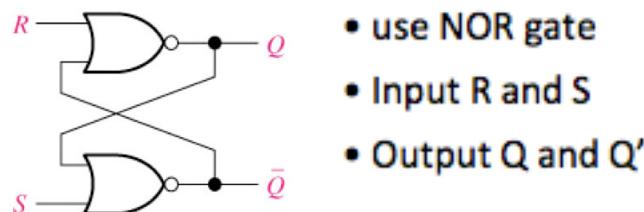(b) Active-LOW input
S-R latch


Circuit (a) Active-HIGH input S-R latch :



- use NOR gate
- Input R and S
- Output Q and Q'


Circuit (b) Active-LOW input S'-R' latch :

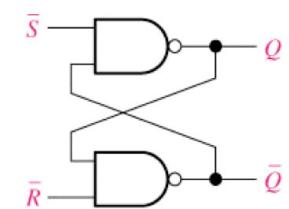- use NAND gate
- Input S' and R'
- Output Q and Q'



Active-HIGH

INPUTS		OUTPUTS		COMMENTS
S	R	Q	\bar{Q}	
0	0	NC	NC	No change. Latch remains in present state
0	1	0	1	Latch RESET
1	0	1	0	Latch SET
1	1	0	0	Invalid condition

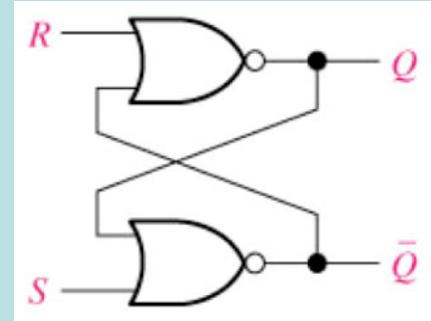


Explanation :



- The Q and Q-bar outputs are supposed to be in **opposite** states.
- Q=1** and Q-bar=0 is defined as **Set** (by making S=1 and R=0)
- Q=0** and Q-bar=1 is defined as **Reset** (by making S=0 and R=1)
- When S and R are both equal to 0, the latch's outputs **Not Change** in their prior states.
- If Q and Q-bar happen to be forced to the same state (both 0 or both 1), that state is referred to as **invalid**.

Active-LOW

INPUTS		OUTPUTS		COMMENTS
\bar{S}	\bar{R}	Q	\bar{Q}	
0	0	1	1	Invalid condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change. Latch remains in present state


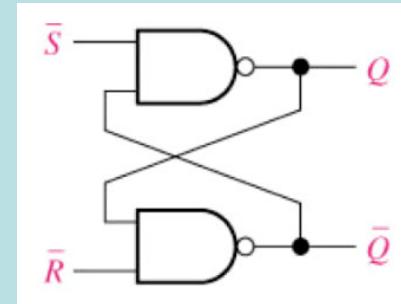


Example: S-R Latch (Active HIGH)

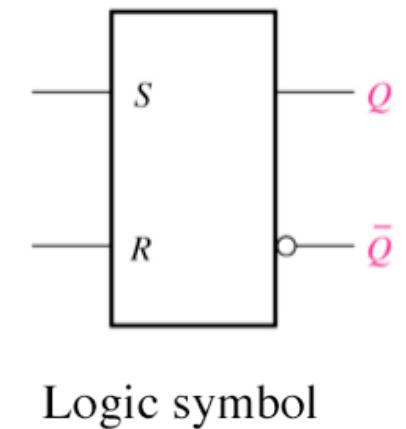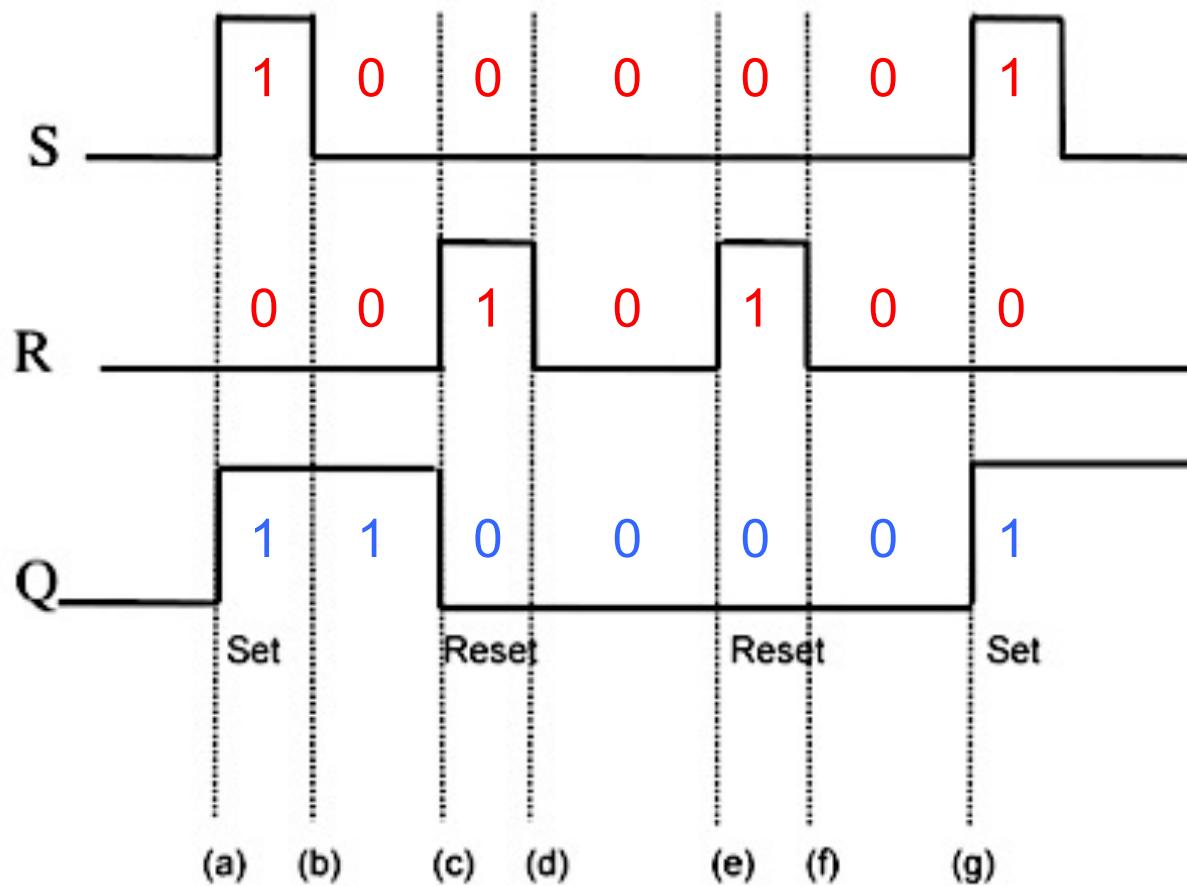

Logic symbol

continue...

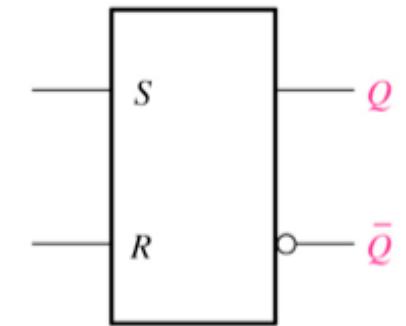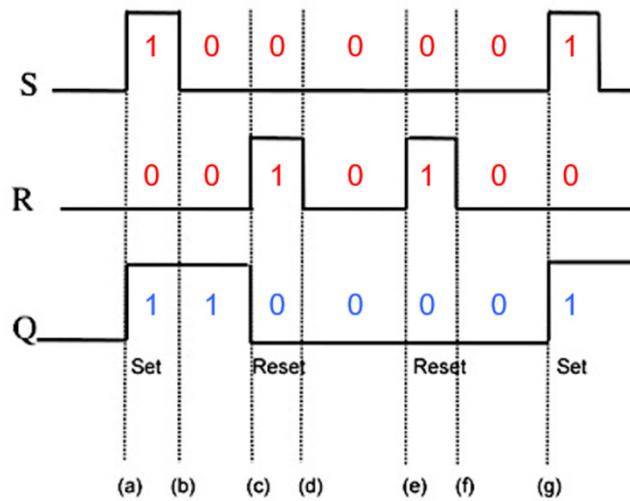


Logic symbol

Explanation:

Location	S	R	Q	State
(a)	1	0	1	SET
(b)	0	0	1	HOLD
(c)	0	1	0	RESET
(d)	0	0	0	HOLD
(e)	0	1	0	RESET
(f)	0	0	0	HOLD
(g)	1	0	1	SET


Extra

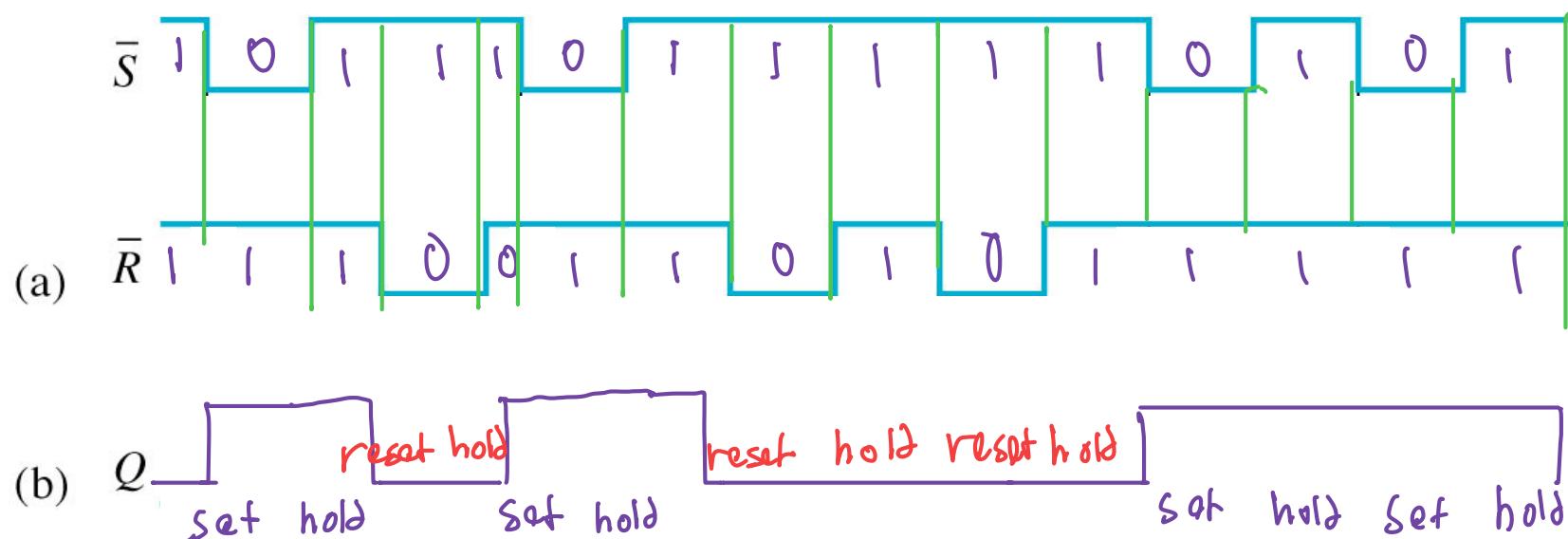Exercise 7.1: If the \bar{S} and \bar{R} waveform in (a) are applied to the inputs of latch (active-LOW), determine the waveform that will be observed on the Q output in (b). Assume that Q is initially LOW.




Active-LOW

INPUTS		OUTPUTS		COMMENTS
\bar{S}	\bar{R}	Q	\bar{Q}	
0	0	1	1	Invalid condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change. Latch remains in present state

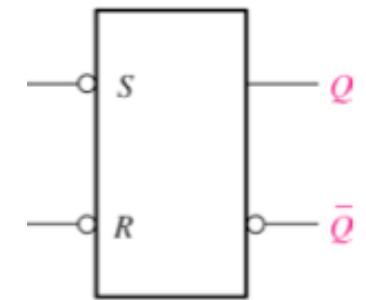

Logic symbol


Solution: (Red 0/1 is no change or hold)

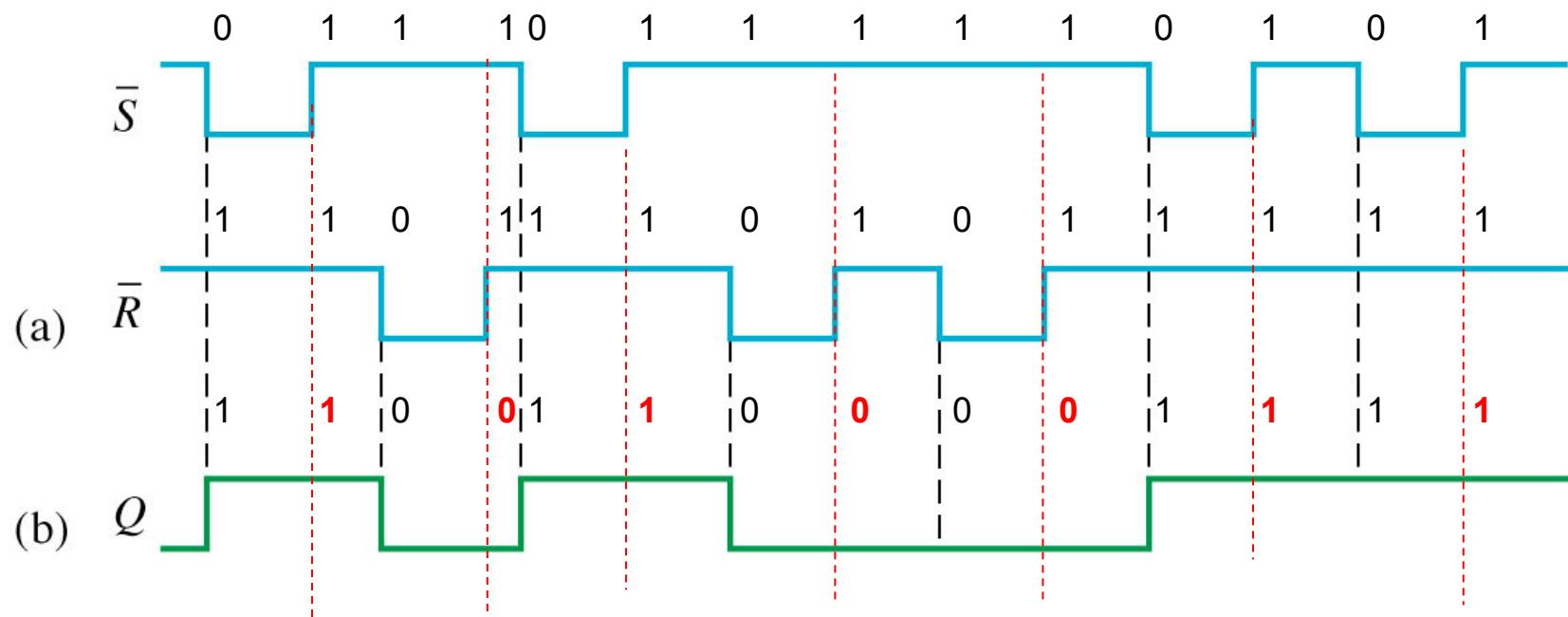

Extra

Self-Test:

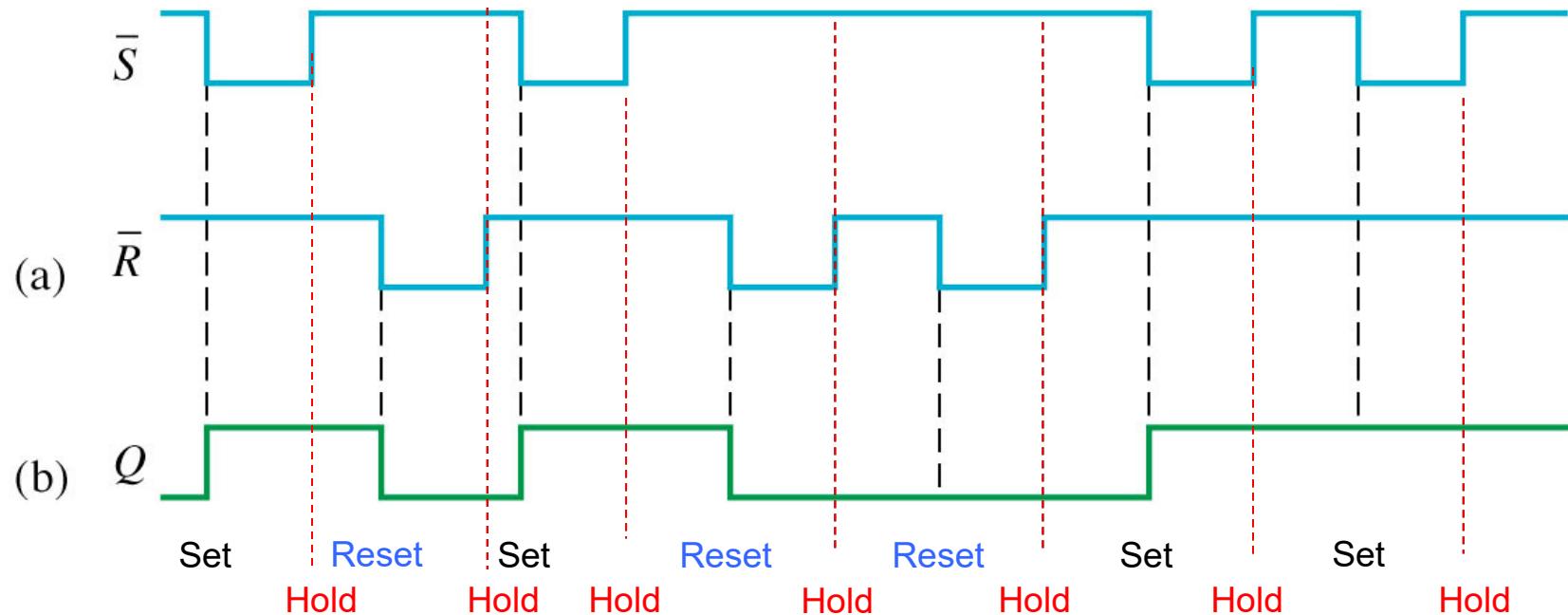Define when the states are *set*, *reset*, *hold* or *invalid* from the output waveform for each of the inputs.




Extra

Self-Test:

Write the sequence of the states (*set*, *reset*, *hold* or *invalid*) for the output Q waveform for all inputs from the beginning.

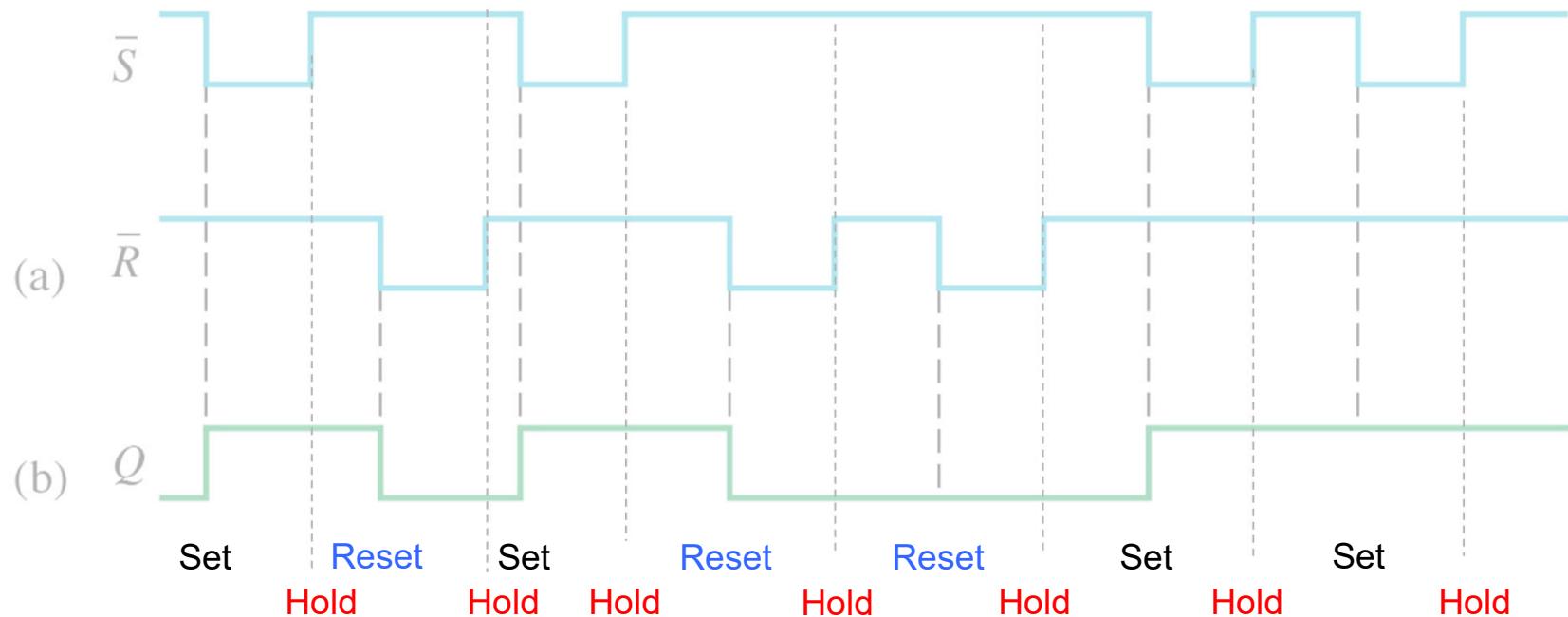Set → Hold → Reset → Hold → Set → Hold → Reset → Hold → Reset → Hold → Set → Hold → Set → Hold



(ii) Gated S-R Latch


- Is a SR Latch controlled by an **enable input (EN)** switch.
- The S and R inputs control the state to which the latch will function when a **HIGH** level is **applied** to the **EN** input.
- The latch will **not change** until **EN** is **HIGH**, and as long as it **remains HIGH**, the output is controlled by the state of the S and R input.
- The **invalid state** occurs when **both** S and R are simultaneously **HIGH**.

INFO :

EN = 1, Latch is On
EN = 0, Latch is Off

Gated S-R Latch: Truth Table


EN	S	R	Output, Q
0	0/1	0/1	No Change
1	0	0	No Change
1	0	1	Q=0 (Reset)
1	1	0	Q=1 (Set)
1	1	1	Invalid

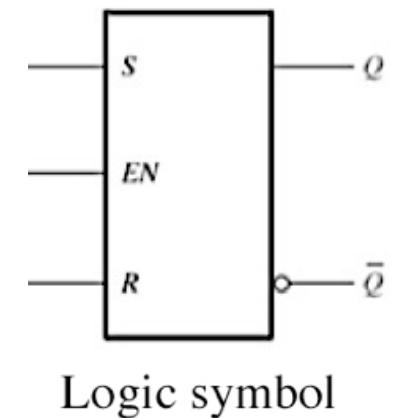


Example: Gated S-R Latch.

Find the waveform for Q.


Assume that Q is initially LOW.

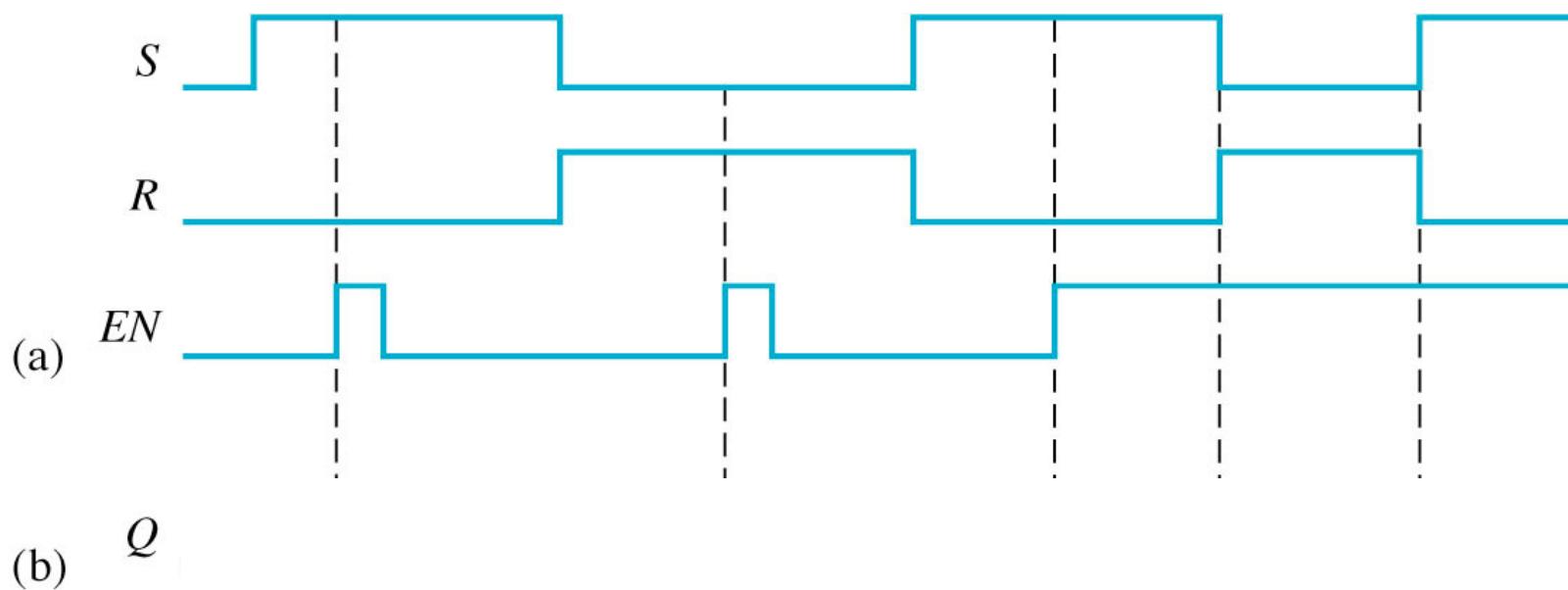



INPUTS		OUTPUTS	
S	R	Q	\bar{Q}
0	0	NC	NC
0	1	0	1
1	0	1	0
1	1	0	0

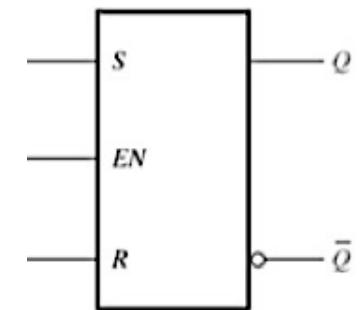

Solution: Assume that Q is initially LOW.

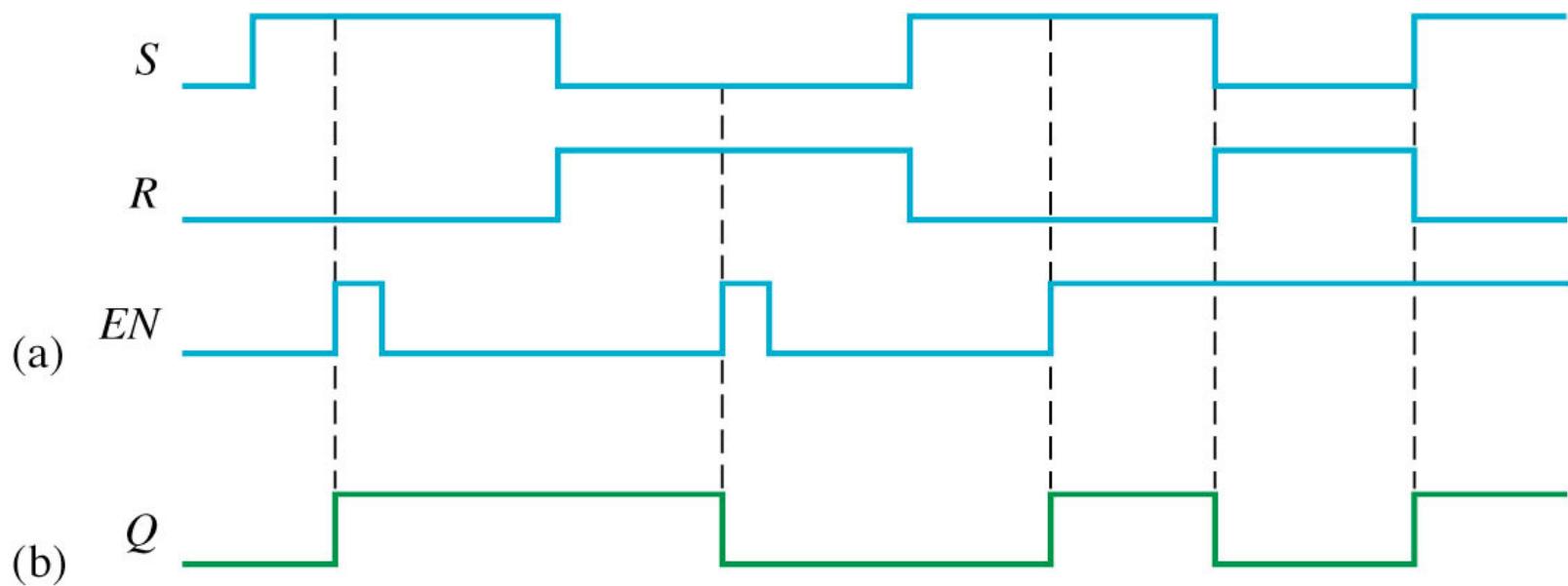

Exercise 7.2:

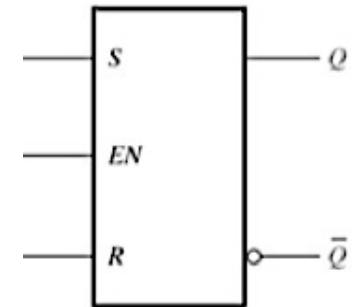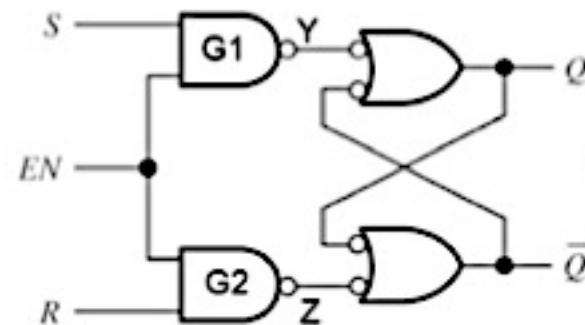


Referring to logic diagram above, fill in the table. Assume initially $Q = 0$ and $Q' = 1$


$\overline{S \cdot EN}$	$\overline{R \cdot EN}$	Q
0	0	0
0	1	0
1	0	0
1	1	0
0	0	0
0	1	1
1	0	1
1	1	—

Active-LOW

INPUTS		OUTPUTS		COMMENTS
\bar{S}	\bar{R}	Q	\bar{Q}	
0	0	1	1	Invalid condition
0	1	1	0	Latch SET
1	0	0	1	Latch RESET
1	1	NC	NC	No change. Latch remains in present state

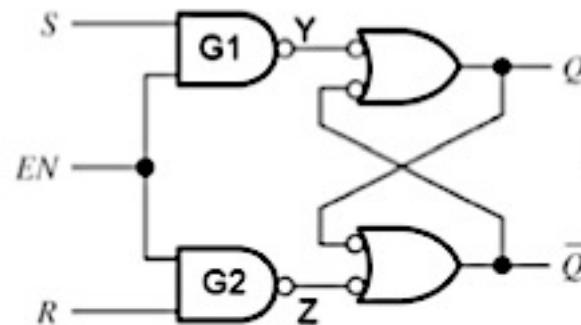

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

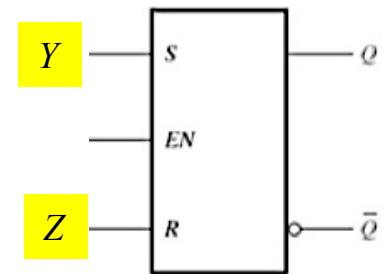

Solution:

Referring to logic diagram above, fill in the table. Assume initially $Q = 0$ and $\bar{Q} = 1$

$Q \rightarrow$ Run as 'Active Low S-R' latch
when $EN = 1$

EN	$\overline{S \cdot EN}$		$\overline{R \cdot EN}$		STATE
	S	R	Y	Z	
0	0	0	1	1	Hold
0	0	1	1	1	
0	1	0	1	1	
0	1	1	1	1	
1	0	0	1	1	Hold
1	0	1	1	0	Set
1	1	0	0	1	Reset
1	1	1	0	0	Invalid

$EN=0$

$EN=1$

Example: Gated S-R Latch.


Find the waveform for Q.


Assume that Q is initially LOW.

R reset


Set

hold

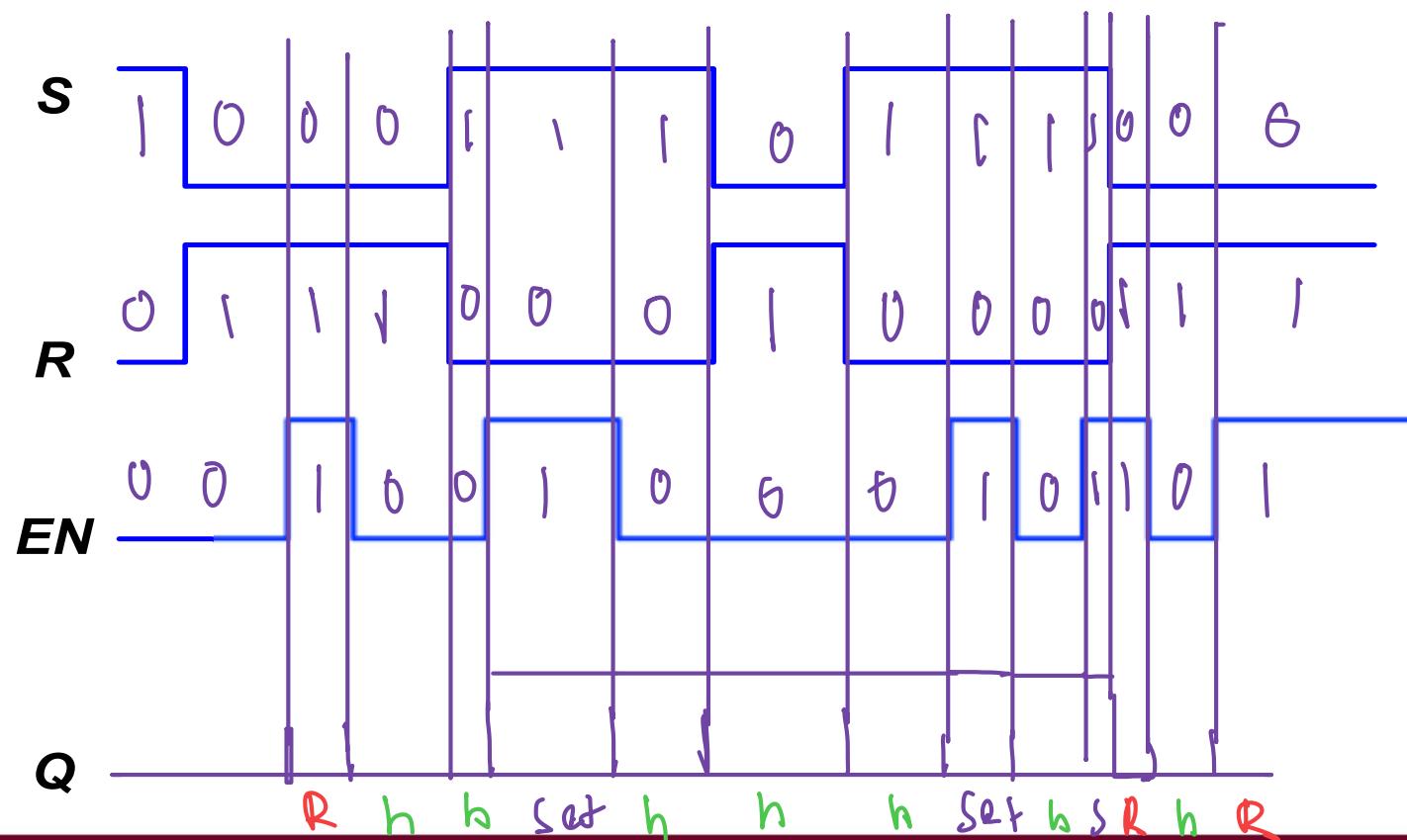

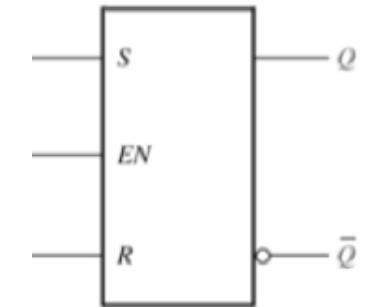

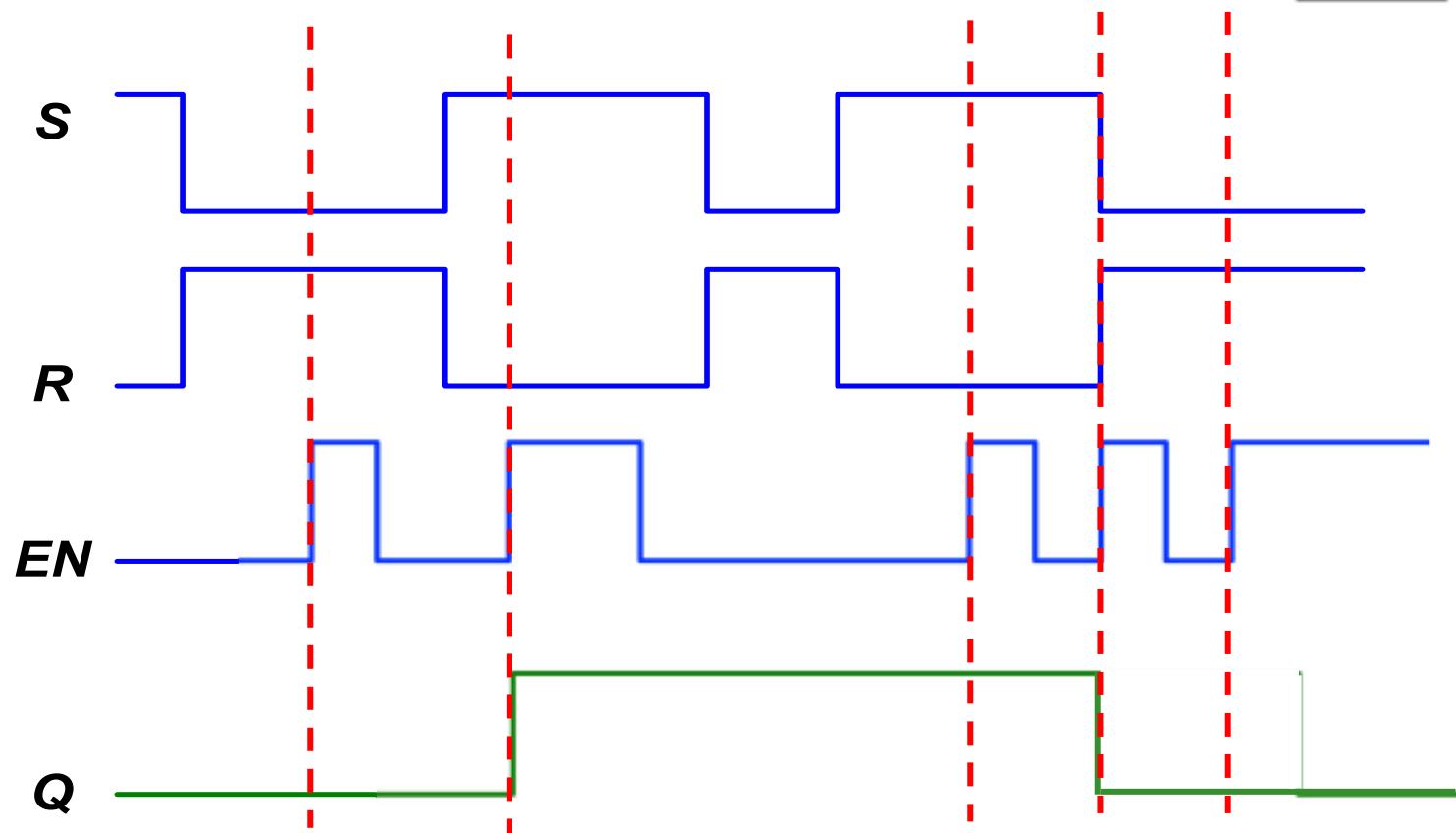Solution: Assume that Q is initially LOW.




(Module: page 220)

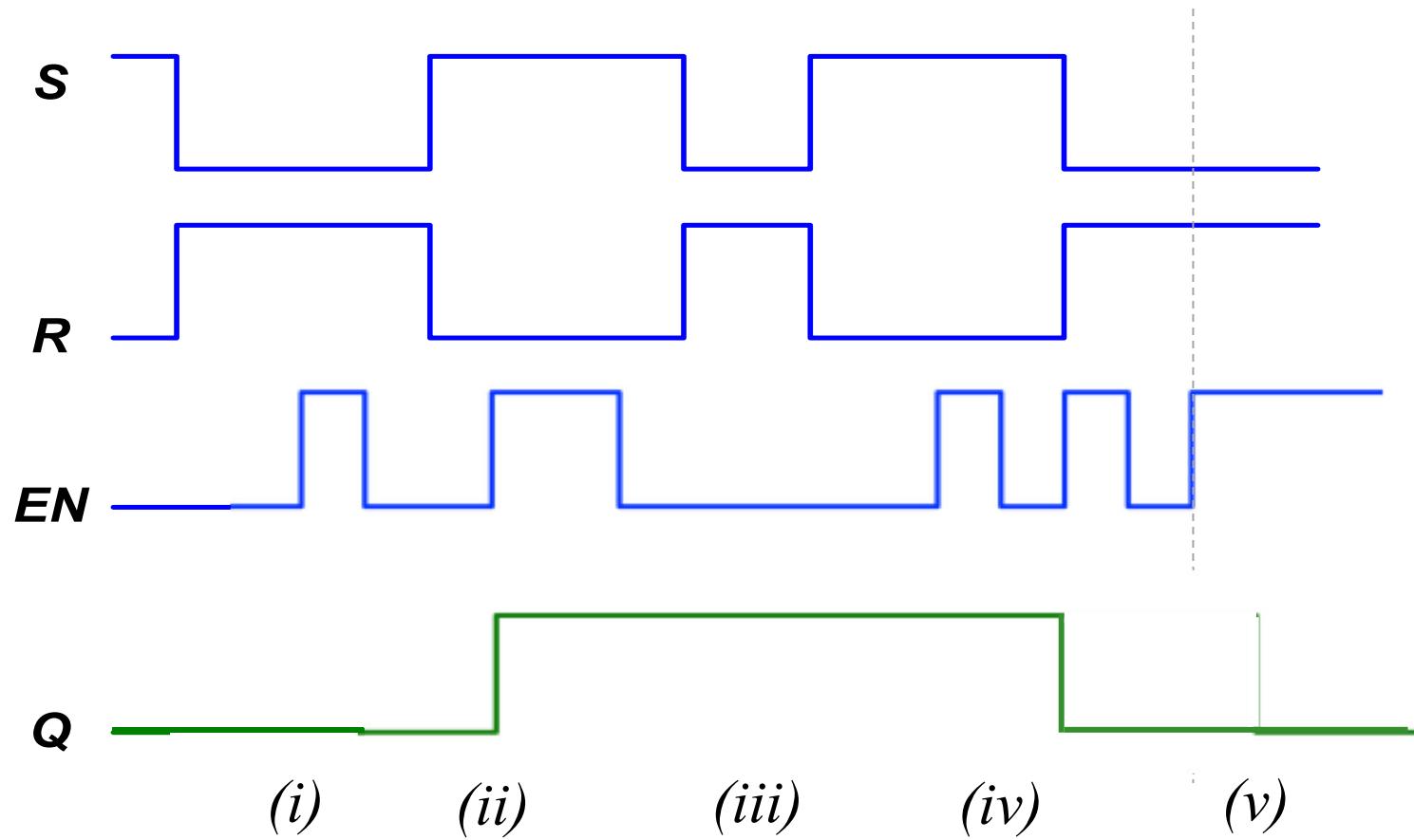i) Reset ii) Set iii) hold iv) hold
v) reset


Self-Test:

Define the states (*set*, *reset*, *hold* or *invalid*) for all outputs waveform Q that label as *i*, *ii*, *iii*, *iv* and *v*.




Solution:

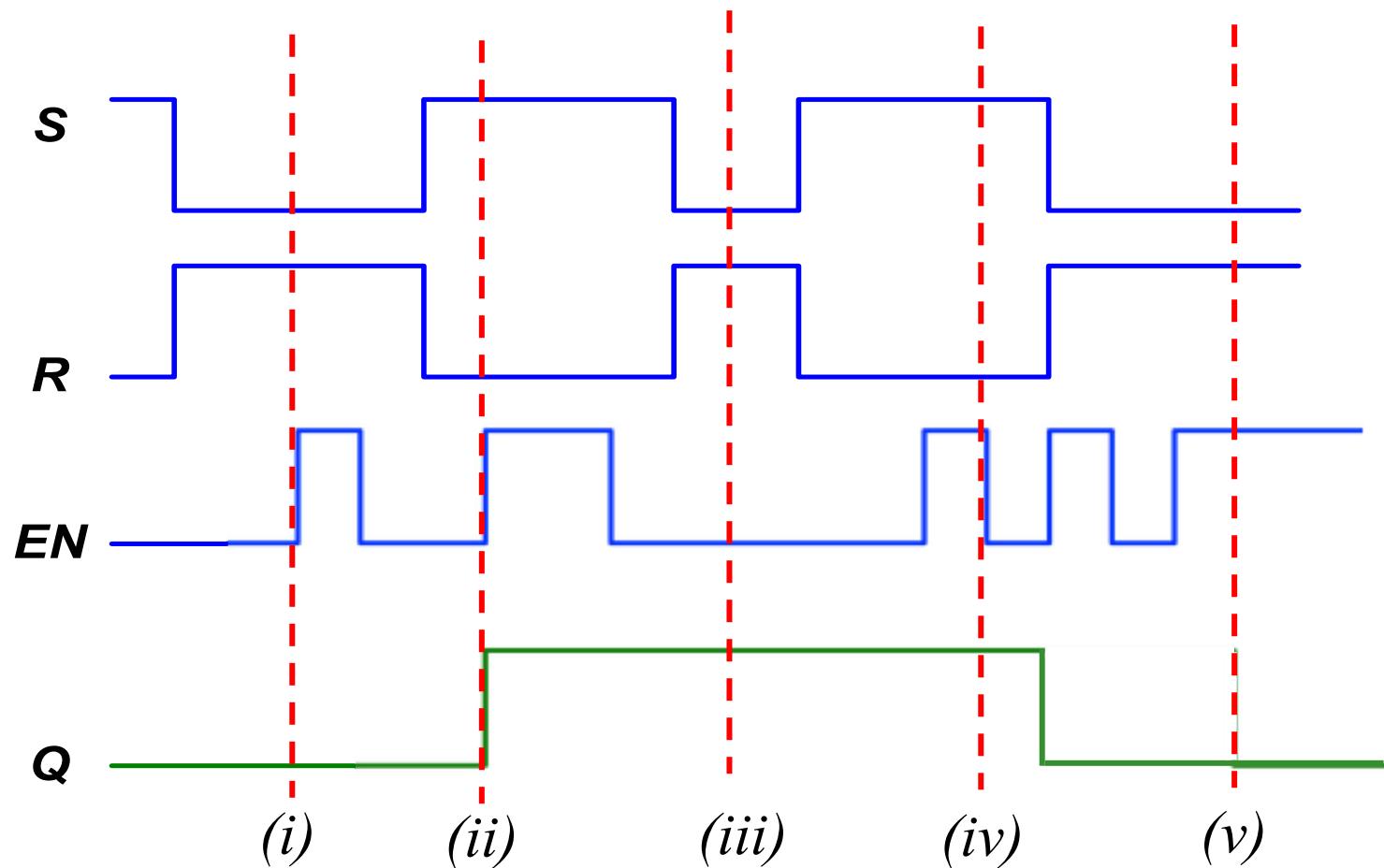
- (i) Reset
- (ii) Set
- (iii) Hold / No change
- (iv) Hold / No change
- (v) Reset



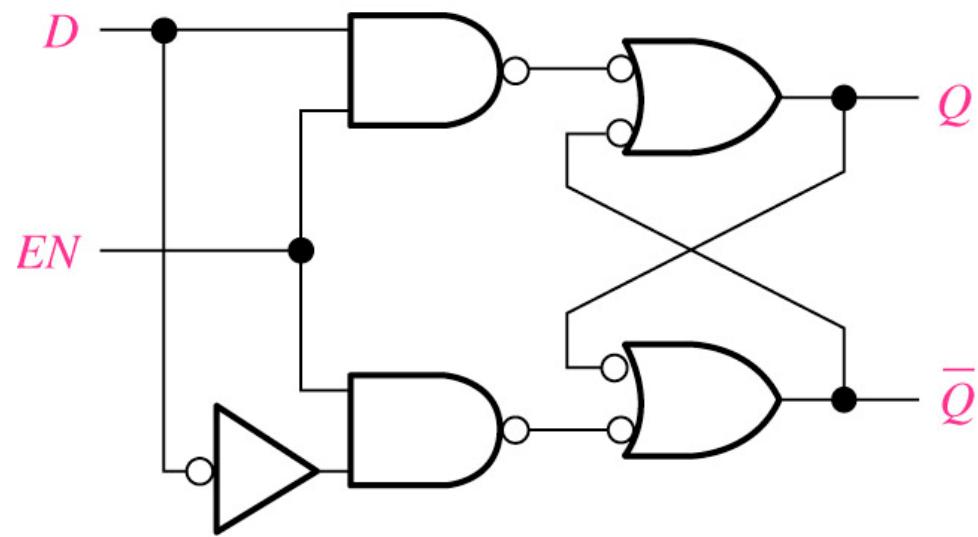(iii) Gated D Latch:
Logic diagram & logic symbol




(a) Logic diagram

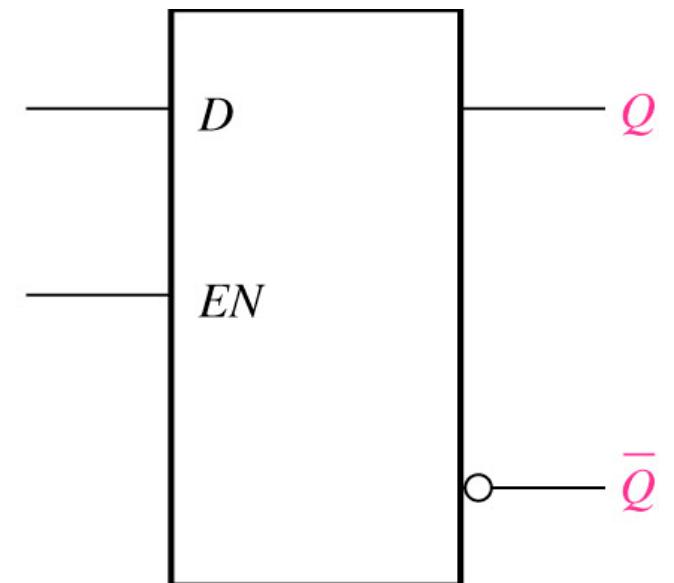


(b) Logic symbol


Gated D Latch

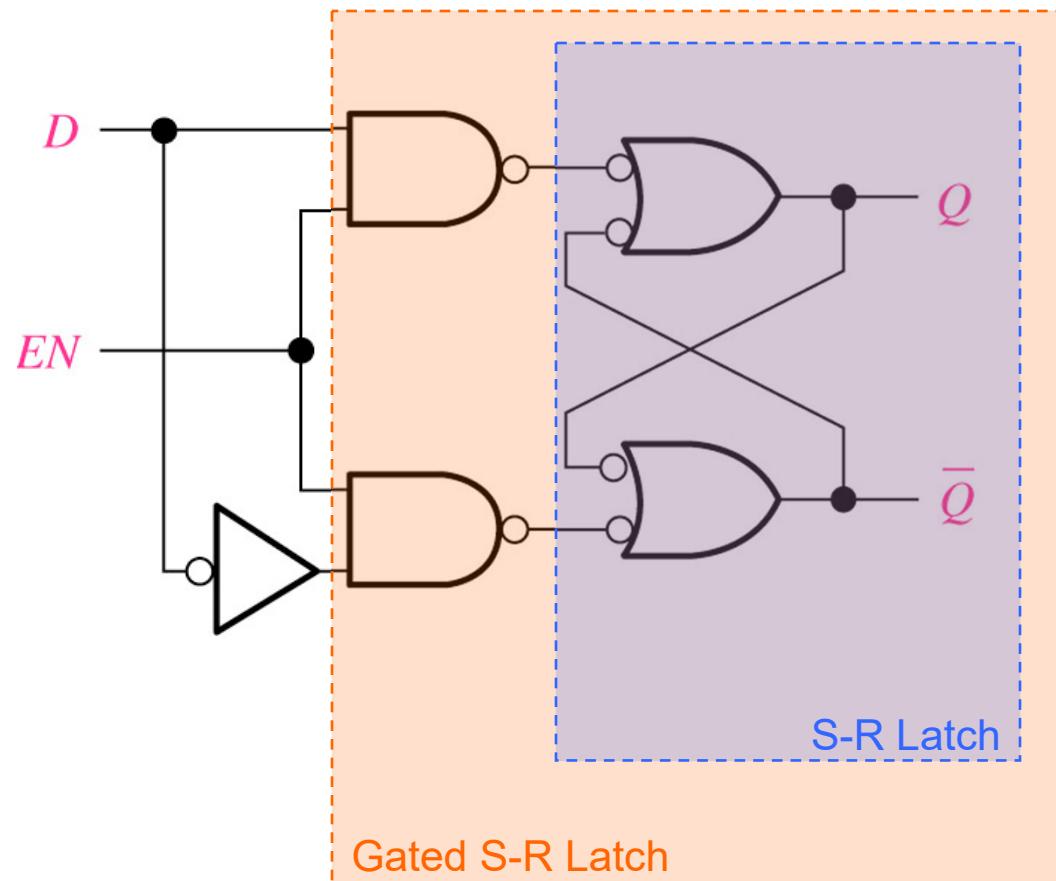


Modified Gated S-R Latch

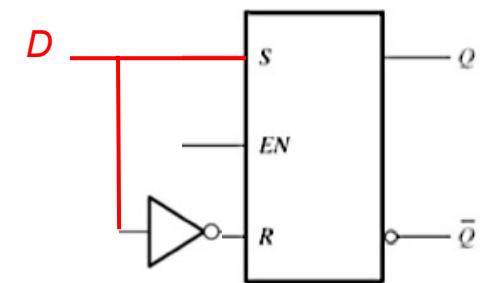

Gated D Latch

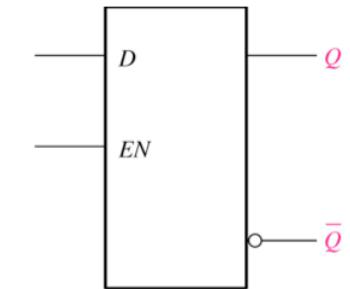

Gated D Latch:

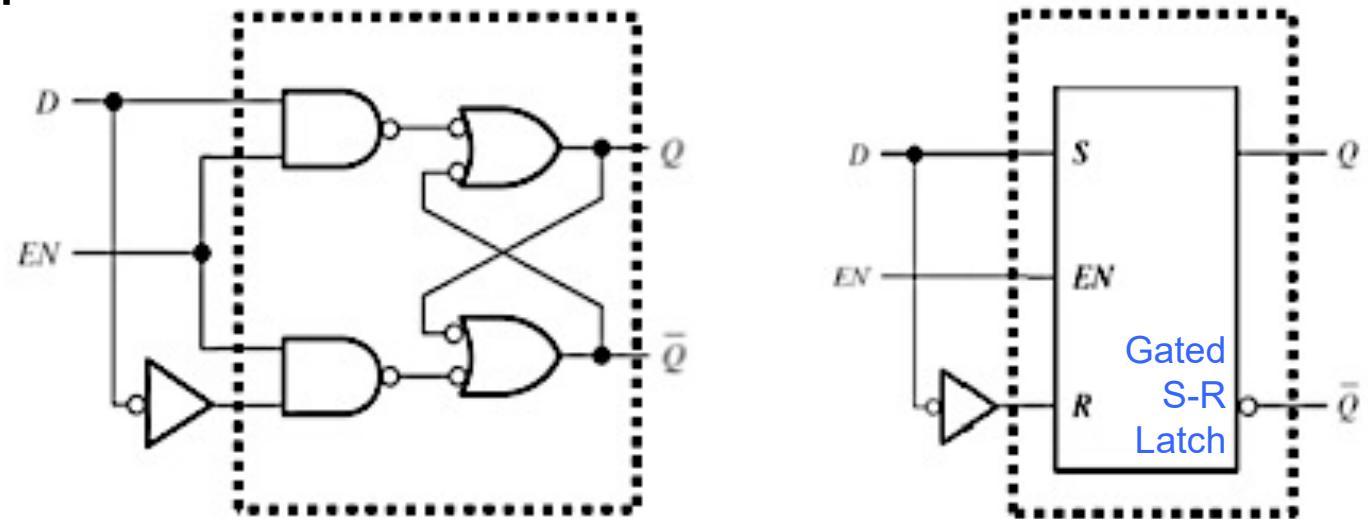

The purpose of the inverter is to make sure that R is the complement of S and R will never be the same as S . So that, we have only two condition at the input of SR.

Condition 1: $D = 0$, therefore $S = 0$, $R = 1$ which make $Q = 0$

Condition 2: $D = 1$, therefore $S = 1$, $R = 0$ which make $Q = 1$


Just like gated SR, when $EN=0$, the output does not change. BUT, if $EN=1$, the output will depend on the value of input D .

So, we can conclude that $Q=D$ when $EN=1$.

$EN=1 \rightarrow Q=D$

Gated D Latch: Truth Table

EN	D	Output, Q
0	0	No Change
0	1	No Change
1	0	$Q = 0$
1	1	$Q = 1$

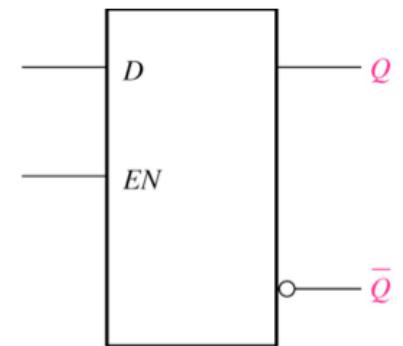


EN = 1, Latch is On
EN = 0, Latch is Off

$$EN = 1 \rightarrow Q = D$$

Example: Gated D Latch.


Find the waveform for Q.

Assume that Q is initially LOW.

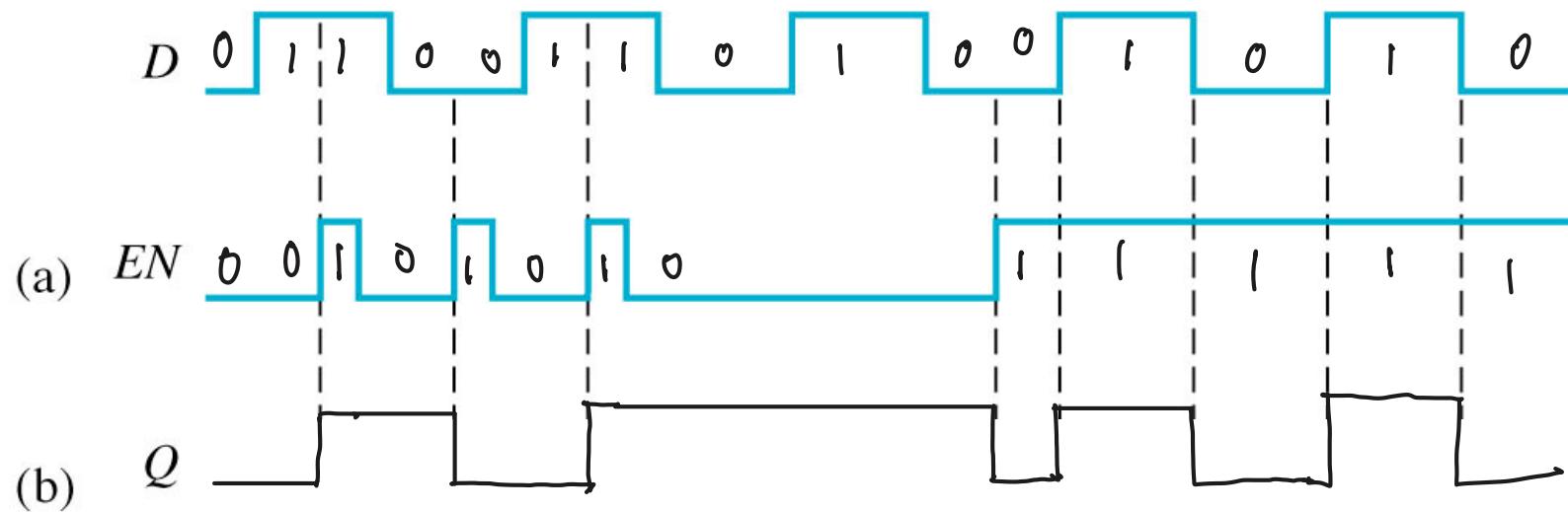


Solution:

EN	D	Output
0	0	No Change
0	1	No Change
1	0	$Q = 0$
1	1	$Q = 1$

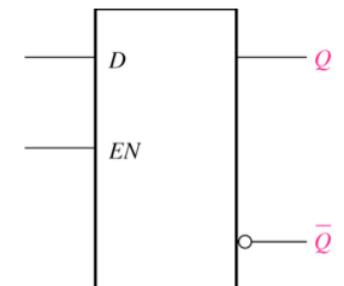

Logic symbol

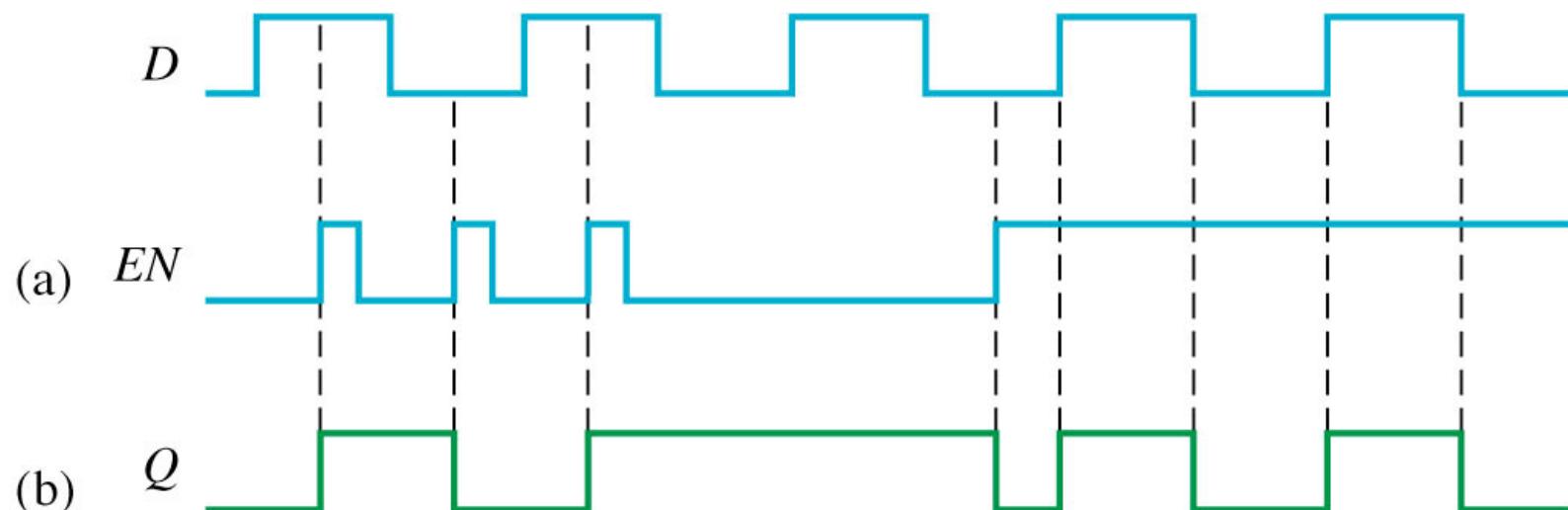



UTM
UNIVERSITI TEKNOLOGI MALAYSIA

www.utm.my

Flip-Flops




- **Flip-flops (FF)** are **synchronous** bi-stable storage devices capable of storing one bit, where the **output** state only **changes at** a specified point on a **triggering input** called the **Clock (C)**.
- FFs are **edge-triggered**, means that the output changes are synchronized with the **Clock** signal. This may either be
 - a **LOW-to-HIGH** (rising edge) transition or
 - a **HIGH-to-LOW** (falling edge) transition
- Type of Flip-Flops:
 - i) **S-R**
 - ii) **D**
 - iii) **J-K**
 - iv) **T**

Edge-Triggered FF


KEY TERMS :

Rising edge = positive edge
Falling edge = negative edge


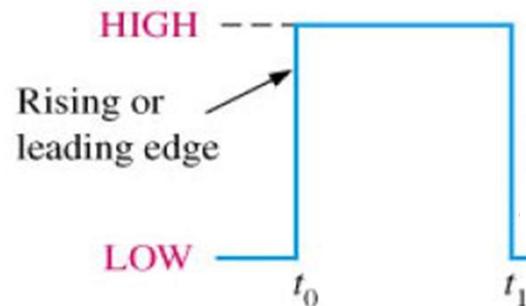
Flip-flop is an important device in a sequential circuit



(a) Positive-going pulse

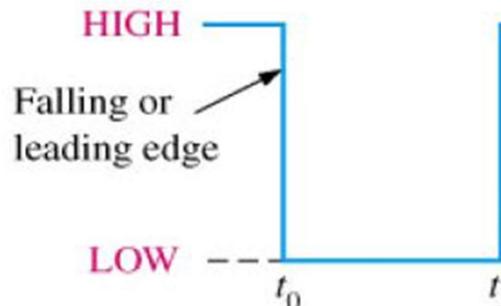



(b) Negative-going pulse

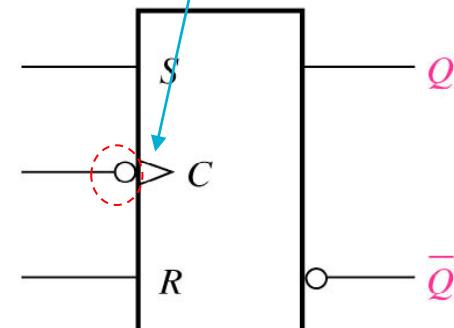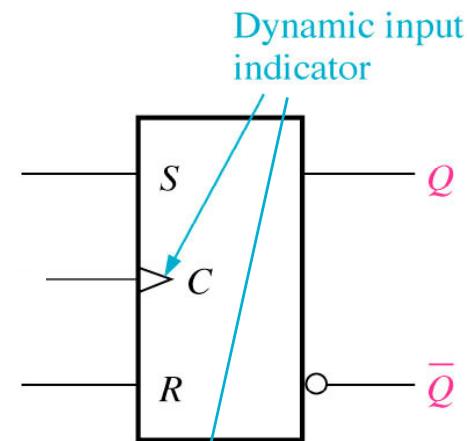

Edge-Triggered FF logic symbol




Difference:

Latch vs Flip-Flop


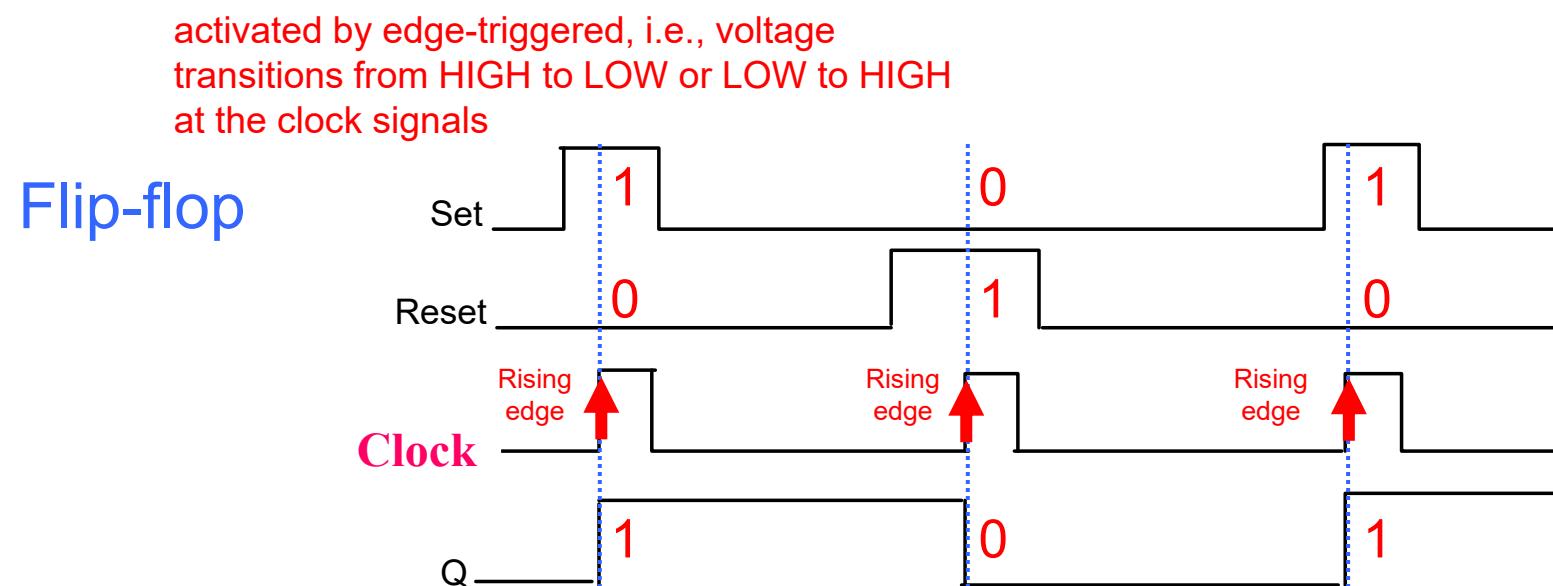
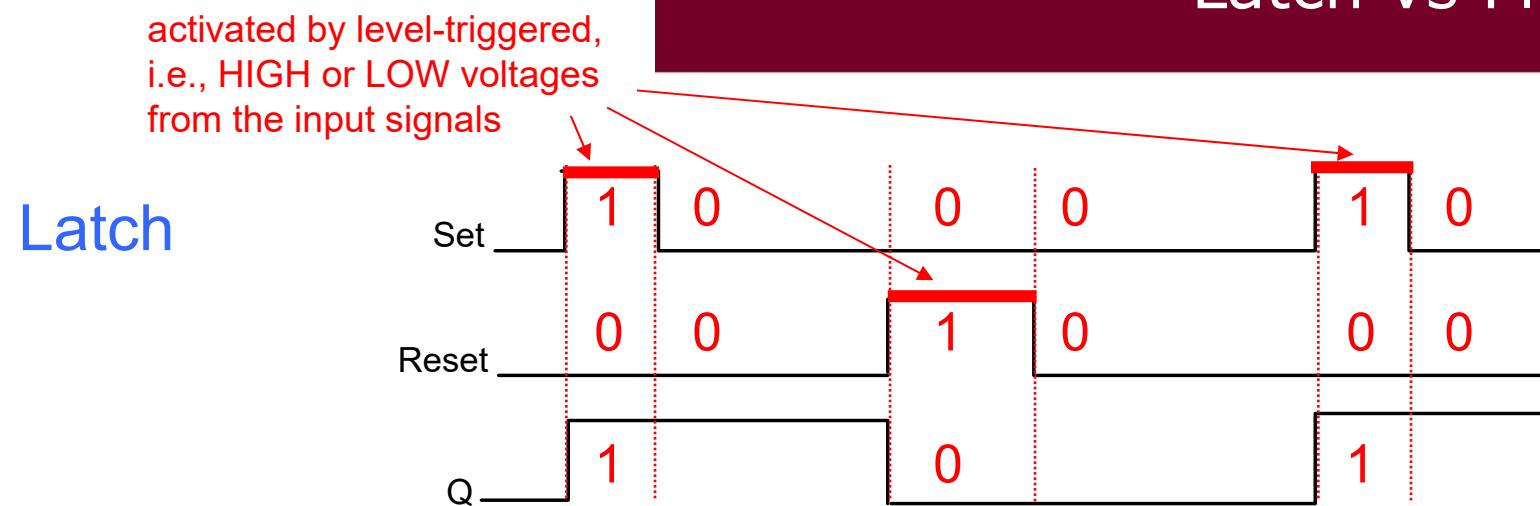


Type of Flip-Flops

(Positive edge-triggered)

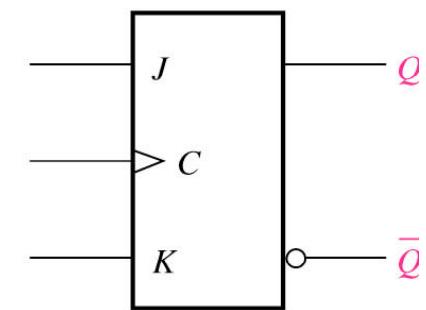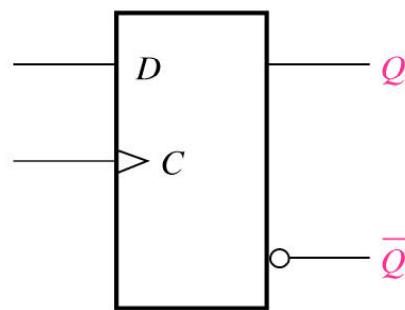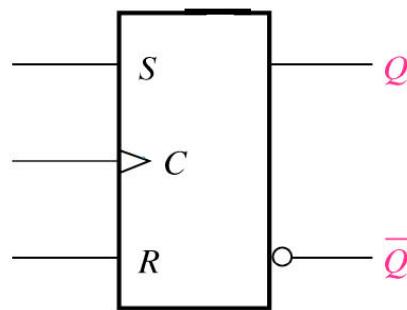

(Negative
edge-
triggered)

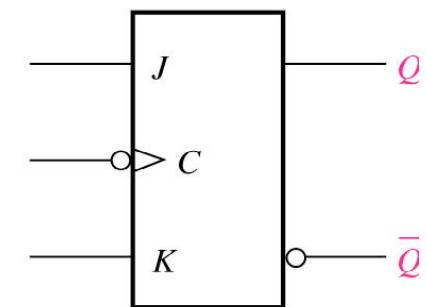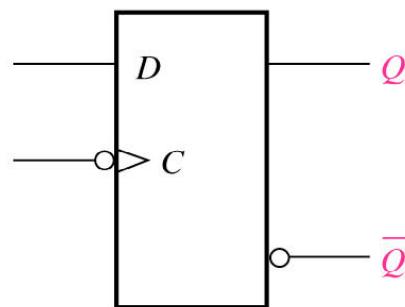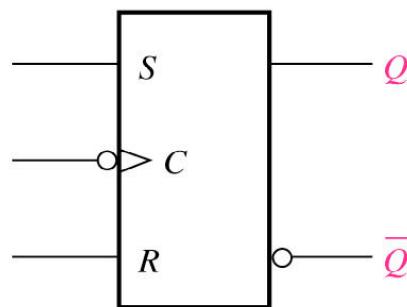


(a) S-R


(b) D

(c) J-K


(i) S-R Flip-Flop

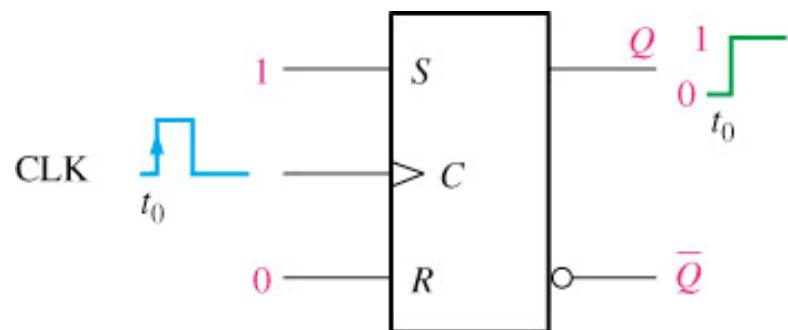

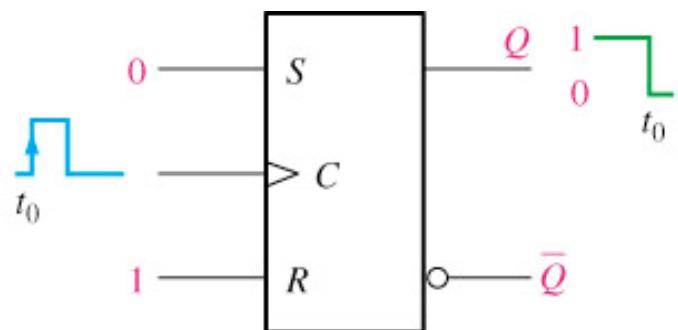
(a) $S = 1, R = 0$ flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



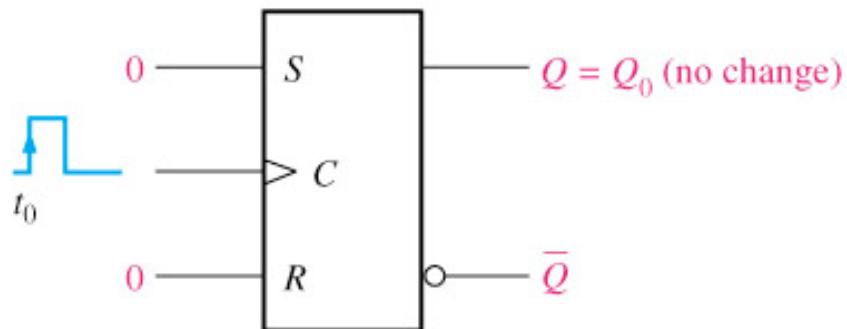(b) $S = 0, R = 1$ flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)



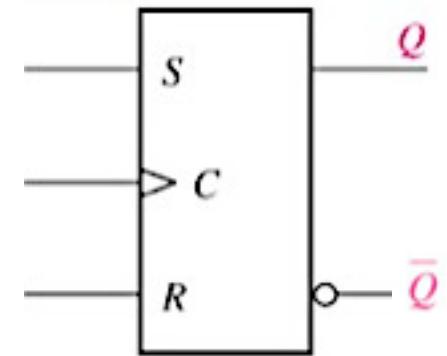(c) $S = 0, R = 0$ flip-flop does not change. (If SET, it remains SET; if RESET, it remains RESET.)





S	R	CLK	Output		Comments
			Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No Change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	?	?	Invalid

TRUTH TABLE

↑ = clock transition LOW to HIGH

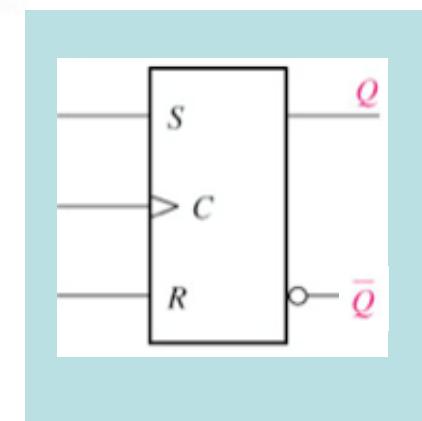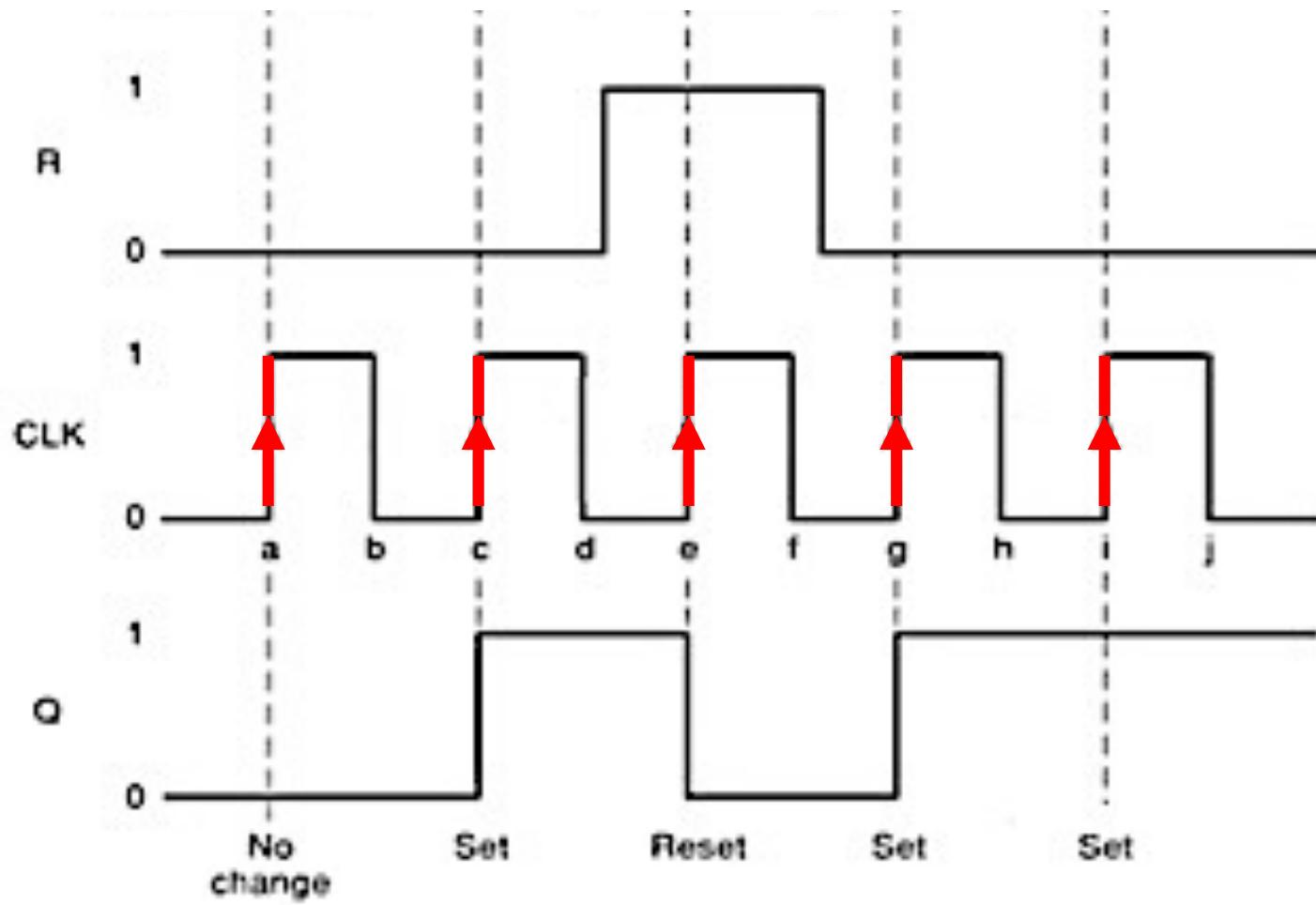
Q_0 = output level prior to clock transition



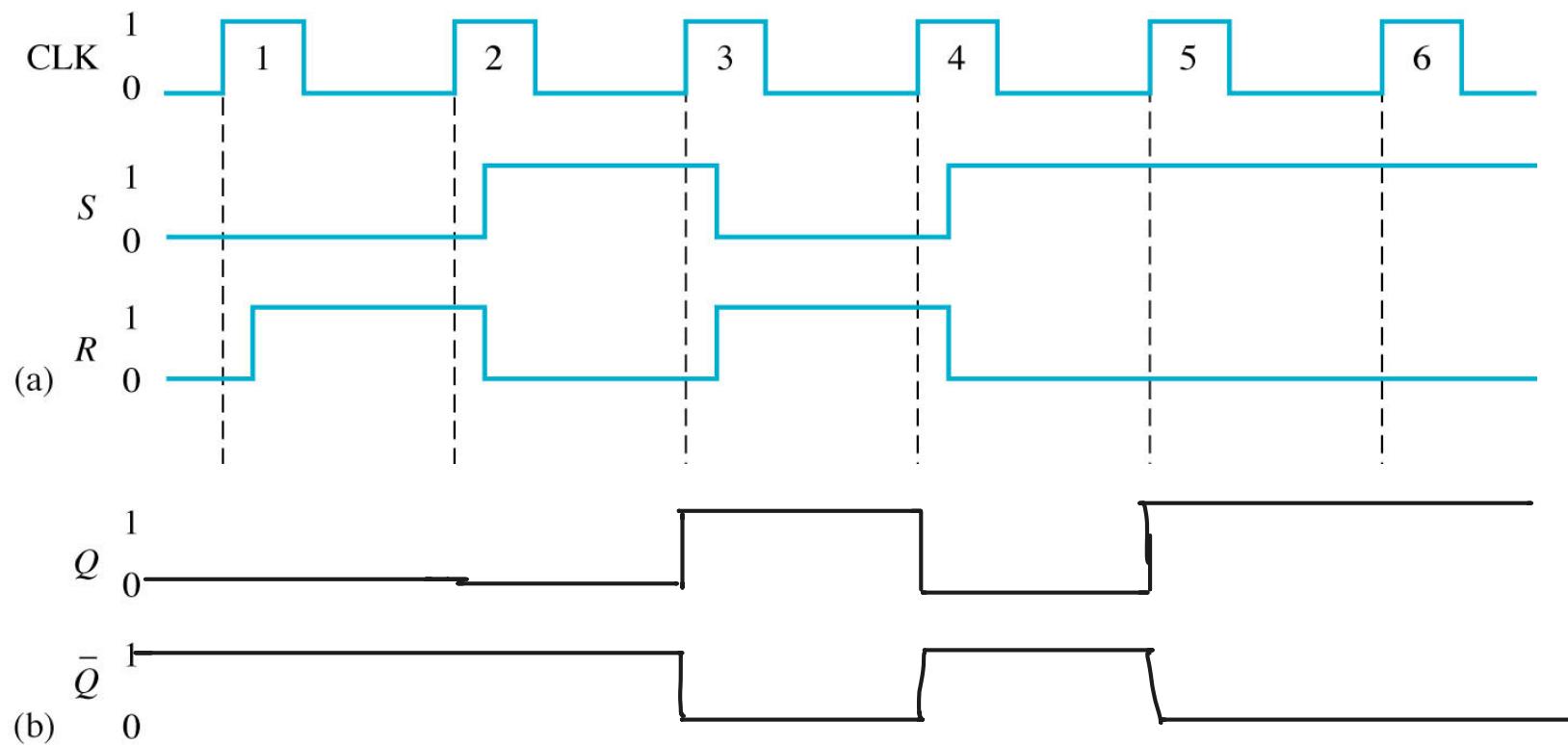Example: S-R Flip-Flop.

Find the waveform for Q and \bar{Q} .

Assume that the positive edge-triggered flip-flop is initially RESET.






S-R Flip-Flop.

Find the waveform for Q and Q bar.

Assume that the positive edge-triggered
, flip-flop is initially RESET.

Solution:

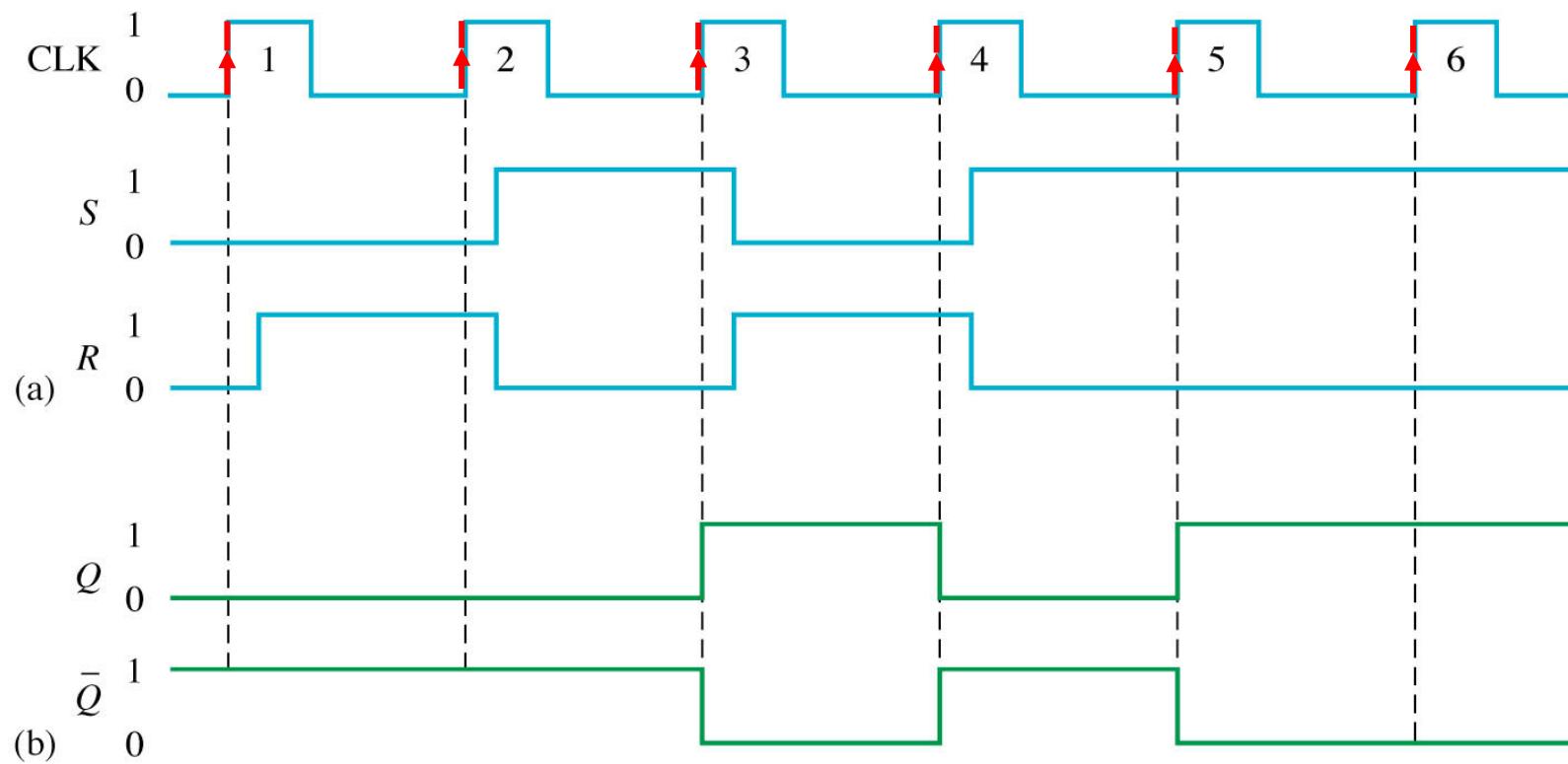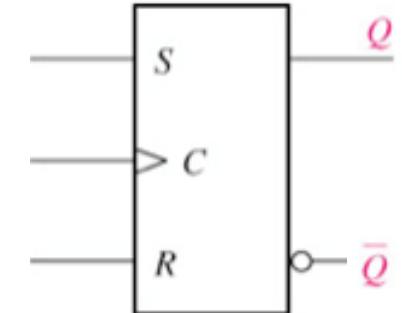

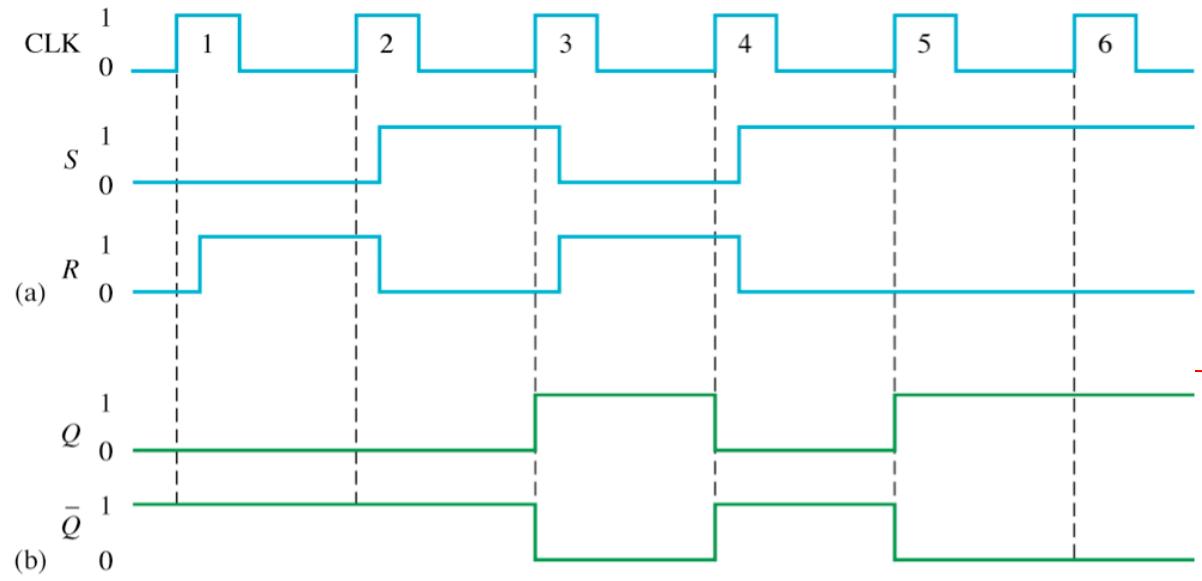


Once Q is determined, \bar{Q} is easily found since it is simply the complement of Q .

Clock Pulse	S	R	Q
1	0	0	Does not change
2	0	1	LOW (RESET)
3	1	0	HIGH (SET)
4	0	1	LOW (RESET)
5	1	0	HIGH (SET)
6	1	0	Stay HIGH

Exercise 7.3:


Given the inputs S and R for Gated S-R Latch with the output Q_1 , and for flip-flop with output Q_2 . Find the waveforms for Q_1 and Q_2 . Assume that both outputs are initially LOW and the flip-flop activated at positive edge-triggered.

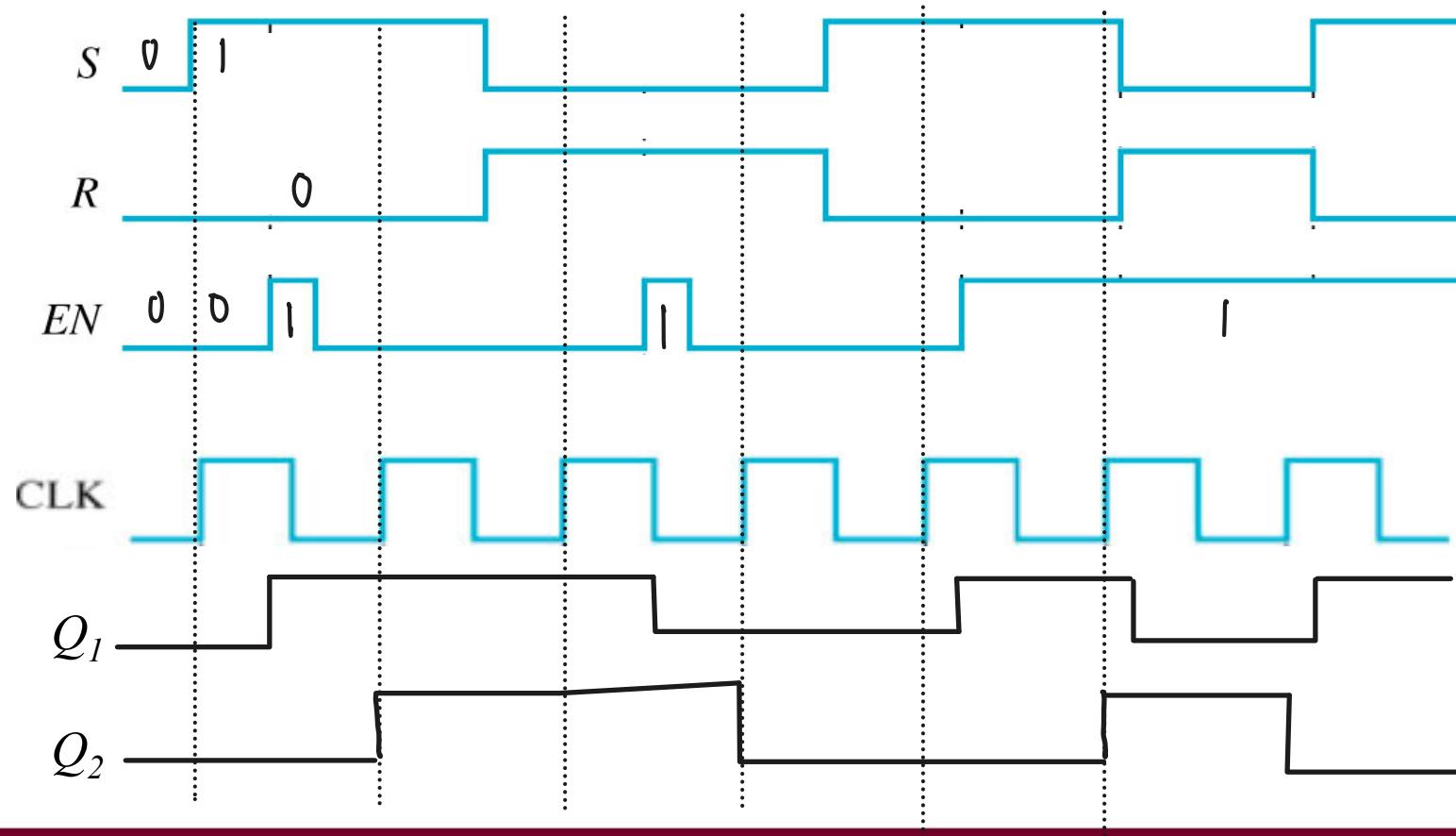

Solution 7.3:


Gated S-R Latch with the output Q_1

-> waveforms for Q_1 :

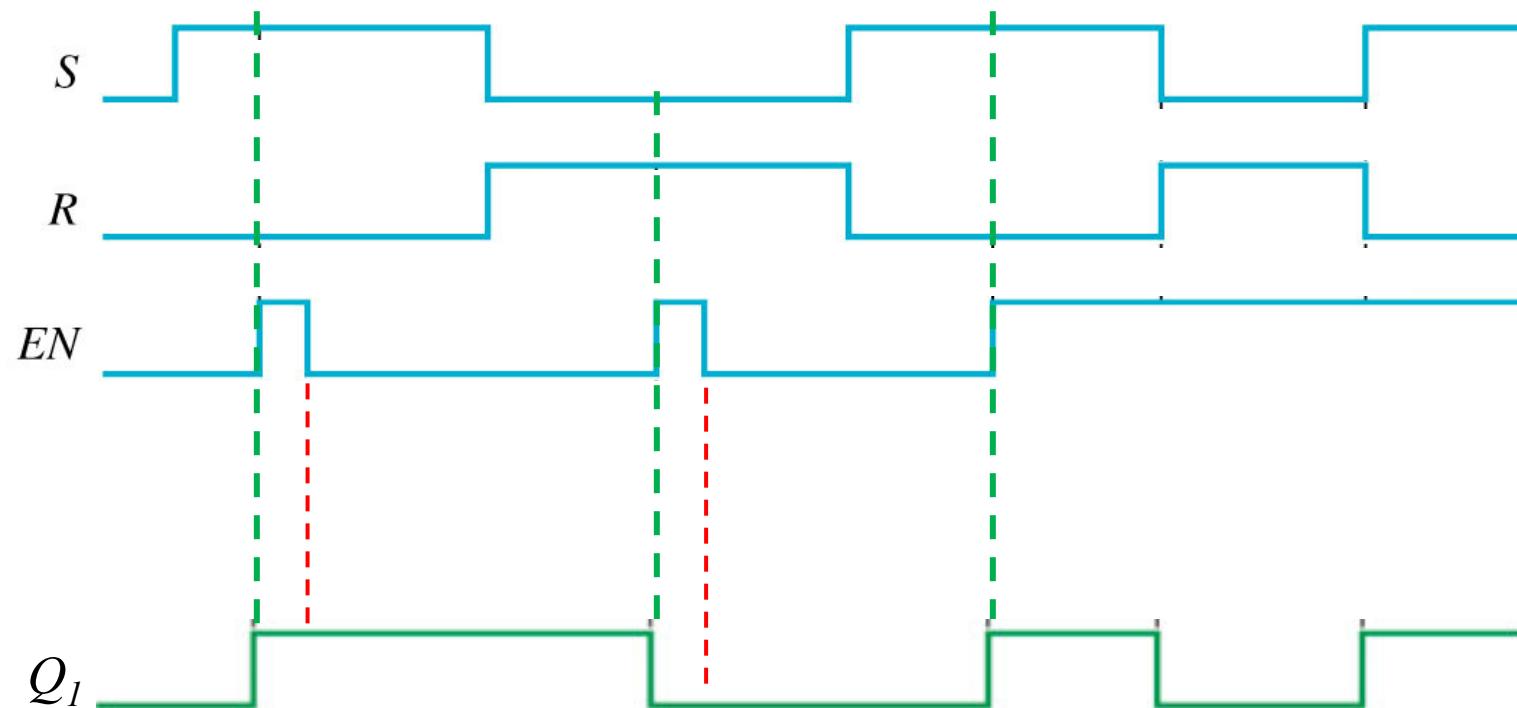


Solution 7.3:

Flip-flop with output Q_2 and activated at positive edge-triggered
-> waveforms for Q_2 :

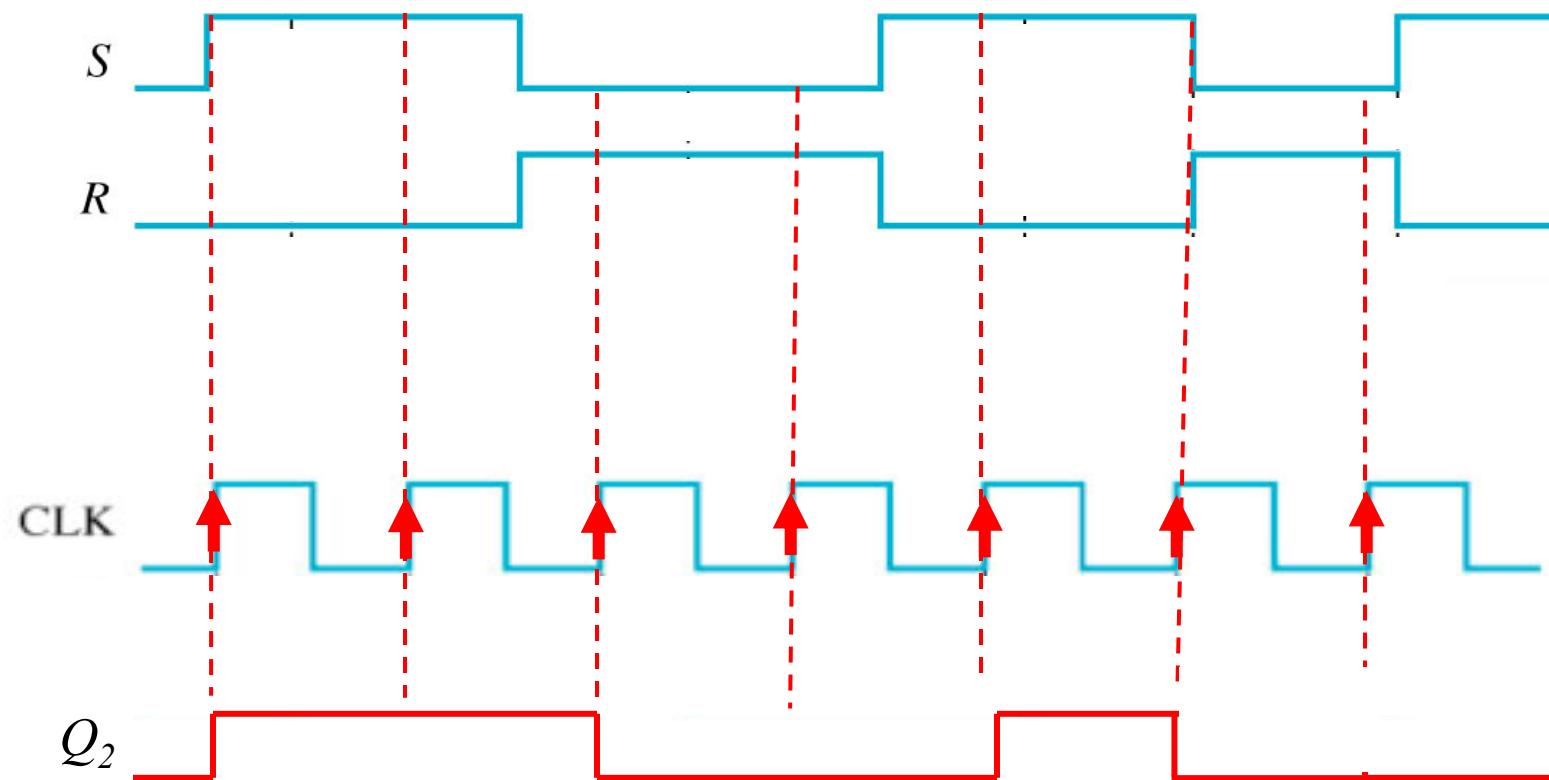


Solution 7.3:

Combined waveforms for Q_1 and Q_2 :

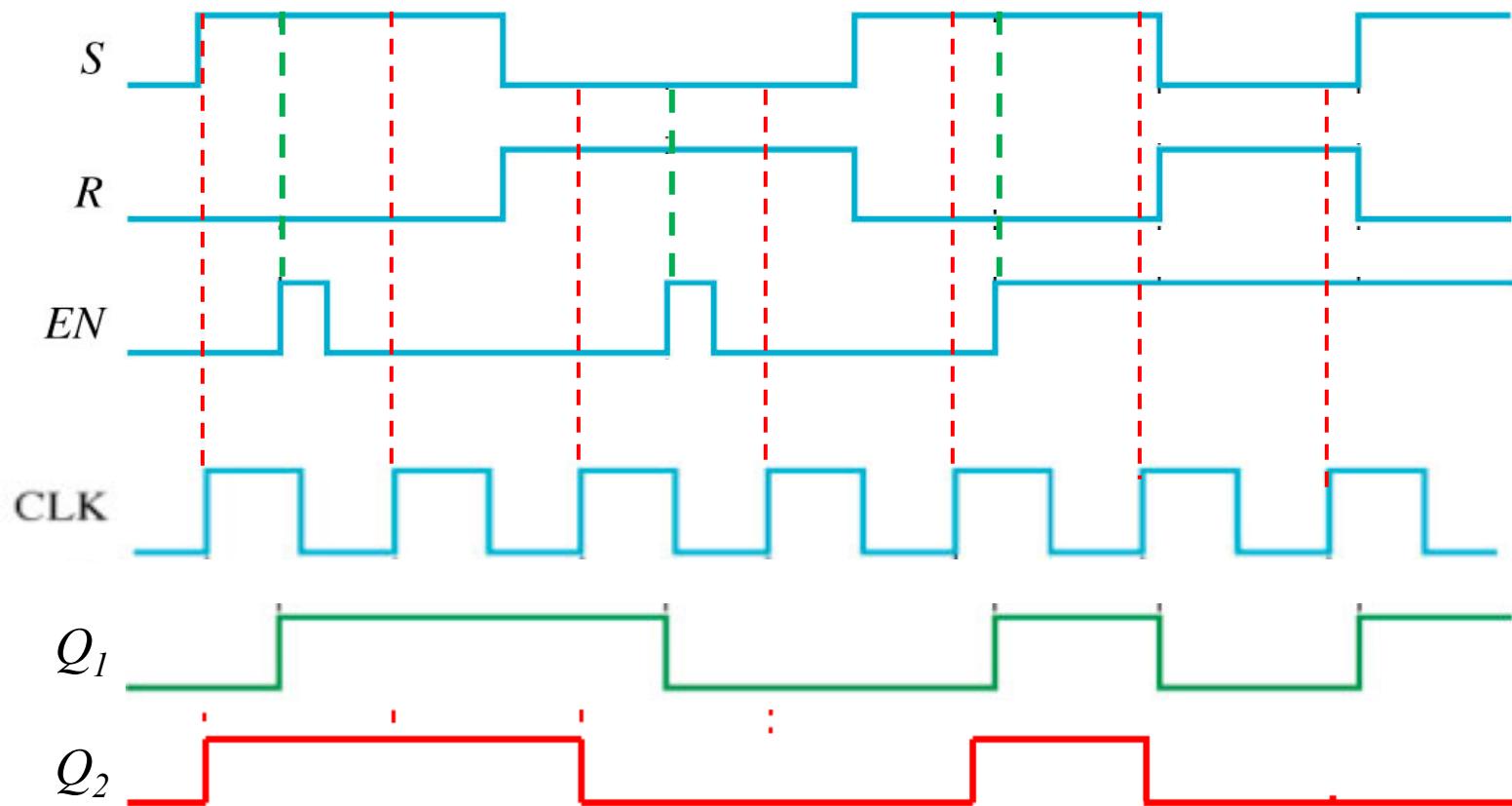


Self-Test:

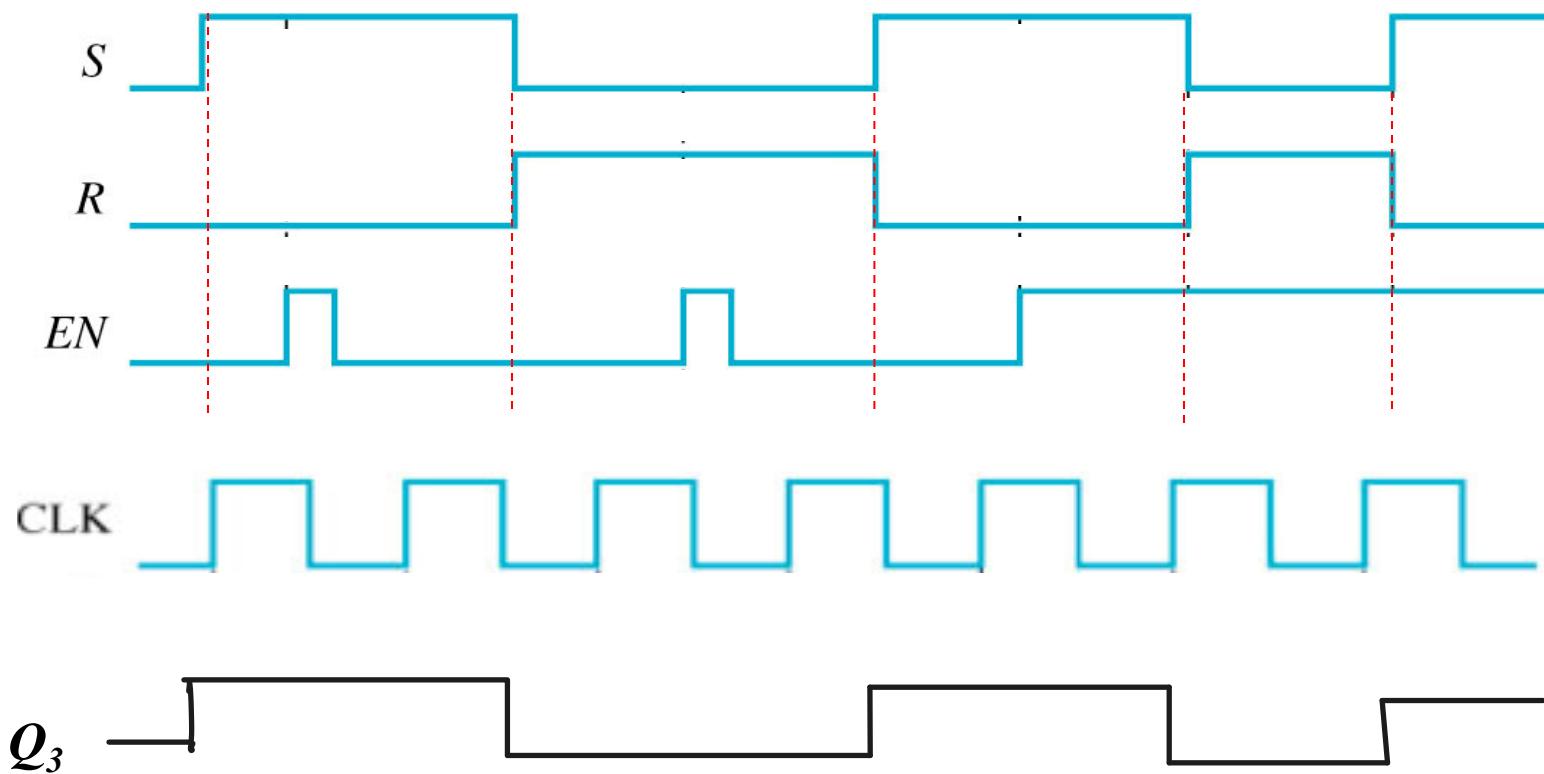If a S-R Latch is used with output Q_3 , find the waveforms for Q_3 . Is the waveform Q_3 similar to the waveform Q_1 in Exercise 7.3. Justify your answer. Assume that the outputs are initially LOW.




Self-Test:

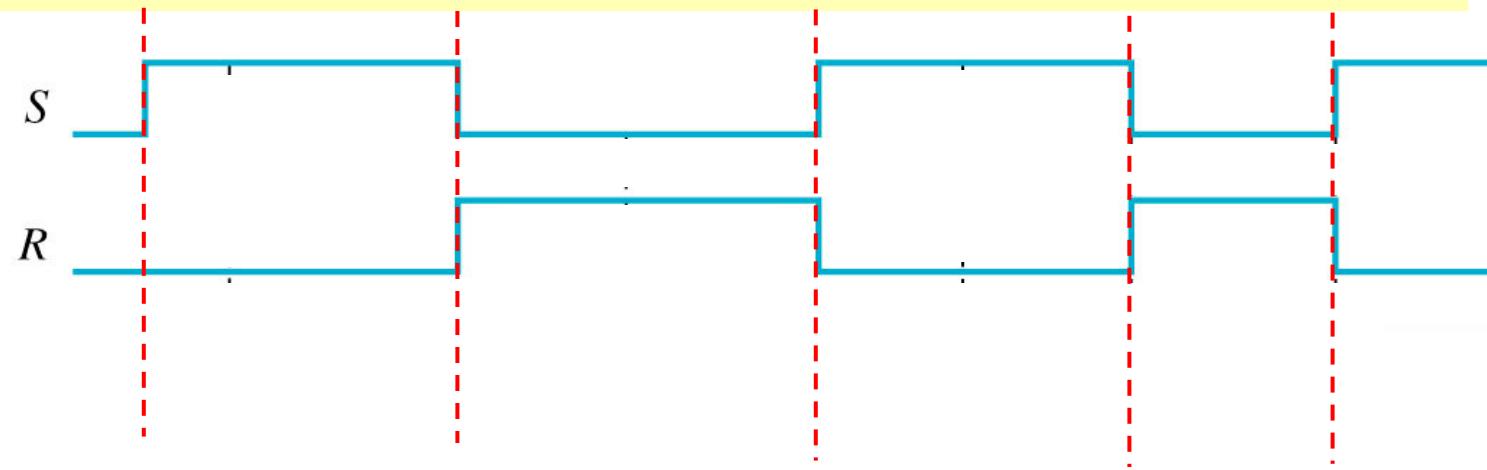S-R Latch is used with output Q_3 , ... the waveforms for Q_3 .




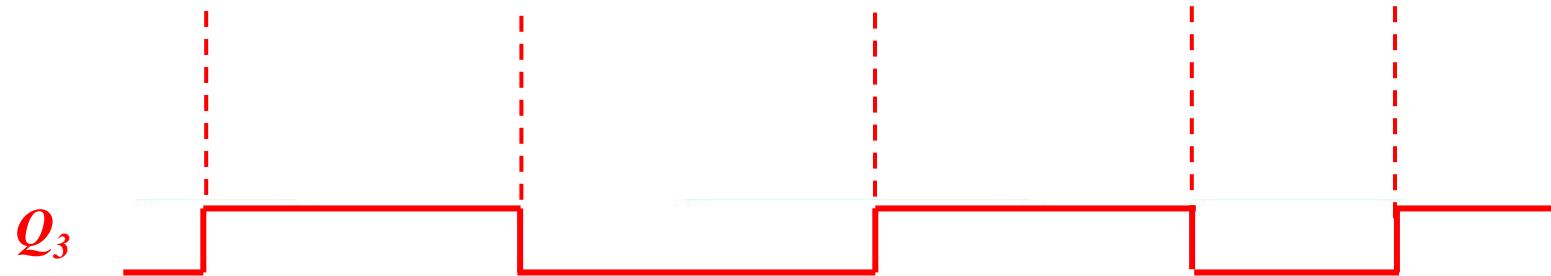S-R Latch **no need** the **EN** switch to produce the output Q_3



Self-Test:

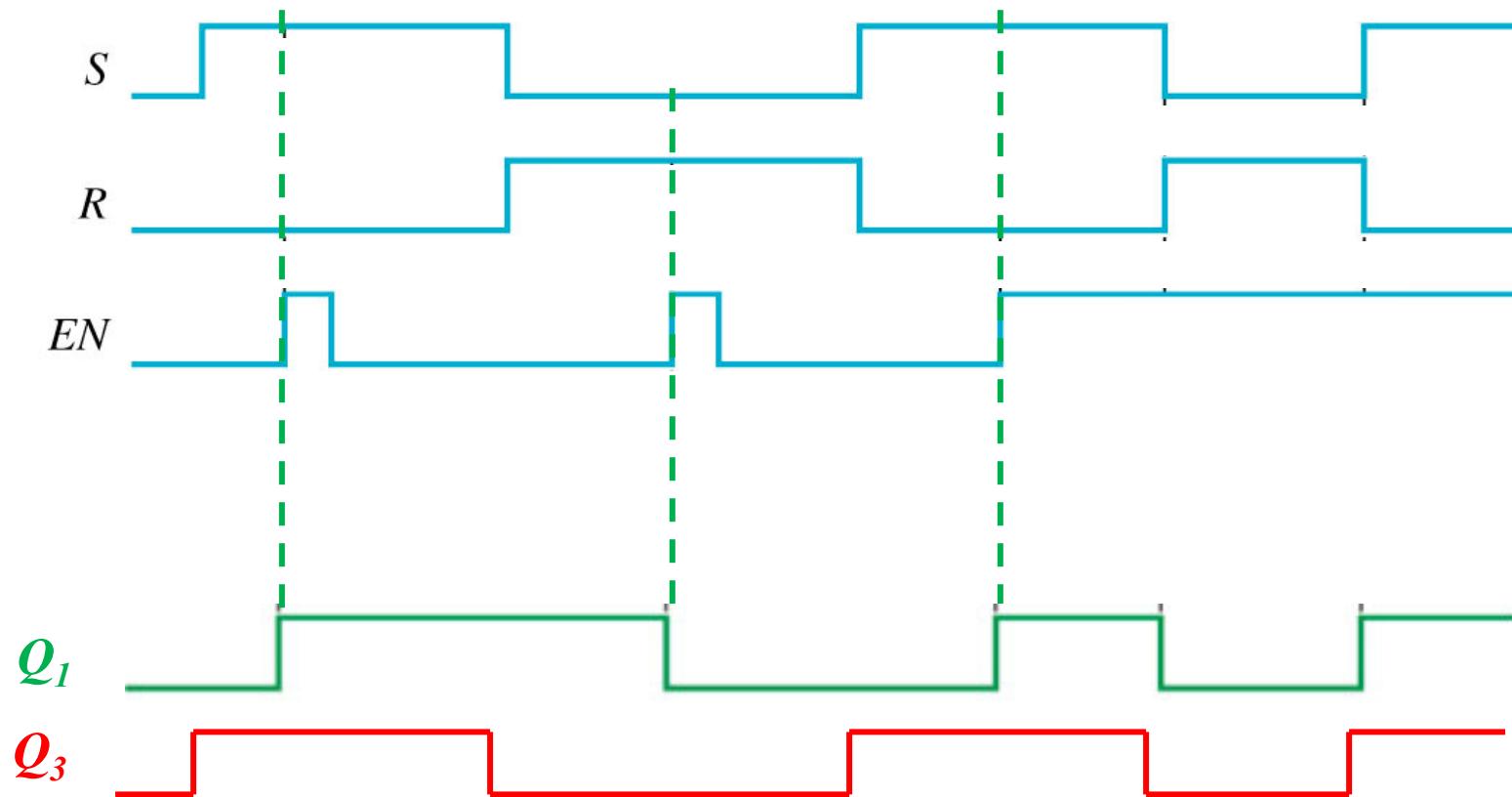
Is the waveforms Q_3 similar to the waveform Q_1 in Exercise 7.3 ? Justify your answer.






- The JK FF is versatile and is a widely used type of FF.
- The difference between J-K and S-R:

J-K has **no invalid state** as S-R.

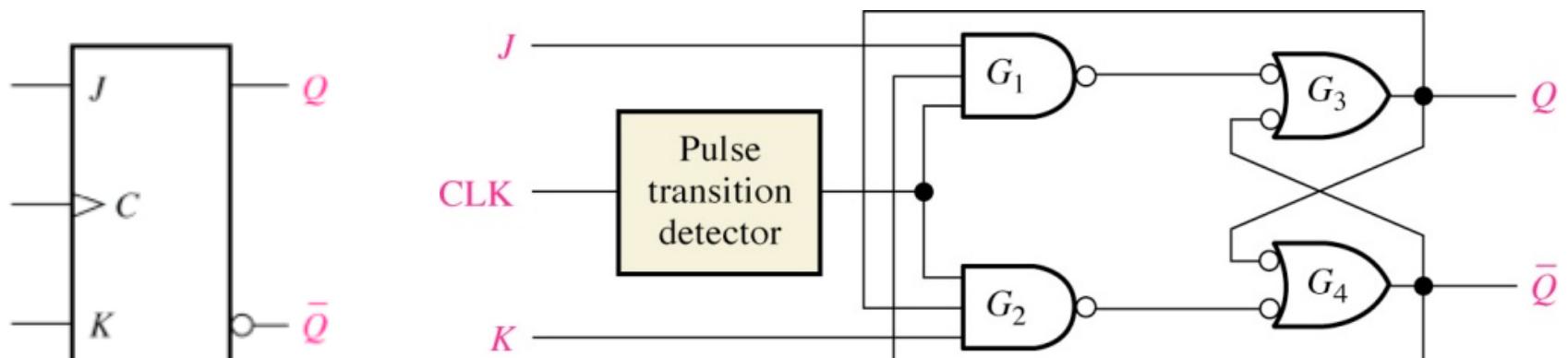

Logic Symbol

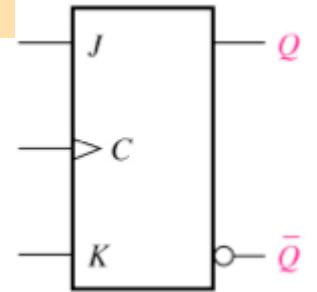

Logic symbol

J	K	CLK	Output		Comments
			Q	\bar{Q}	
0	0	\uparrow/\downarrow	Q_0	\bar{Q}_0	No Change
0	1	\uparrow/\downarrow	0	1	RESET
1	0	\uparrow/\downarrow	<u>1</u>	0	SET
1	1	\uparrow/\downarrow	\bar{Q}_0	Q_0	Toggle


TRUTH TABLE

\uparrow = clock transition LOW
to HIGH

Q_0 = output level prior to
clock transition

Example: J-K Flip-Flop.
Find the waveform for Q.
Assume that Q is initially LOW.

Positive
or
negative
triggered?

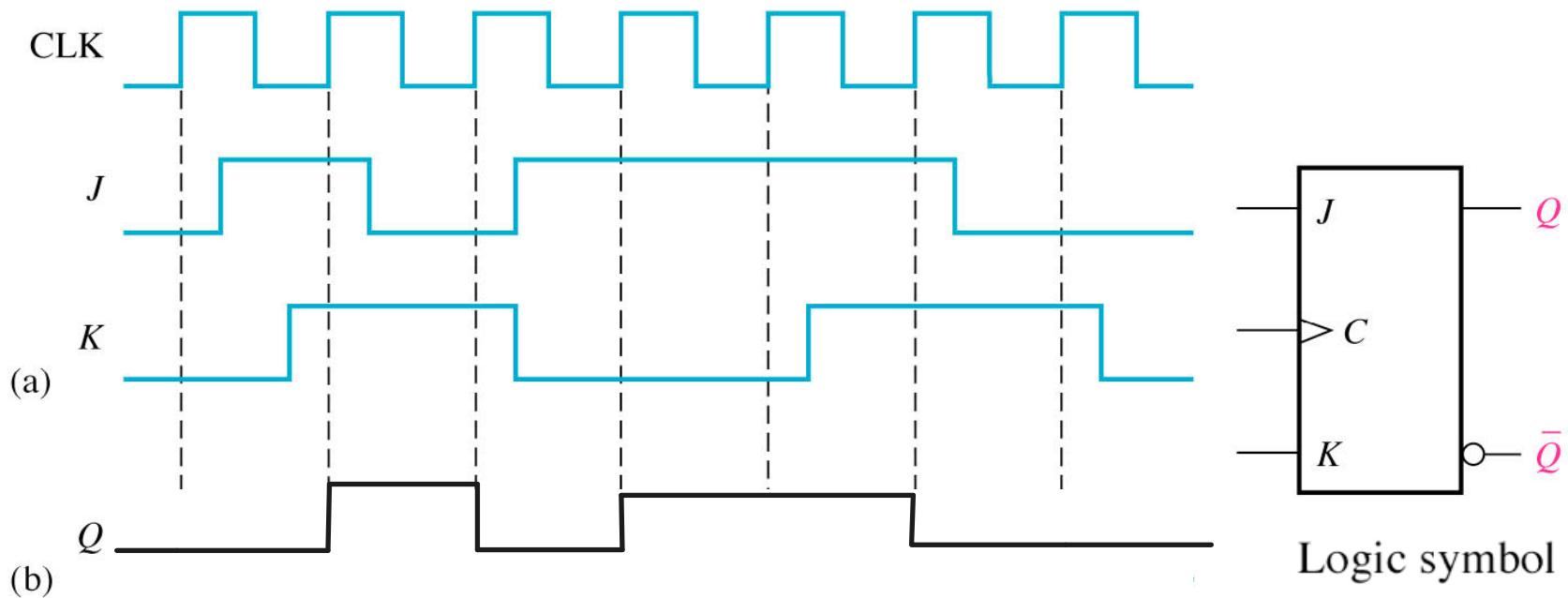


Solution:

J	K	CLK	Output		Comments
			Q	\bar{Q}	
0	0	\uparrow/\downarrow	Q_0	\bar{Q}_0	No Change
0	1	\uparrow/\downarrow	0	1	RESET
1	0	\uparrow/\downarrow	1	0	SET
1	1	\uparrow/\downarrow	\bar{Q}_0	Q_0	Toggle


Positive triggered

When the output toggled?

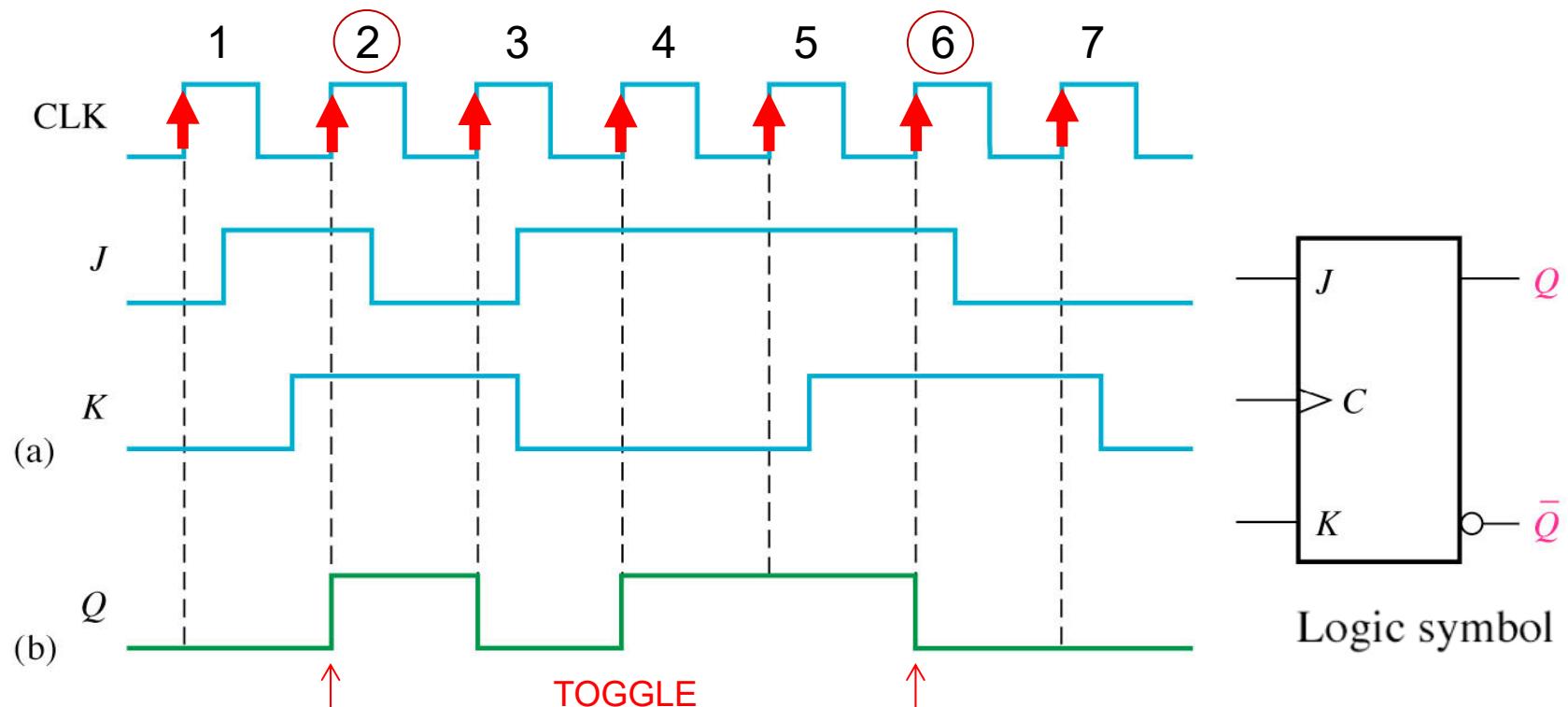

Example: J-K Flip-Flop.
Find the waveform for Q.
Assume that Q is initially LOW.



Positive
or
negative
triggered?

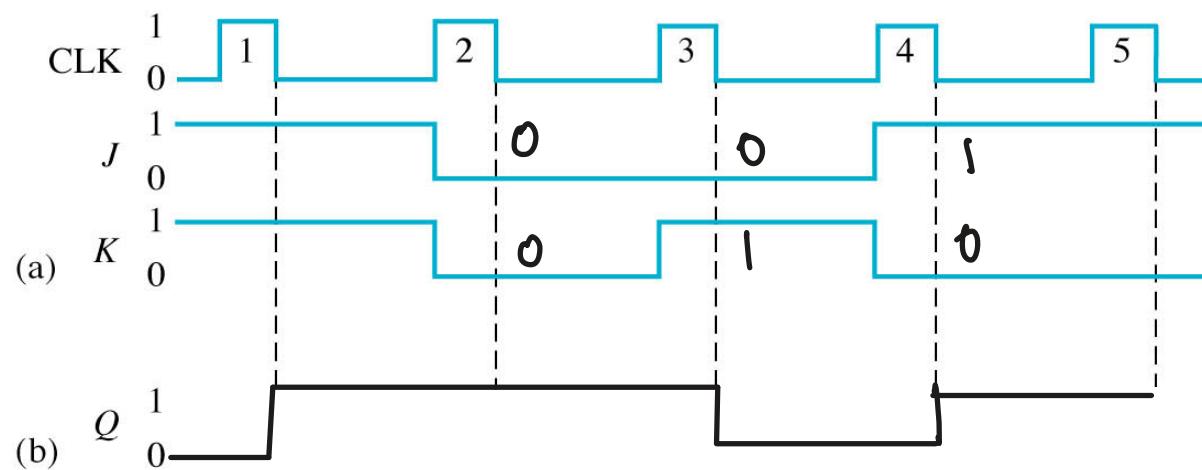

Solution:

J	K	CLK	Output		Comments
			Q	\bar{Q}	
0	0	↑/↓	Q_0	\bar{Q}_0	No Change
0	1	↑/↓	0	1	RESET
1	0	↑/↓	1	0	SET
1	1	↑/↓	\bar{Q}_0	Q_0	Toggle



negative triggered

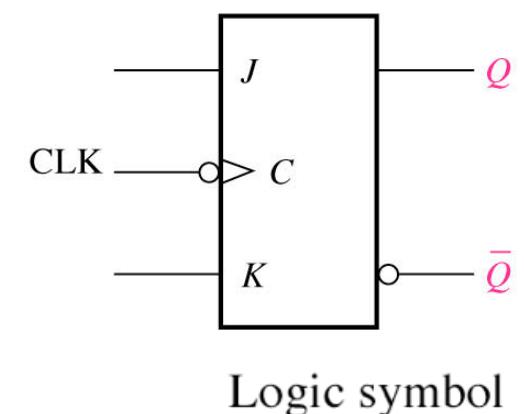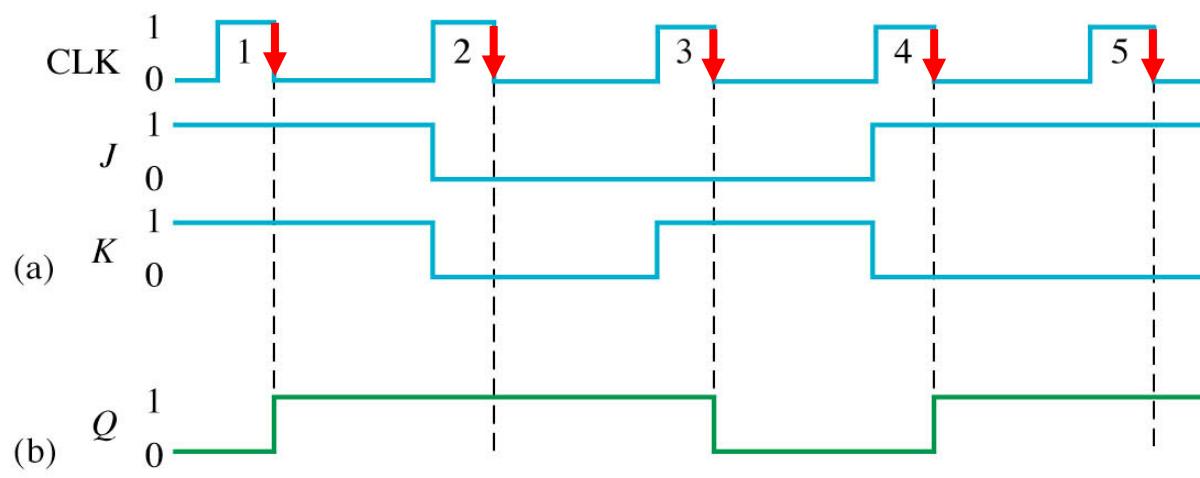



D → Data or Delay

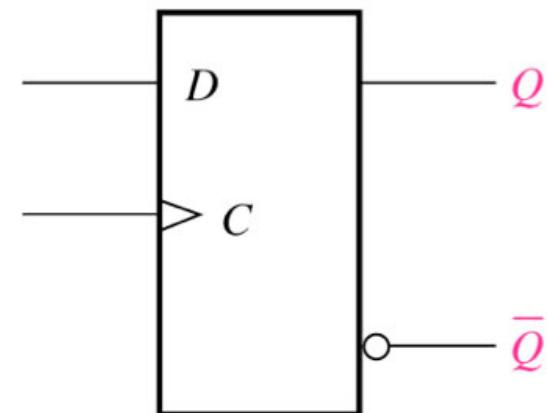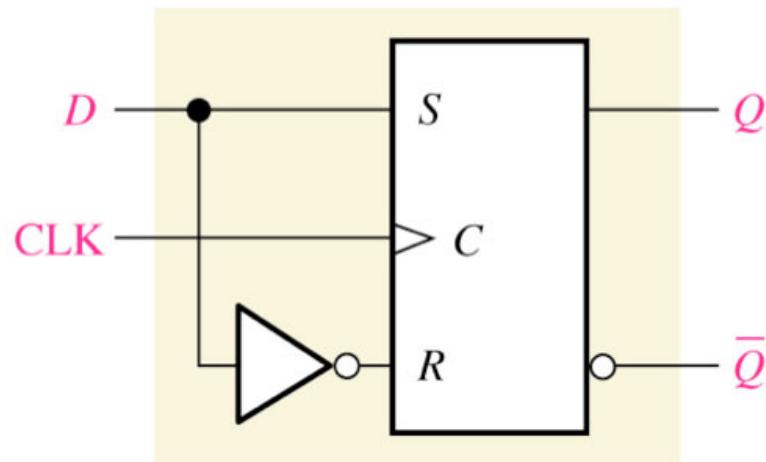- D FF is useful when a single data bit (1 or 0) is to be stored.
- The addition of an **inverter** to an S-R FF creates basic D FF where a **positive edge-triggered** type is shown below:




Logic symbol


TRUTH TABLE

INPUTS		OUTPUTS		COMMENTS
D	CLK	Q	\bar{Q}	
1	↑	1	0	SET (store a 1)
0	↑	0	1	RESET (store 0)

(for positive edge-triggered)

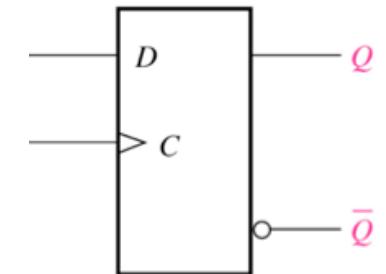



Logic symbol

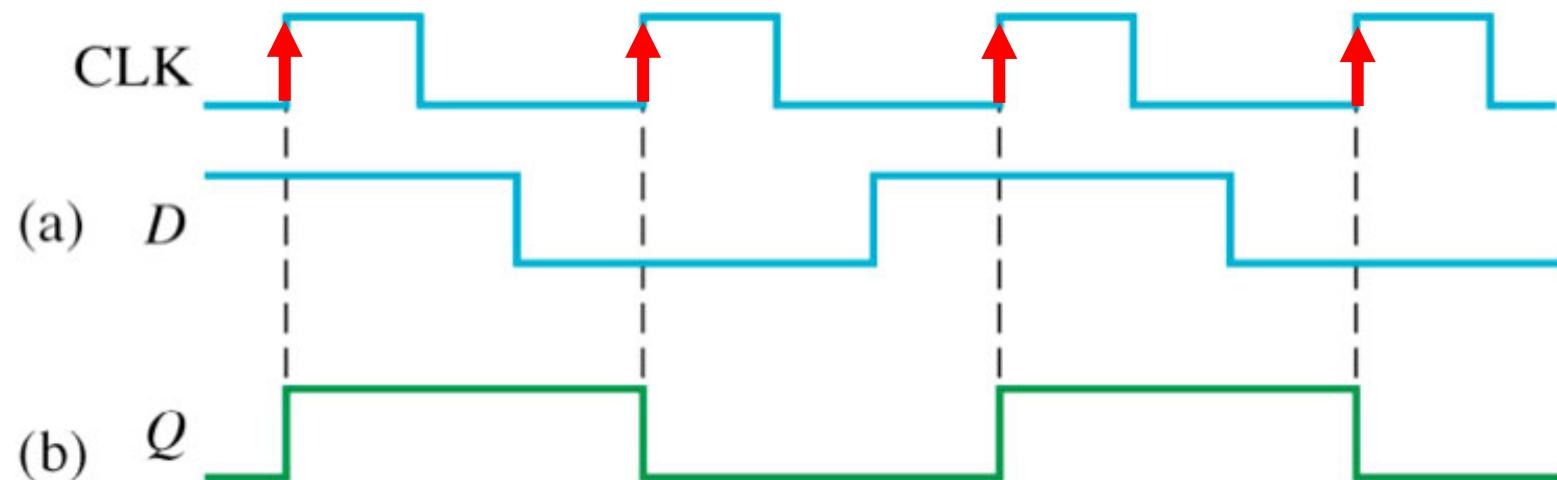

Remember, Q follows D at the active triggering clock edge.



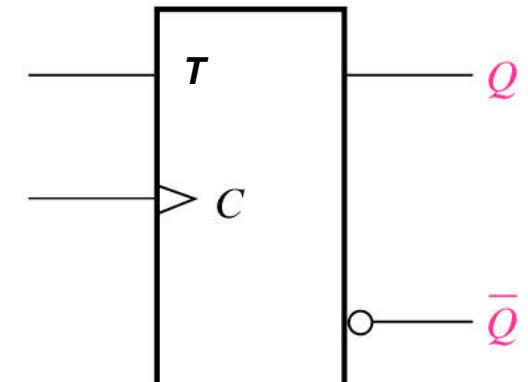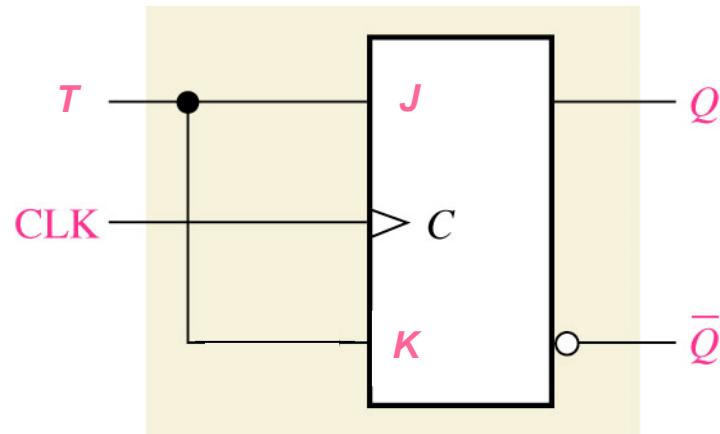
- Also called as **toggle flip-flop**.
- Frequently used in building **counters**.



Logic Symbol


TRUTH TABLE

T	CLK \uparrow/\downarrow	Output		Comments
		Q	Q_{next}	
0	\uparrow/\downarrow	0	0	HOLD
0	\uparrow/\downarrow	1	1	HOLD
1	\uparrow/\downarrow	0	1	TOGGLE
1	\uparrow/\downarrow	1	0	TOGGLE

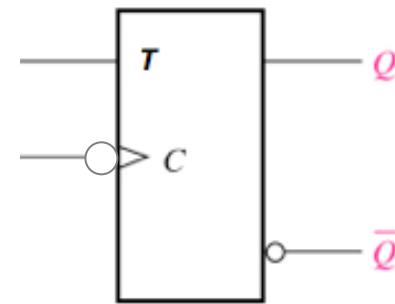

Logic symbol

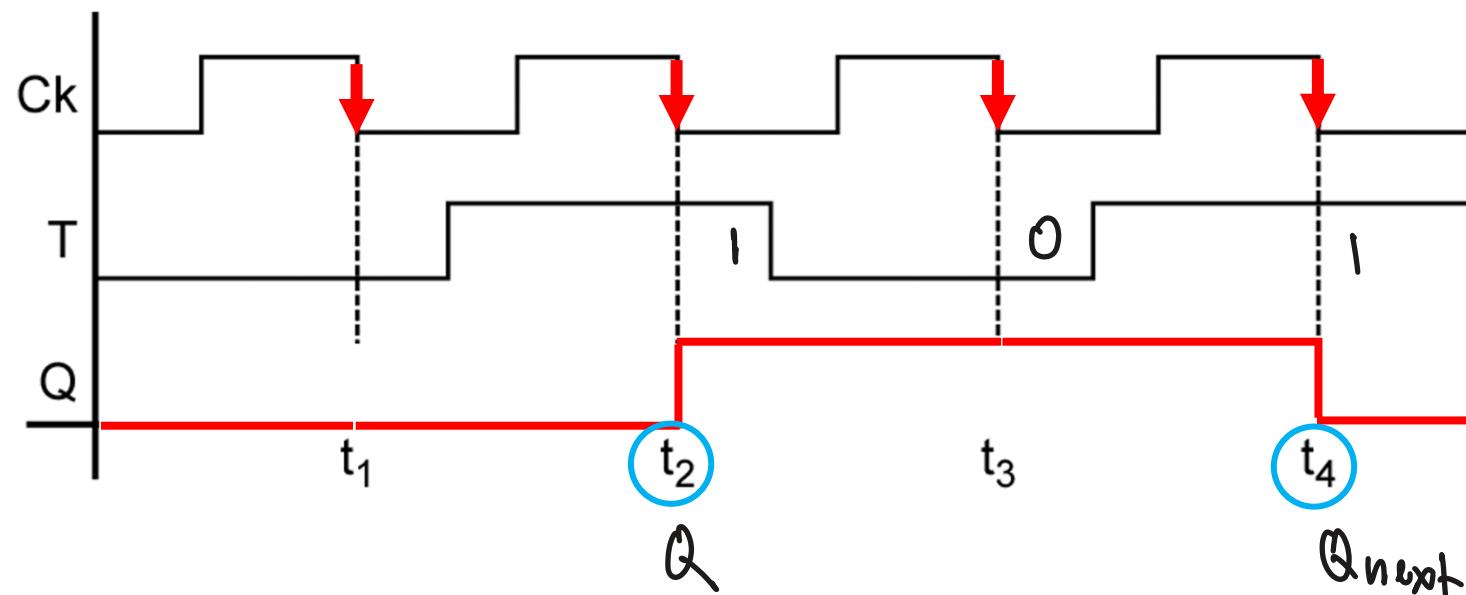
Timing Diagram for T Flip-Flop (Negative-Edge Triggered)




Homework

Try :

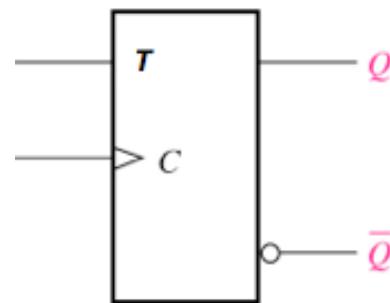
Consider a positive-edge trigger for a T-FF. Draw the waveforms for Q. Assume that the output is initially LOW.



Logic symbol

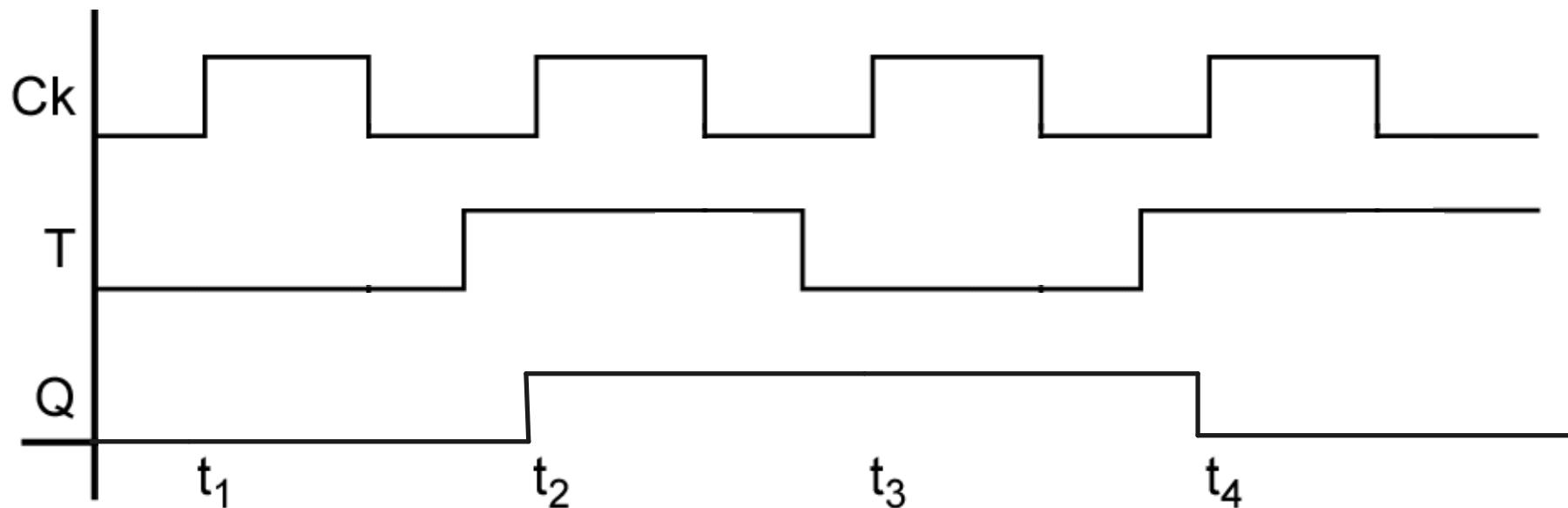


Exercise 7.4:

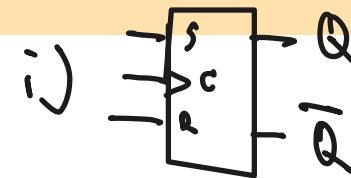

Homework

Given the inputs S and R for flip-flop with the inputs always complement to each other and activated at negative edge-triggered.


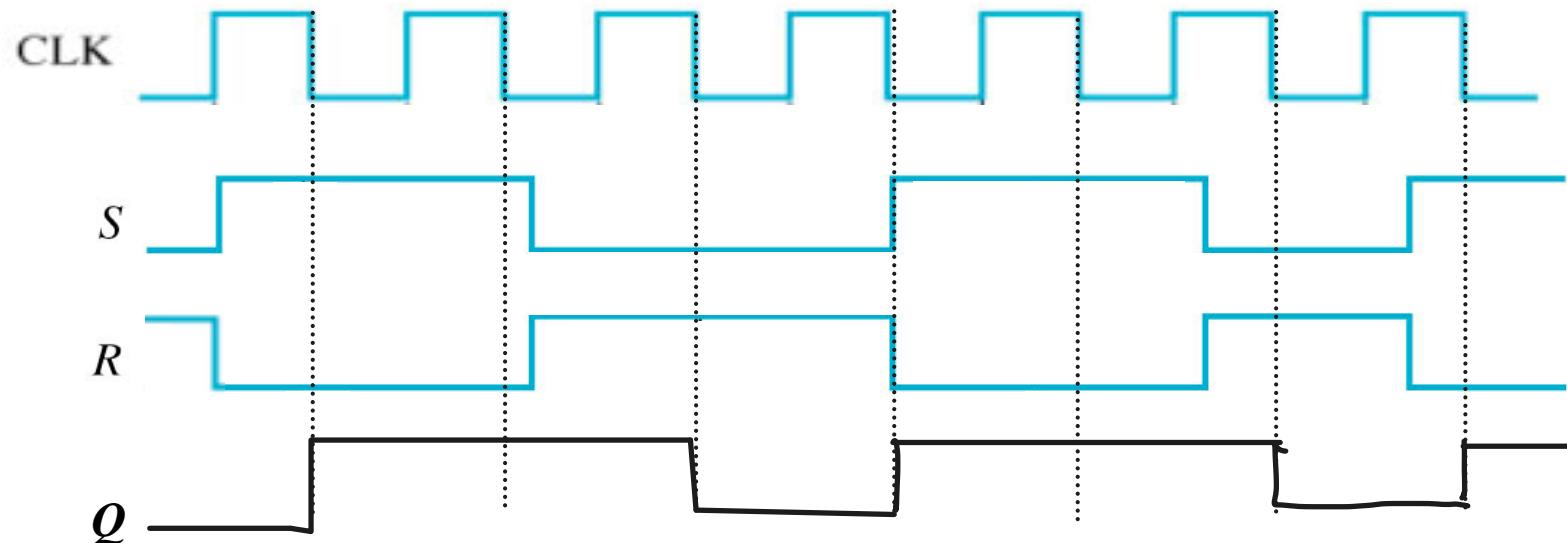
- Draw the logic symbol for the flip-flop.
- Find the waveforms Q. Assume that the output is initially LOW.






JK Flip Flop with Asynchronous Input

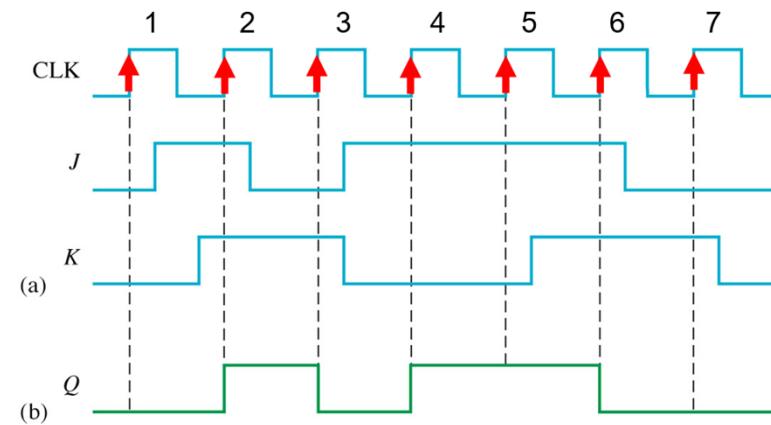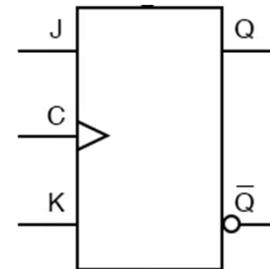- The J and K inputs are called **synchronous inputs** since they only influence the state of the flip flop when the **clock** input is present.
- Synchronous → J and K inputs transferred on the triggering edge of the clock






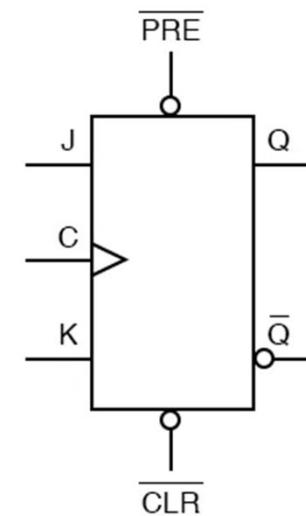- This flip flop can also have **other inputs** called **Preset** and **Clear** that can be used for *setting* the flip flop to **1** or *resetting* it to **0**.
- Asynchronous → These inputs can **change the state** of the flip flop regardless of the clock signal.
 - Preset ($\overline{\text{PRE}}$) or Direct SET
 - Clear ($\overline{\text{CLR}}$) or Direct RESET



TRUTH TABLE

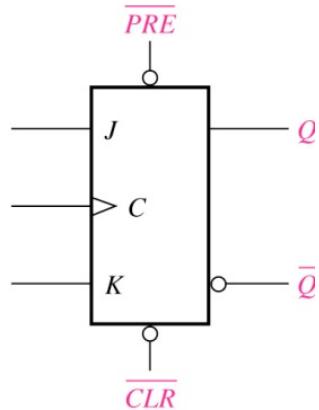

\overline{PRE}	\overline{CLR}	FF	MODE
0	1	SET	Asynchronous
1	0	RESET	Asynchronous
1	1	JK	Synchronous
0	0	-	-

FF Response:

$$Q = 1$$

$$Q = 0$$

FF Clock Working

Not Used

- **Flip-flop input priority:**


Priority	FF Input
Highest	$\overline{PRE}, \overline{CLR}$ (Asynchronous input)
Medium	Clock
Lowest	J-K, S-R, D, T (Synchronous input)
- Flip-flop asynchronous input has the highest priority.
 - Which means that if the asynchronous input active, the output will immediately change regardless the value of synchronous input or clock.

\overline{PRE}	\overline{CLR}	FF
0	1	SET
1	0	RESET
1	1	JK

(Module: page 231)

Note:

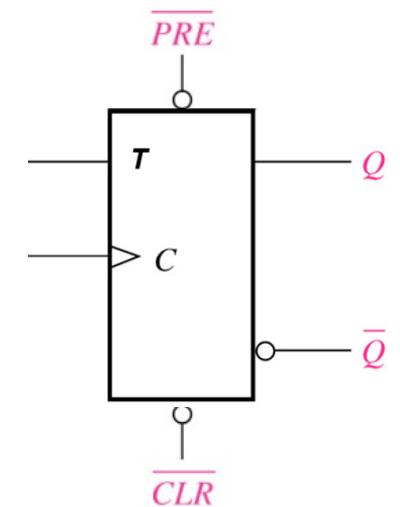
When $J = K = 1$,
it works as **T flip-flop**




Example: J-K Flip-Flop with both inputs are HIGH.

Find the waveform for Q.

Assume that Q is initially LOW.

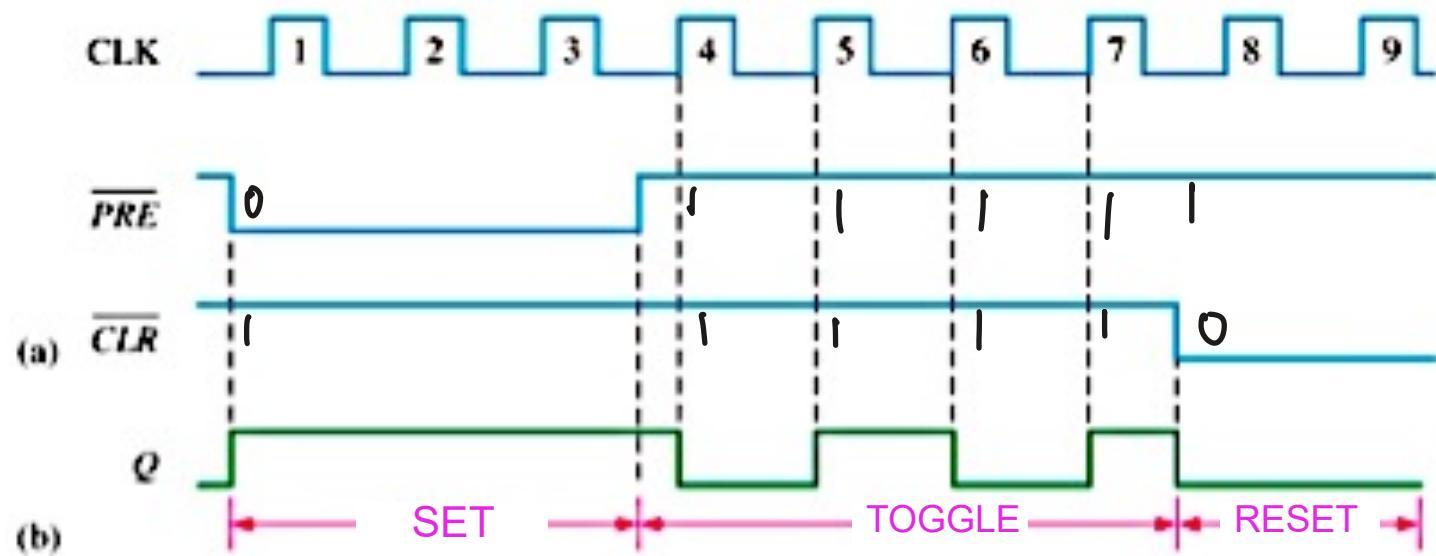

PRE	\overline{CLR}	FF	MODE
0	1	SET	Asynchronous
1	0	RESET	Asynchronous
1	1	JK	Synchronous

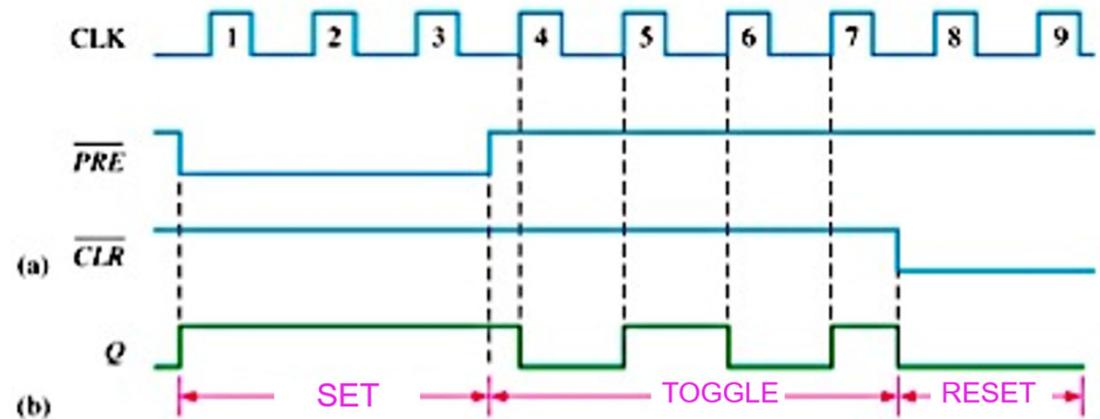


clk <i>pulse</i>	PRE	\overline{CLR}	J	K	FF	Comment
1,2,3	0	1	1	1	SET	JK inputs - dont care
4,5,6, 7	1	1	1	1	Toggle	Synchronous mode.
8,9	1	0	1	1	RESET	JK inputs - dont care

Homework

Exercise 7.5:

Find the waveform for Q.


Assume that asynchronous J-K FF is used with both inputs are HIGH, and Q is initially LOW.

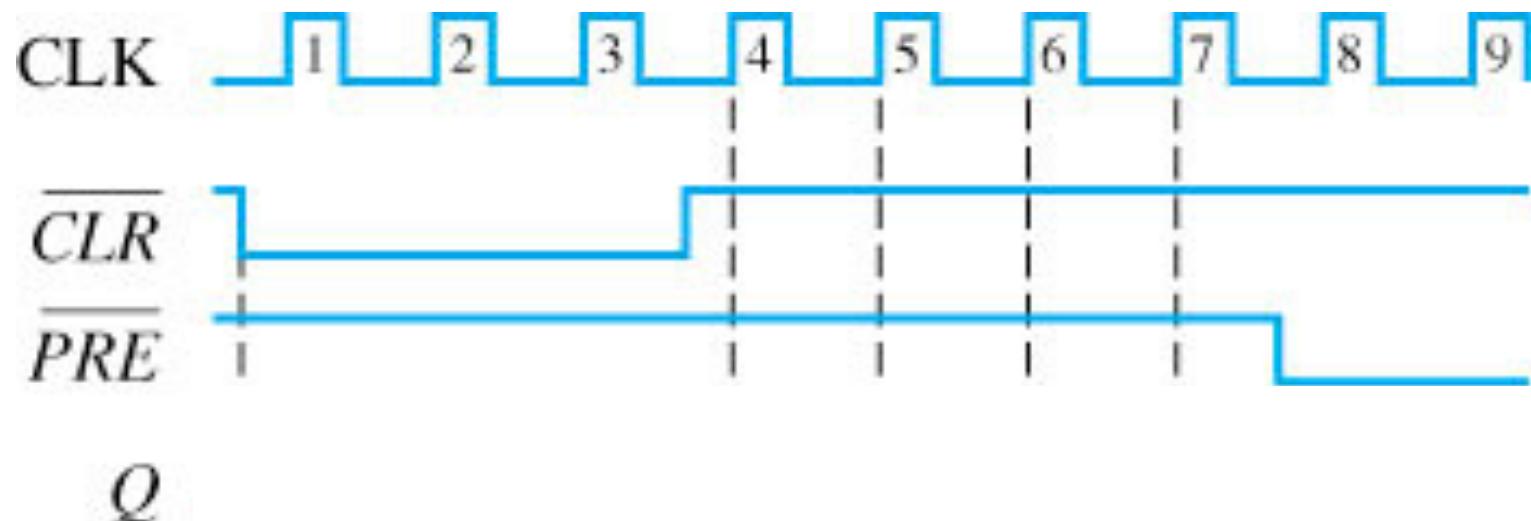

Exercise 7.6:

Find the waveform for Q for asynchronous J-K FF.

Assume that Q is initially HIGH.

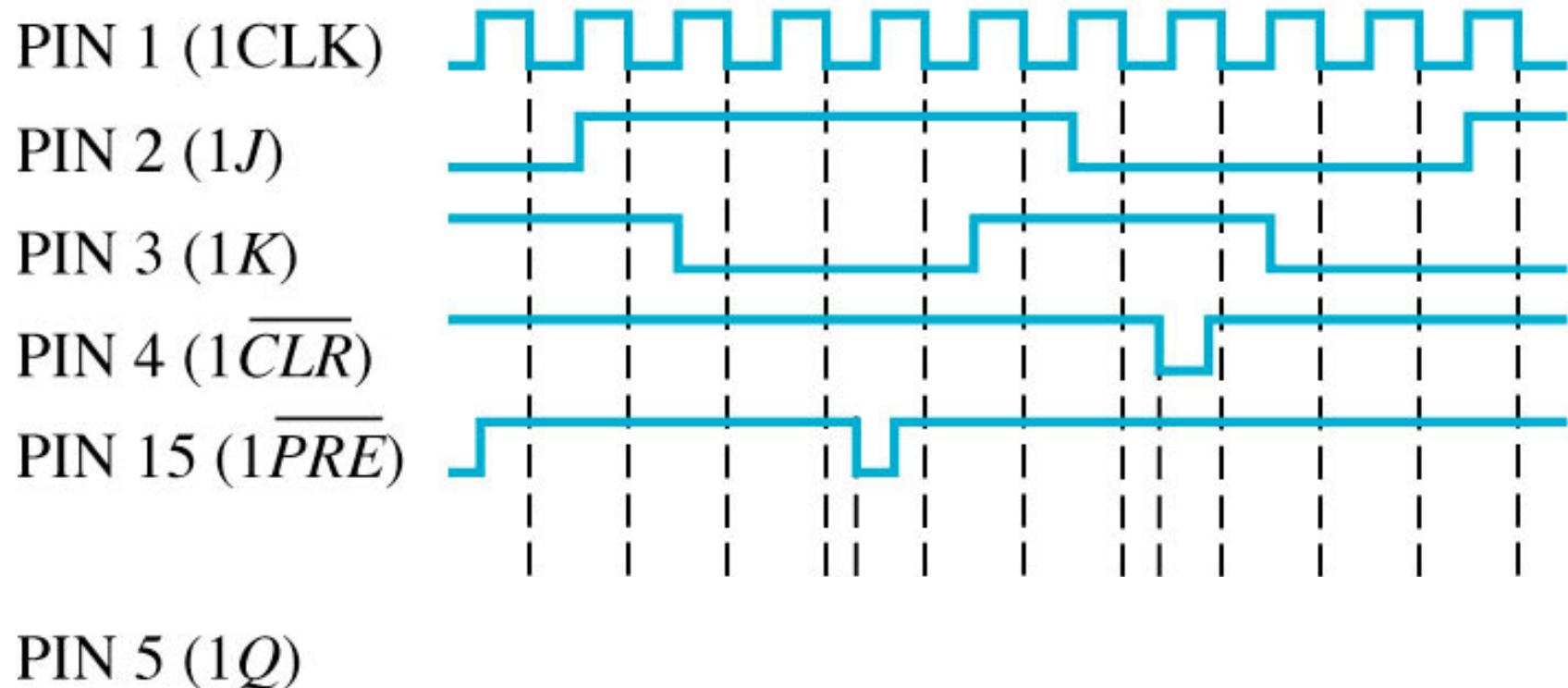

Homework

Exercise 7.7: Complete the table in sequence.

Assume a J-K flip-flop is used with \overline{PRE} and \overline{CLR} inputs, and output Q.

\overline{PRE}	\overline{CLR}	J	K	Q	Mode	Comment
1	1	1	0			
1	1	1	1			
0	1	0	1			
1	1	0	0			
1	0	1	0			
0	1	1	1			
1	1	0	0			
1	1	1	1			

Mode: (Asynchronous / Synchronous)

Comment: (SET / RESET / HOLD/ TOGGLED / PRESET / CLEAR / INVALID)



Summary

Latch & Flip-Flop

	Latch	Gated Latch	Flip-Flop
Output Characteristics	<p>Output / next state depends to:</p> <ul style="list-style-type: none">• current inputs &• previous outputs / state	<p>Output / next state depends to</p> <ul style="list-style-type: none">• enable gate input• current inputs• previous outputs / state	<p>Output / next state depends to:</p> <ul style="list-style-type: none">• edge-triggered clock• current inputs• previous outputs / state

S-R Latch/FF

Block Diagram


Basic Operation Truth-table

S	R	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	-	-


For:

- En = 1 (Gated Latch)
-  &  FF


Latch

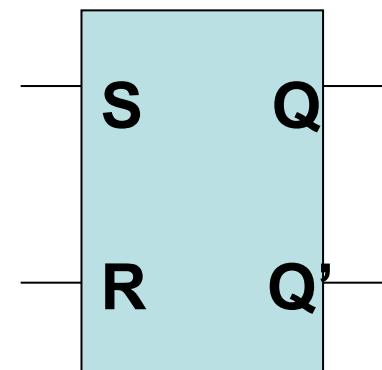

Gated Latch

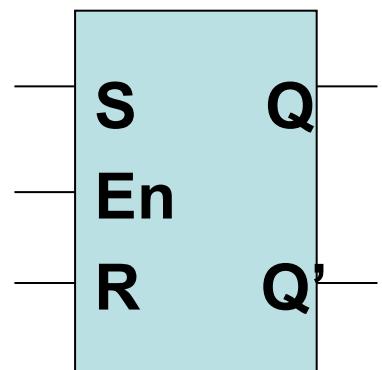

Flip-Flop

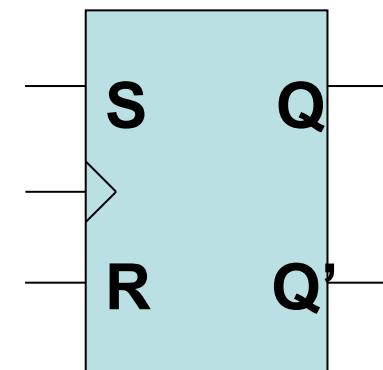

S	R	En	Q	Q'
0	0	1	Q	Q'
0	1	1	0	1
1	0	1	1	0
1	1	1	-	-
X	X	0	Q	Q'


D Latch/FF

Block Diagram


Basic Operation Truth-table

D	Q	Q'
0	0	1
1	1	0


Latch

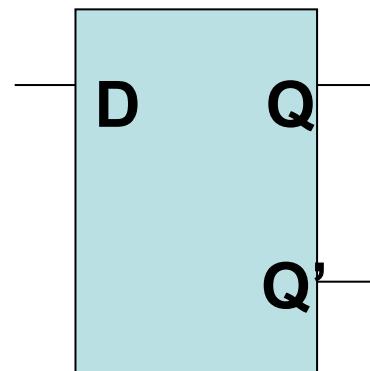

Gated Latch

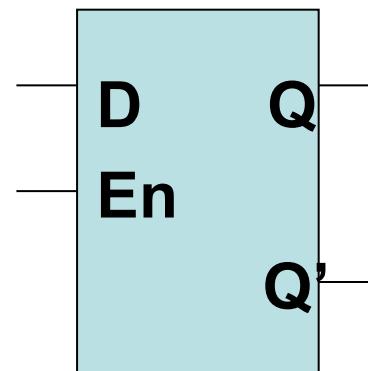

Flip-Flop

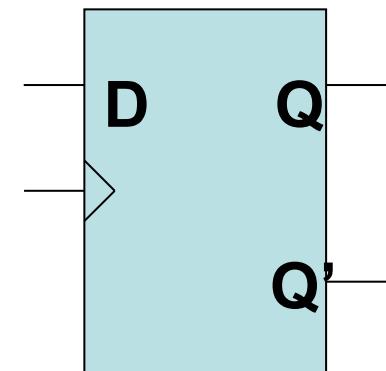

For:

- $En = 1$ (Gated Latch)
- \uparrow & \downarrow FF

D	En	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q	Q'

J-K FF

Block Diagram

Basic Operation
Truth-table

J	K	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	Q'	Q


Latch

Nil

Gated Latch

Nil

Flip-Flop

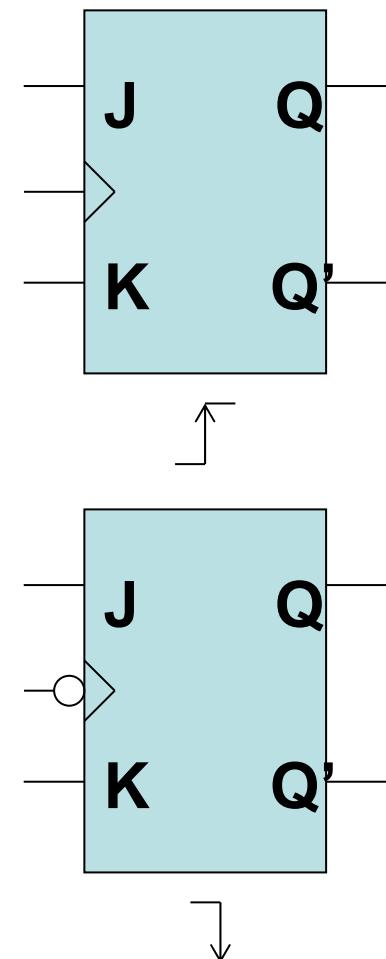

Asyn. J-K FF

Block Diagram

Basic Operation Truth-table

\overline{PRE}	\overline{CLR}	FF
0	1	SET
1	0	RESET
1	1	JK

J	K	Q	Q'
0	0	Q	Q'
0	1	0	1
1	0	1	0
1	1	Q'	Q

Latch

Gated Latch

Flip-Flop

Nil

Nil

