



UNIVERSITI
TEKNOLOGI
MALAYSIA
www.utm.my

SECR1013 DIGITAL LOGIC


**MODULE 8b:
COUNTERS (SYNC)**

FACULTY OF COMPUTING




Synchronous Counters:

Synchronous Counters

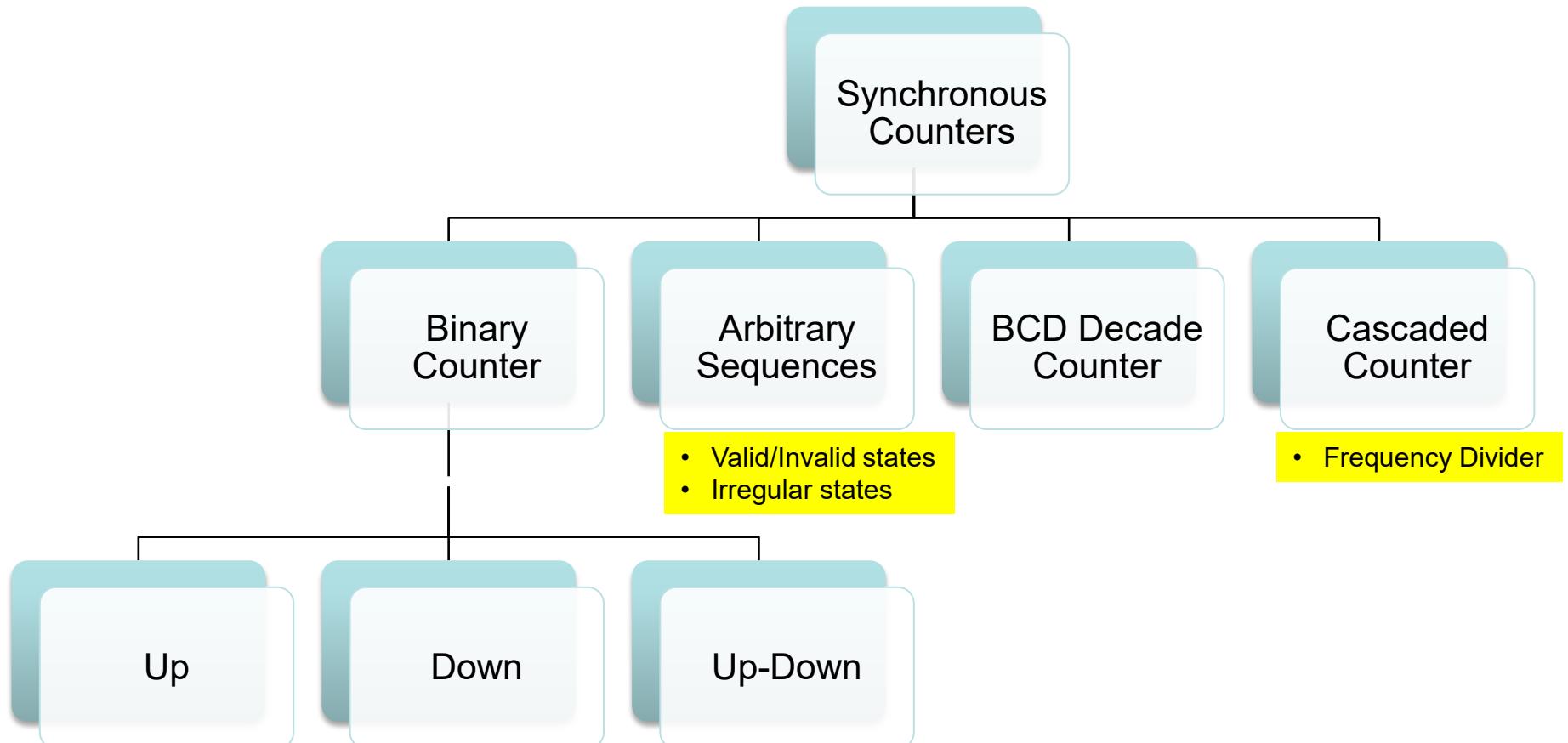

RECAP

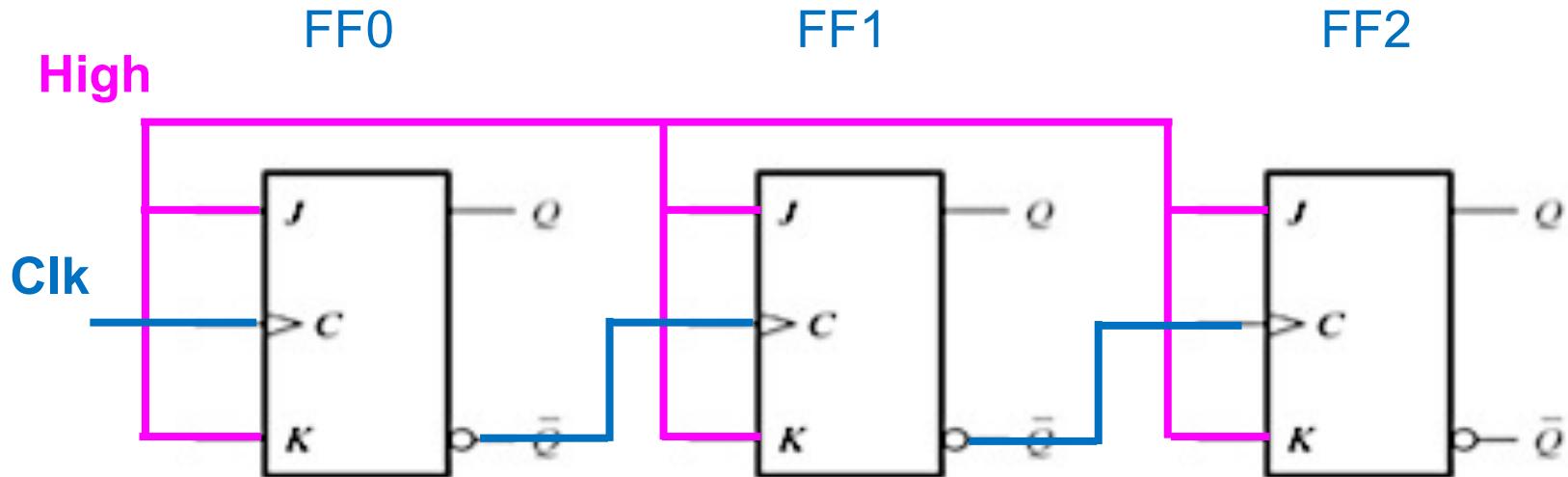Design 3-bit Count Up Asynchronous Counter using J-K Flip-flop




Async counter is
easy, straight
forward to design

How ...


Design 3-bit Count Up

Synchronous Counter using J-K Flip-flop


FF0

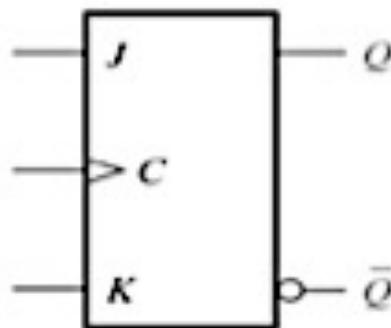

FF1

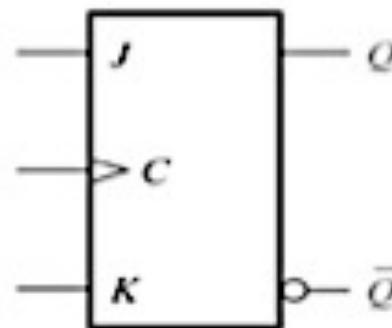

FF2

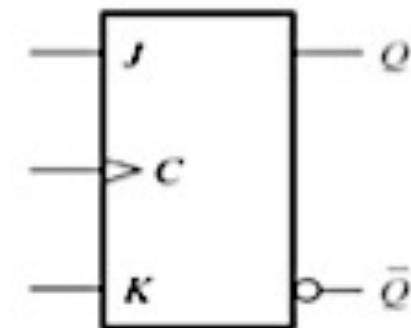

Sync counter is **not**
straight forward to
design!

Synchronous Counter Design

- **Step 1**
Describe a general sequential circuit in terms of its basic parts and its input and outputs.
- **Step 2**
Develop state diagram.
- **Step 3**
Create next state table.
- **Step 4**
Create flip-flop transition table.
- **Step 5**
Use K-maps to derive the logic equations.
- **Step 6**
Implement counter implementation.

Excitation Table

Truth table for a positive edge-triggered J-K flip-flop.

Inputs			Outputs		Comments
J	K	CLK	Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\bar{Q}_0	Q_0	Toggle

FF Excitation Table

- JK Flip-Flop

Refer to JK FF truth table

About creating Transition table

FF State		Present State	Next State
J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


NO CHANGE

RESET

SET

TOGGLE

J,K = 0/1 = X
*don't care

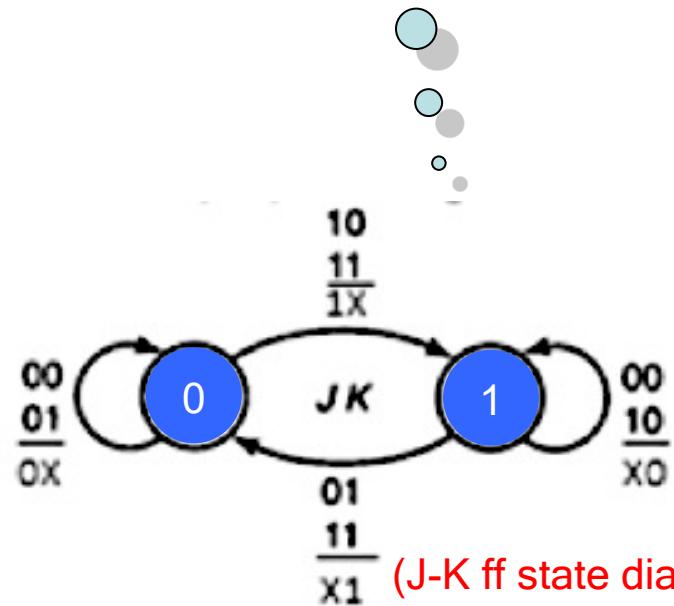

Truth table for a positive edge-triggered J-K flip-flop.

Inputs			Outputs		Comments
J	K	CLK	Q	\bar{Q}	
0	0	↑	Q_0	\bar{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\bar{Q}_0	Q_0	Toggle

FF Excitation Table

JK-ff Excitation Table

- JK Flip-Flop

Refer to JK FF truth table

FF State		Present State	Next State
J	K	Q_n	Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


NO CHANGE

RESET

SET

TOGGLE

Present State	Next State	FF State	
		J	K
Q_n	Q_{n+1}		
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

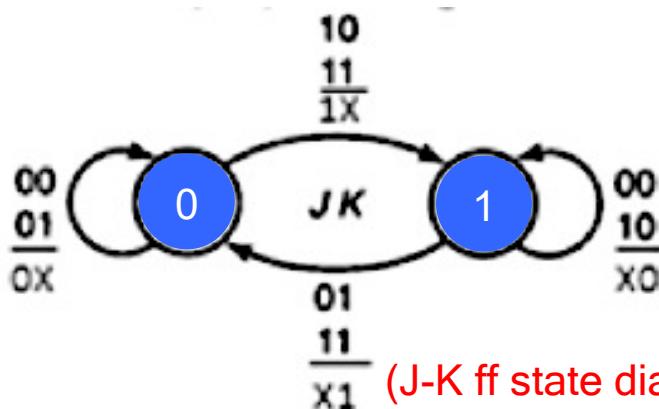

Exercise 8b.1:

Construct the excitation table for **D flip-flop**

(using its state diagram)

Solution:

D flip-flop excitation table

Present State	Next State	FF State
Q_n	Q_{n+1}	D

Exercise 8b.1:


Construct the excitation table for **D flip-flop**

(using its state diagram)

D	Present state Q_n	Next state Q_{n+1}
0	0	0
0	1	0
1	0	1
1	1	1

Truth table of D flip flop

D flip flop state diagram

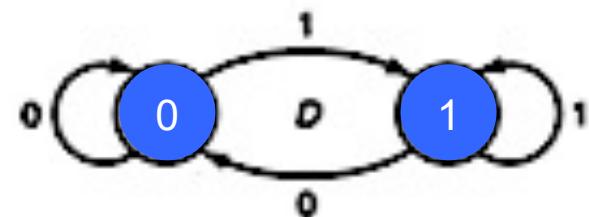

D flip-flop excitation table

Present State	Next State	FF State
Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

=

Q_{n+1}	D
0	0
1	1

Exercise 8b.2:

Construct the
excitation table
for **T flip-flop**

(using its state
diagram)

Solution:

T flip-flop excitation table

Present State	Next State	FF State
Q_n	Q_{n+1}	T


Exercise 8b.2:

Construct the excitation table for **T flip-flop**

(using its state diagram)

T	Q	Q_{n+1}	State
0	0	0	NO CHANGE
0	1	1	
1	0	1	TOGGLES
1	1	0	

Truth Table of T flip flop

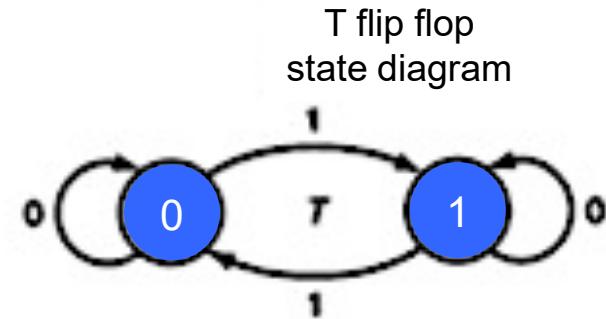

T flip-flop excitation table

Present State	Next State	FF State
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

=

Q_{n+1}	T
Q_n	0
\bar{Q}_n	1

Note:

These **excitation tables** will be used while filling in the flip-flop **transition table** in **STEP 4** of designing synchronous counter.

Summary

Excitation tables of flip-flops:

NO CHANGE / RESET

SET / TOGGLE

RESET / TOGGLE

NO CHANGE / SET

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

J-K flip-flop

Q_{n+1}	D
0	0
1	1

D flip-flop


Q_{n+1}	T
Q_n	0
\overline{Q}_n	1

T flip-flop



Synchronous Counters:


Up

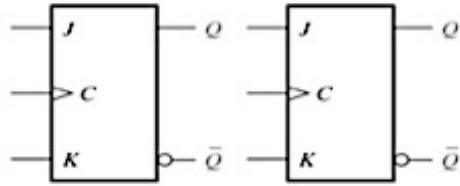

Design 2-bit Up Synchronous Counter: J-K Flip-flop

- Step 1:
To design 2-bit up synchronous counter using JK FF.

- Step 2: Draw state diagram

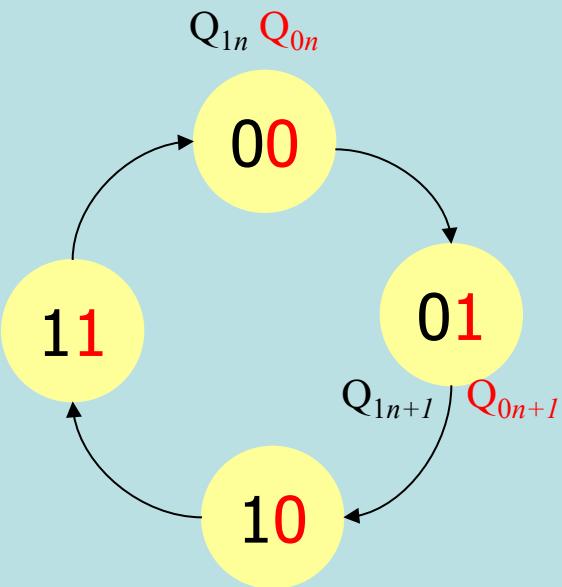

- Step 3: Create next state table

Present State		Next State	
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

Note:

While filling in the flip-flop transition table, refer to the excitation table.

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Step 4:

Construct the flip-flop transition table

FF1

FF0

Present State		Next State		JK Transition			
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}	J ₁	K ₁	J ₀	K ₀
0	0	0	1				
0	1	1	0				
1	0	1	1				
1	1	0	0				

Note:

While filling in the flip-flop transition table, refer to the excitation table.

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- Step 4:

Construct the flip-flop transition table

FF1

FF0




Present State		Next State		JK Transition			
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}	J ₁	K ₁	J ₀	K ₀
0	0	0	1	0	X	1	X
0	1	1	0	1	X	X	1
1	0	1	1	X	0	1	X
1	1	0	0	X	1	X	1

Present State		Next State		JK Transition			
Q_{1n}	Q_{0n}	Q_{1n+1}	Q_{0n+1}	J_1	K_1	J_0	K_0
0	0			0	X	1	X
0	1			1	X	X	1
1	0			X	0	1	X
1	1			X	1	X	1


- Step 5:

Use K-maps to derive the logic equations

(*for present state only*).

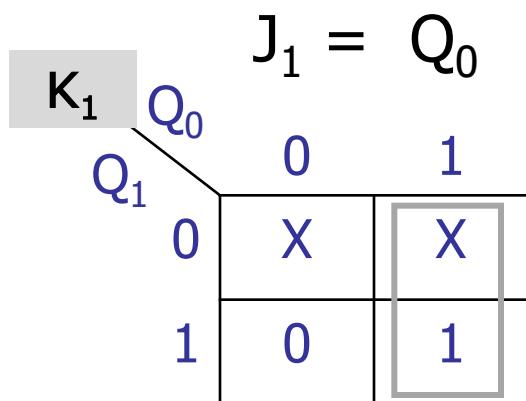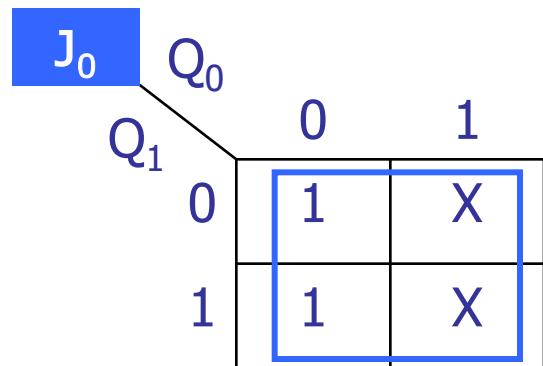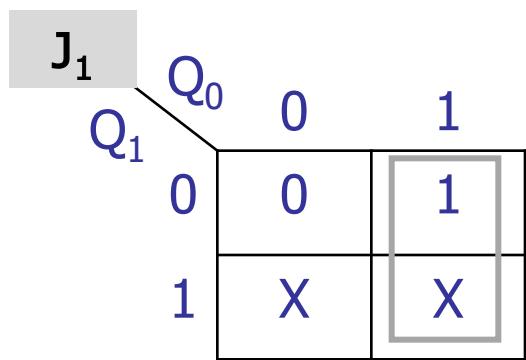

$$K_1 = Q_0$$

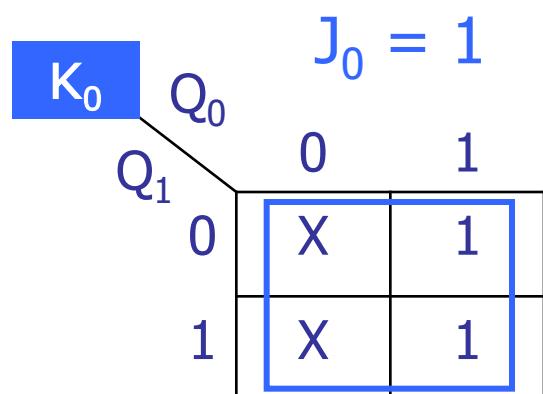

$$K_0 = \bar{Q}_0$$

- Step 6: Implement counter by drawing the logic symbol connection / counter circuit.



FF0

$$J_0 = 1$$

$$K_0 = 1$$

FF1

$$J_1 = Q_0$$
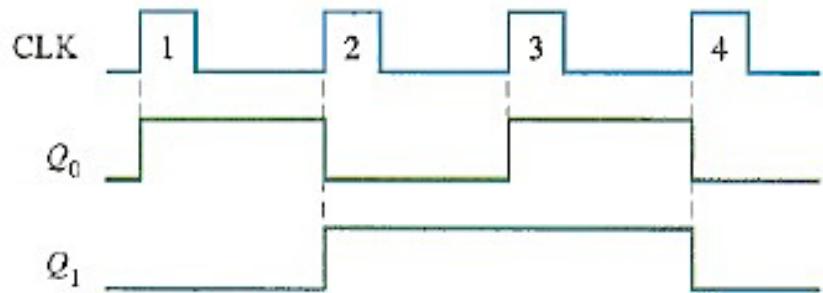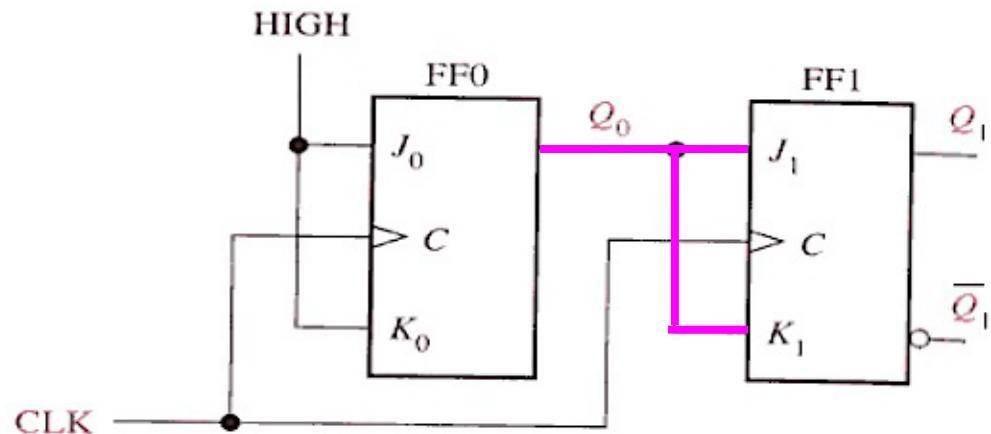
$$K_1 = Q_0$$


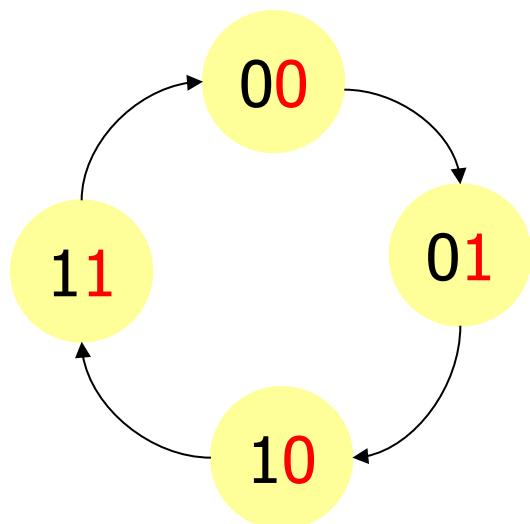
Q_1 toggle when $Q_0=1$

- Q_0 toggle at positive edge (CLK1, CLK2, CLK3, CLK4)
- Q_1 toggle when $Q_0=1$ at positive edge (CLK2, CLK4)

Exercise 8b.3: Design 2-bit up synchronous counter that using D flip-flop with positive edge triggered. Show all steps clearly.

Solution 8b.3:

- Step 2: Draw state diagram
- Step 3: Create next state table



Present State		Next State	
Q_1	Q_0	Q_{1+}	Q_{0+}
0	0	0	1
0	1	1	0
1	0	1	1
1	1	0	0

Note:

While filling in the flip-flop transition table, refer to the excitation table.

Q_{n+1}	D
0	0
1	1

- **Step 4:**

Construct flip-flop transition table using D excitation table.

Present State		Next State		D Transition	
Q_1	Q_0	Q_{1+}	Q_{0+}	D_1	D_0
0	0	0	1	0	1
0	1	1	0	1	0
1	0	1	1	1	1
1	1	0	0	0	0

Note:

While filling in the flip-flop transition table, refer to the excitation table.

Q_{n+1}	D
0	0
1	1

- **Step 5:** Use K-maps to derive the logic equations.

- Step 4:
Construct flip-flop transition table using excitation table.

Present State		Next State		D Transition	
Q_1	Q_0	Q_{1+}	Q_{0+}	D ₁	D ₀
0	0			0	1
0	1			1	0
1	0			1	1
1	1			0	0

D_0 Q_0

0	1
0	1
1	1
1	0

$$D_0 = \bar{Q}_0$$



D_1 Q_0

0	1
0	1
1	1
1	0

$$\begin{aligned} D_1 &= Q_0 \bar{Q}_1 + \bar{Q}_0 Q_1 \\ &= Q_0 \oplus Q_1 \end{aligned}$$

(XOR Page: 97, 152)

- **Step 6:** Implement counter implementation by drawing the logic symbol connection / counter circuit.

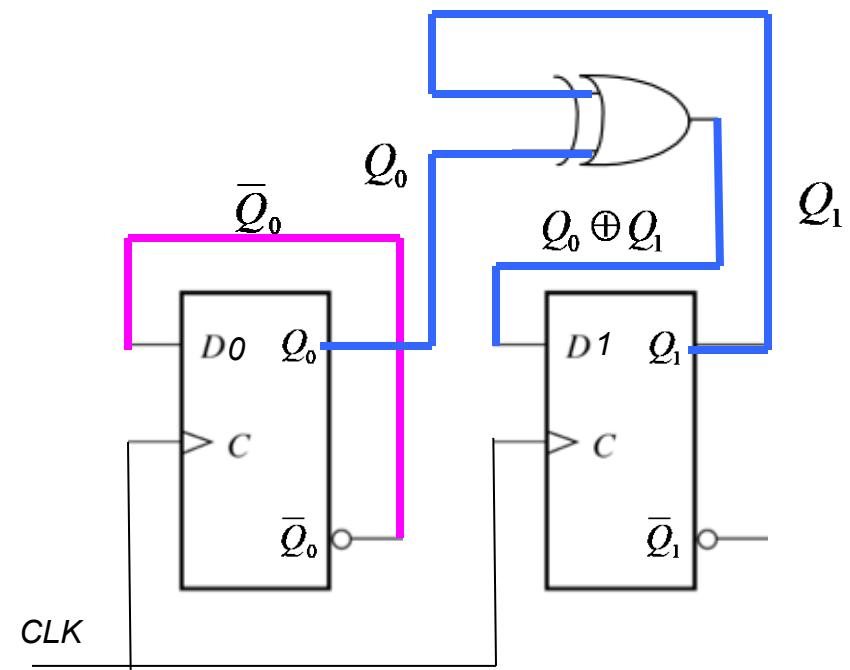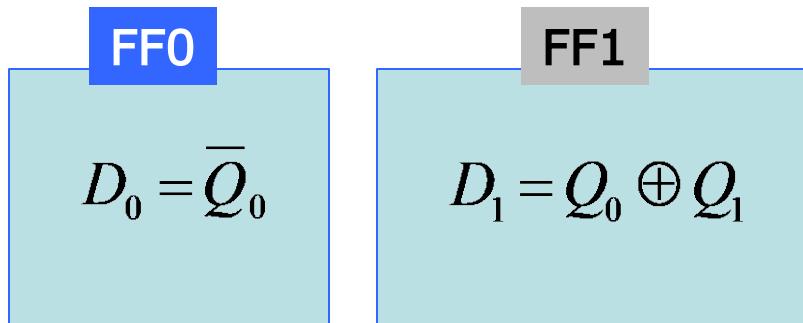




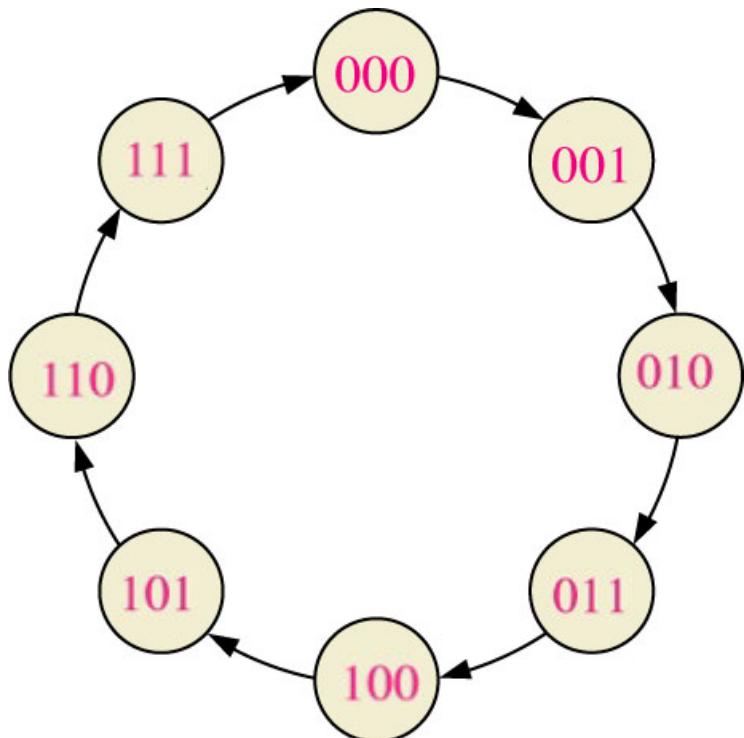Exercise 8b.4: Design 3-bit up synchronous counter that using T flip-flop with positive edge triggered. Show all steps clearly.

Design 3-bit Up Synchronous Counter: J-K Flip-flop

- Step 2: State diagram
- Step 3: Next State table



Present State			Next State		
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Note:

While filling in
the flip-flop
transition table,
refer to the
excitation table.

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- Step 4:

FF transition table

FF2

FF1


FF0

Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	0	1	1	0	X	X	0	1	X
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	0	0	0	X	1	X	1	X	1


- Step 5:

Create K-map to determine the Boolean expression


Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0				0	X	0	X	1	X
0	0	1				0	X	1	X	X	1
0	1	0				0	X	X	0	1	X
0	1	1				1	X	X	1	X	1
1	0	0				X	0	0	X	1	X
1	0	1				X	0	1	X	X	1
1	1	0				X	0	X	0	1	X
1	1	1				X	1	X	1	X	1

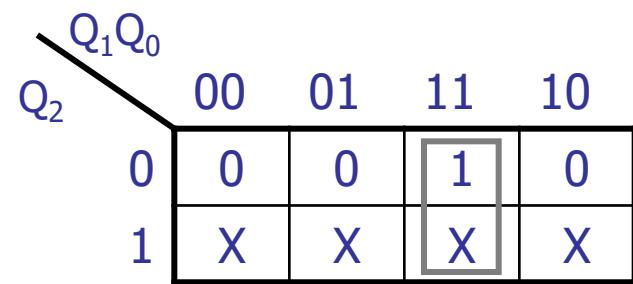


$$J_2 = Q_1Q_0$$

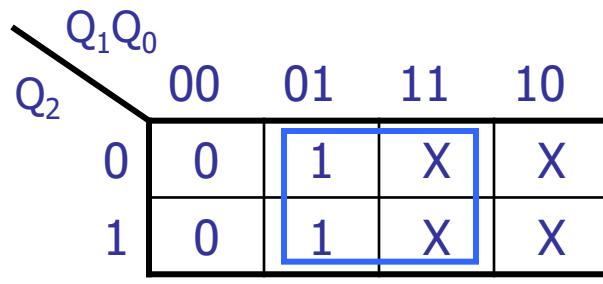


$$J_1 =$$

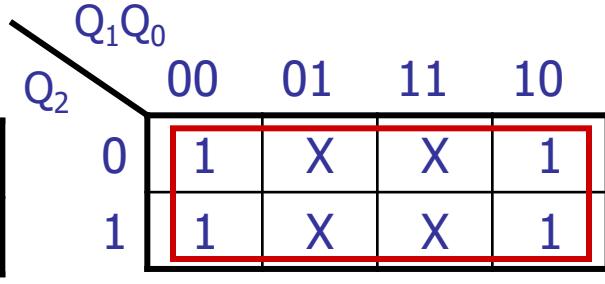


$$J_0 =$$

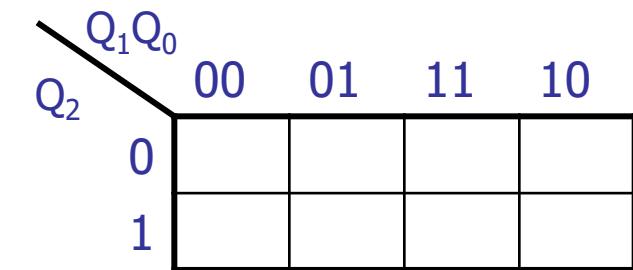

$$K_2 =$$

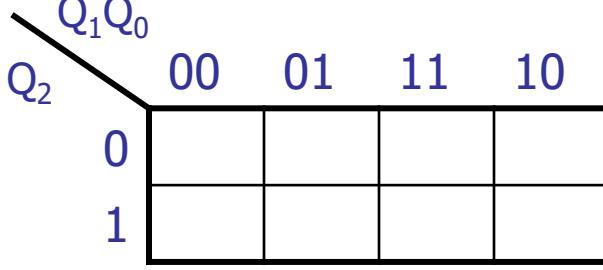

$$K_1 =$$

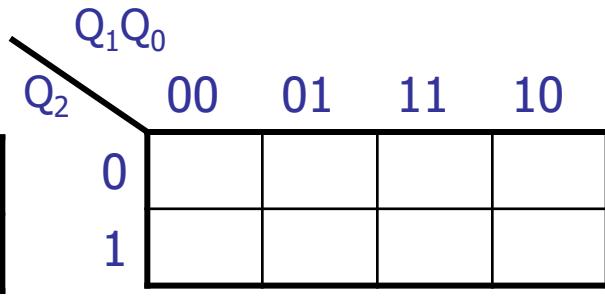


$$K_0 =$$


- Step 5:

Create K-map to determine the Boolean expression


Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0				0	X	0	X	1	X
0	0	1				0	X	1	X	X	1
0	1	0				0	X	X	0	1	X
0	1	1				1	X	X	1	X	1
1	0	0				X	0	0	X	1	X
1	0	1				X	0	1	X	X	1
1	1	0				X	0	X	0	1	X
1	1	1				X	1	X	1	X	1

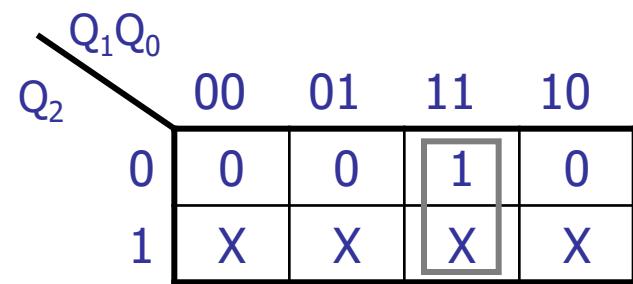


$$J_2 = Q_1 Q_0$$

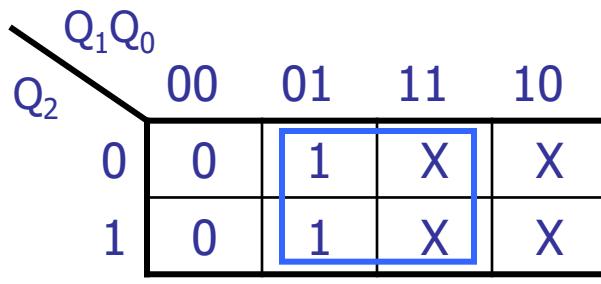


$$J_1 = Q_0$$

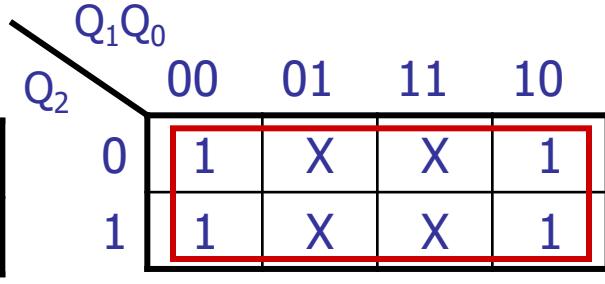


$$J_0 = 1$$

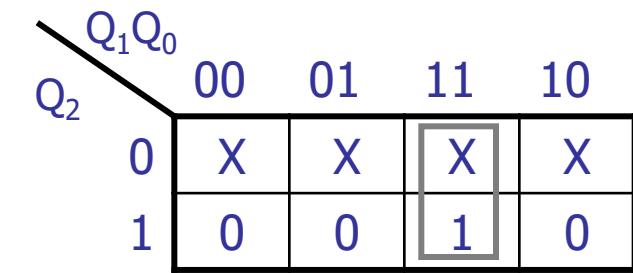

$$K_2 = Q_1 Q_0$$



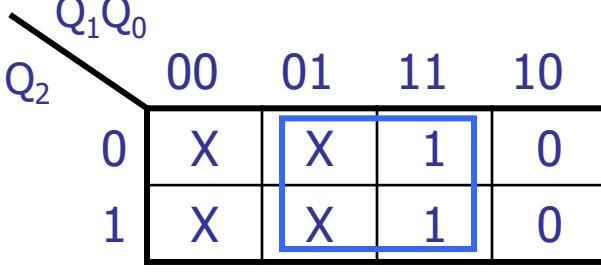


$$K_1 = Q_0$$

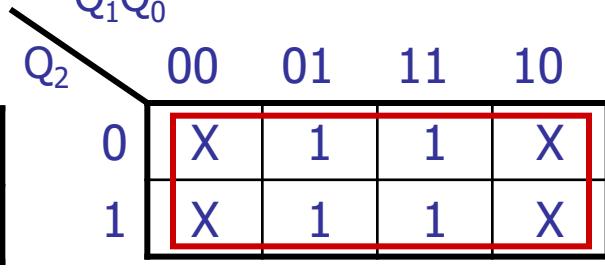

$$K_0 = 1$$

- Step 6:
The implementation of 3-bit synchronous counter

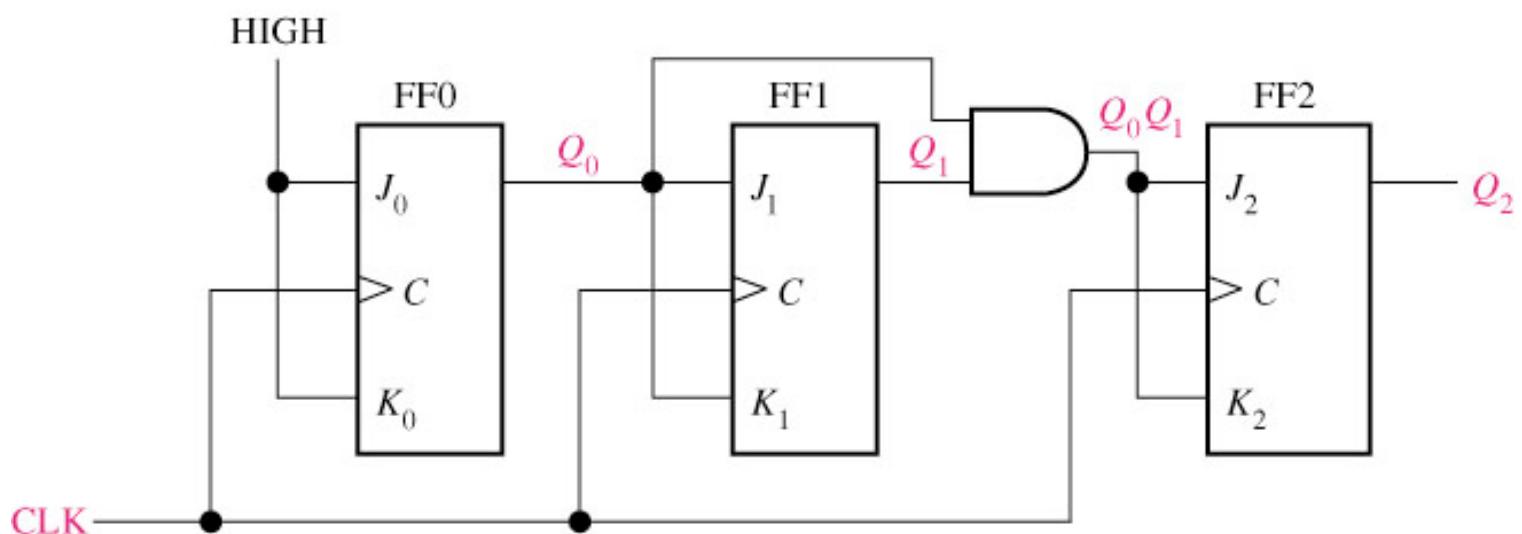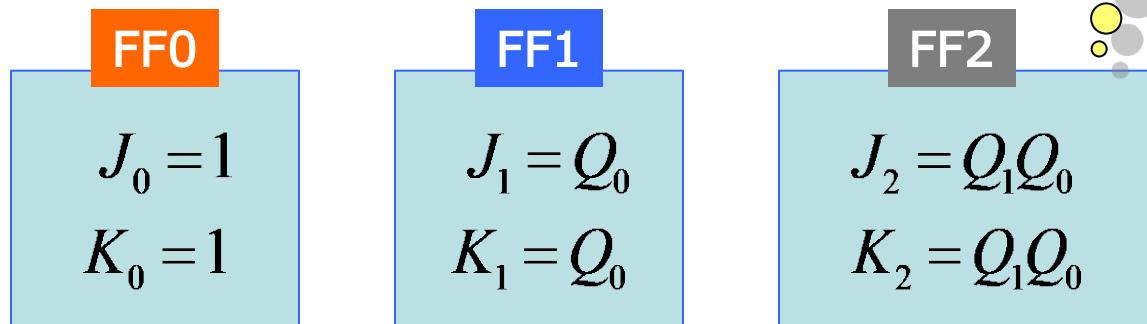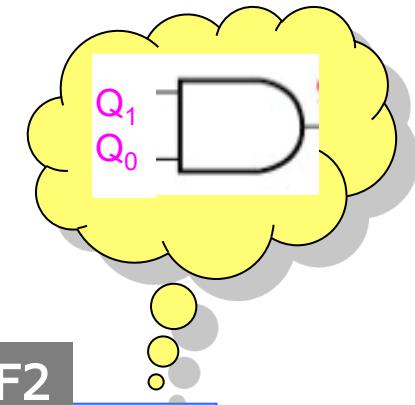



Exercise 8b.5: Design 3-bit up synchronous counter that using D flip-flop with positive edge triggered. Show all steps clearly.



Exercise 8b.6: Design 4-bit up synchronous counter that using the following flip-flops with negative edge triggered.
Show all steps clearly.

- (a) D flip-flop.
- (b) T flip-flop.




Synchronous Counters:

Down

2-bit Down Synchronous Counter: D Flip-flop

- **Step 1:**
To design 2-bit down synchronous counter using D flip-flop.
There is no input or output element in this design.

- **Step 2:** Draw state diagram

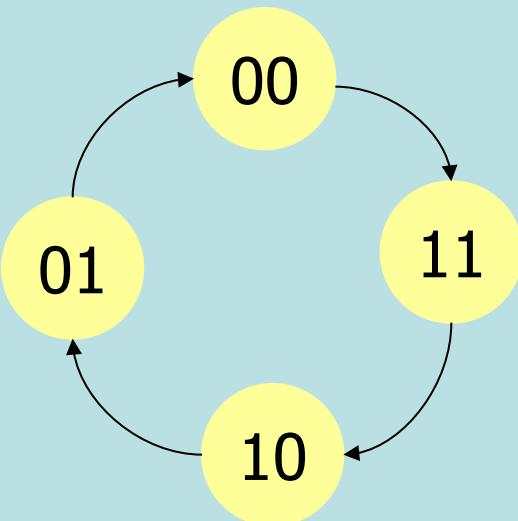

- **Step 3:** Create next state table

Present State		Next State	
Q_1	Q_0	Q_{1+}	Q_{0+}
0	0	1	1
0	1	0	0
1	0	0	1
1	1	1	0

Q_{n+1}	D
0	0
1	1

- Step 4:

Draw flip-flop transition table. For D flip-flop, D input **is the same** as the next state values.

Present State		Next State		D Transition	
Q_1	Q_0	Q_{1+}	Q_{0+}	D_1	D_0
0	0	1	1	1	1
0	1	0	0	0	0
1	0	0	1	0	1
1	1	1	0	1	0

- Step 4:

Draw flip-flop transition table. For D flip-flop, D input is the same as the next state values.

Present State		Next State		D Transition	
Q_1	Q_0	Q_{1+}	Q_{0+}	D_1	D_0
0	0			1	1
0	1			0	0
1	0			0	1
1	1			1	0

Q_{n+1}	D
0	0
1	1

- Step 5: K-Map.

Q_1	0	1
0	1	0
1	1	0

$$D_0 = \overline{Q}_0$$

Q_1	0	1
0	1	0
1	0	1

$$D_1 = \overline{Q}_1 \overline{Q}_0 + Q_1 Q_0$$

$$D_1 = Q_0 \odot Q_1$$



Exercise 8b.7: Draw the circuit for of 2-bit down synchronous counter using D flip-flop with $D_1 = Q_0 \odot Q_1$ and $D_0 = \overline{Q}_0$



Exercise 8b.8: Design 3-bit down synchronous counter that using the following flip-flops with negative edge triggered. Show all steps clearly.

- (a) J-K flip-flop.
- (b) D flip-flop.
- (c) T flip-flop.



- Exercise 8b.9:** Design 4-bit down synchronous counter that using the following flip-flops with positive edge triggered. Show all steps clearly.
- (a) D flip-flop.
 - (b) T flip-flop.



Synchronous Counters:

Up-Down


2-bit UP/DOWN Synchronous Counter: D Flip-flop

- Step 1:

To design 2-bit up-down synchronous counter using D flip-flop based on input X. When $X=0 \rightarrow$ Count UP and $X=1 \rightarrow$ Count DOWN

- Step 2:

Given the state diagram.

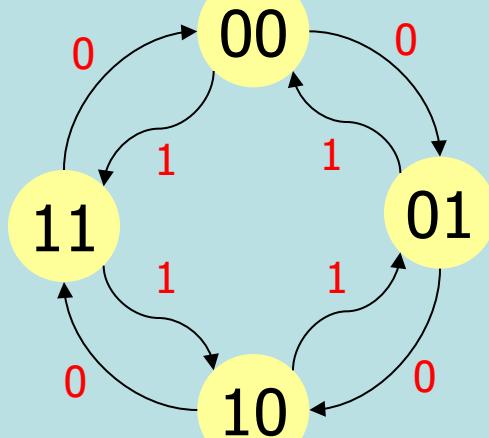

- Step 3: Create next state table


Input, X	Present State		Next State	
	$Q1_n$	$Q0_n$	$Q1_{n+1}$	$Q0_{n+1}$
Count up	0	0	0	1
	0	0	1	0
	0	1	0	1
	0	1	1	0
Count down	1	0	0	1
	1	0	1	0
	1	1	0	1
	1	1	1	0
	1	1	0	0

- Step 4:
D flip-flop transition table.

Input, <i>X</i>	Present State		Next State		D FF	
	Q_1_n	Q_0_n	Q_1_{n+1}	Q_0_{n+1}	D_1	D_0
0	0	0	0	1	0	1
0	0	1	1	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	1	1	1
1	0	1	0	0	0	0
1	1	0	0	1	0	1
1	1	1	1	0	1	0

- Step 4:
D flip-flop transition table.

Input, X	Present State		Next State		D FF	
	Q_1_n	Q_0_n	Q_1_{n+1}	Q_0_{n+1}	D_1	D_0
0	0	0			0	1
0	0	1			1	0
0	1	0			1	1
0	1	1			0	0
1	0	0			1	1
1	0	1			0	0
1	1	0			0	1
1	1	1			1	0

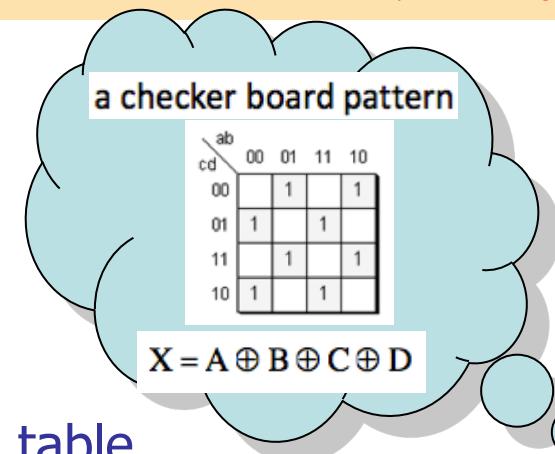

- Step 5:
Define logic equation.
(create k-maps)

$Q_1 Q_0$	00	01	11	10
X	0	1	0	1
	1	0	1	0

$$D_1 = X \oplus Q_1 \oplus Q_0$$

$Q_1 Q_0$	00	01	11	10
X	1	0	0	1
	1	0	0	1

$$D_0 = \bar{Q}_0$$



Exercise 8b.10: Draw the circuit for of 2-bit up-down synchronous counter using D flip-flop with:

$$D_1 = X \oplus Q_1 \oplus Q_0$$

$$D_0 = \overline{Q}_0$$




Synchronous Counters:


Arbitrary Sequences || BCD Decade Counter ||
Cascaded Counter

Counter for Arbitrary Sequences

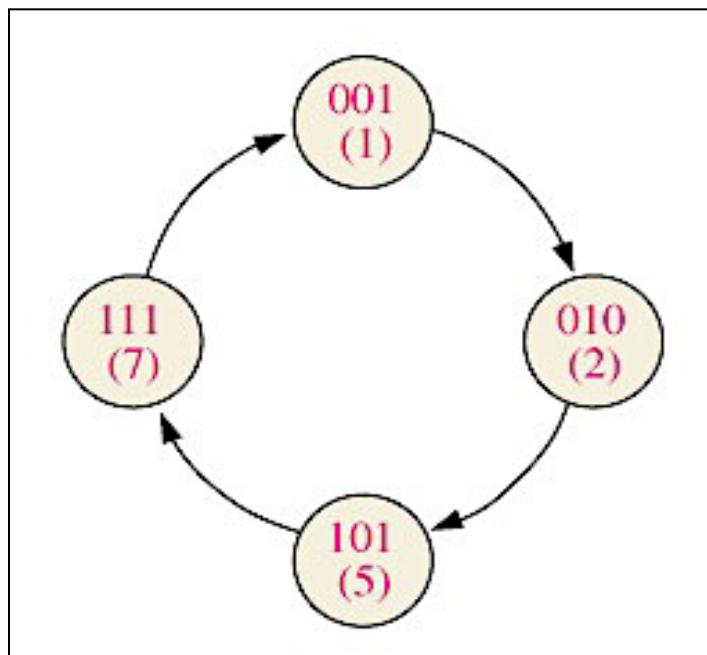- Design the counter base on the given state diagram using T flip-flop.



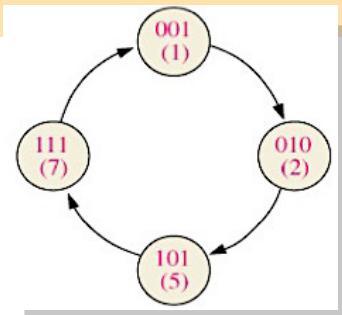- The counter is 3-bit counter
- The total number state = $2^3 = 8$
- Only 4 state (1, 2, 5, 7)
→ **Valid State**
- Other states (0, 3, 4, 6)
→ **Invalid State**
(never occur /**don't care**)




- State table and T flip-flop transition table.

Present State			Next State			T FF		
Q_{2n}	Q_{1n}	Q_{0n}	Q_{2n+1}	Q_{1n+1}	Q_{0n+1}	T_2	T_1	T_0
0	0	0	X	X	X	X	X	X
0	0	1						
0	1	0						
0	1	1	X	X	X	X	X	X
1	0	0	X	X	X	X	X	X
1	0	1						
1	1	0	X	X	X	X	X	X
1	1	1						

**Fill in the next state and T FF transition column

Q_{n+1}	T
Q_n	0
$\overline{Q_n}$	1

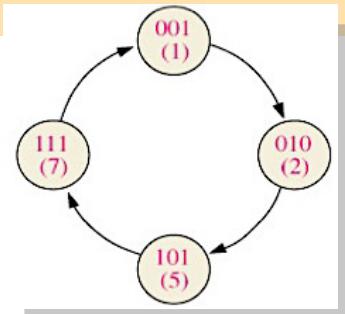

- State table and T flip-flop transition table.

FF2

FF1


FF0

Present State			Next State			T FF		
Q_{2n}	Q_{1n}	Q_{0n}	Q_{2n+1}	Q_{1n+1}	Q_{0n+1}	T_2	T_1	T_0
0	0	0	X	X	X	X	X	X
0	0	1	0	1	0	0	1	1
0	1	0	1	0	1	1	1	1
0	1	1	X	X	X	X	X	X
1	0	0	X	X	X	X	X	X
1	0	1	1	1	1	0	1	0
1	1	0	X	X	X	X	X	X
1	1	1	0	0	1	1	1	0


**Fill in the next state and T FF transition column

Present State			Next State			T FF		
Q_{2n}	Q_{1n}	Q_{0n}	Q_{2n+1}	Q_{1n+1}	Q_{0n+1}	T_2	T_1	T_0
0	0	0				X	X	X
0	0	1				0	1	1
0	1	0				1	1	1
0	1	1				X	X	X
1	0	0				X	X	X
1	0	1				0	1	0
1	1	0				X	X	X
1	1	1				1	1	0

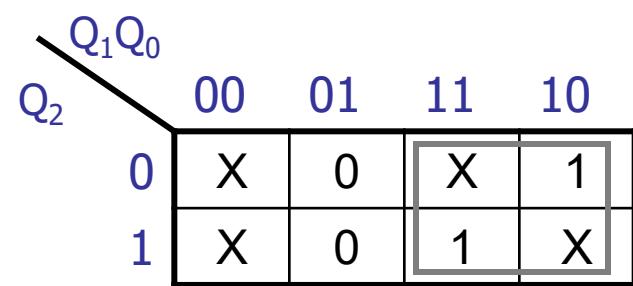
- Step 5: Create K-map to determine the Boolean expression



$$T_2 = Q_1$$

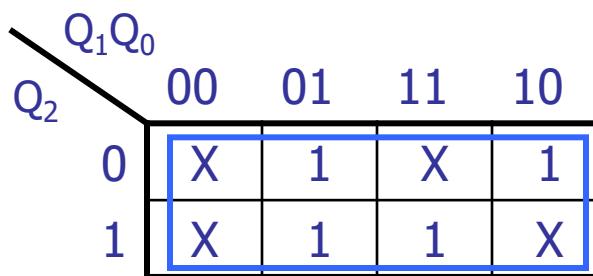


$$T_1 = 1$$

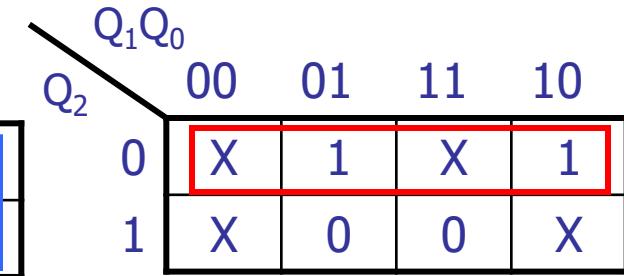

$$T_0 = \overline{Q}_2$$

**Fill in the K-maps

- Step 6: Draw the circuit design.

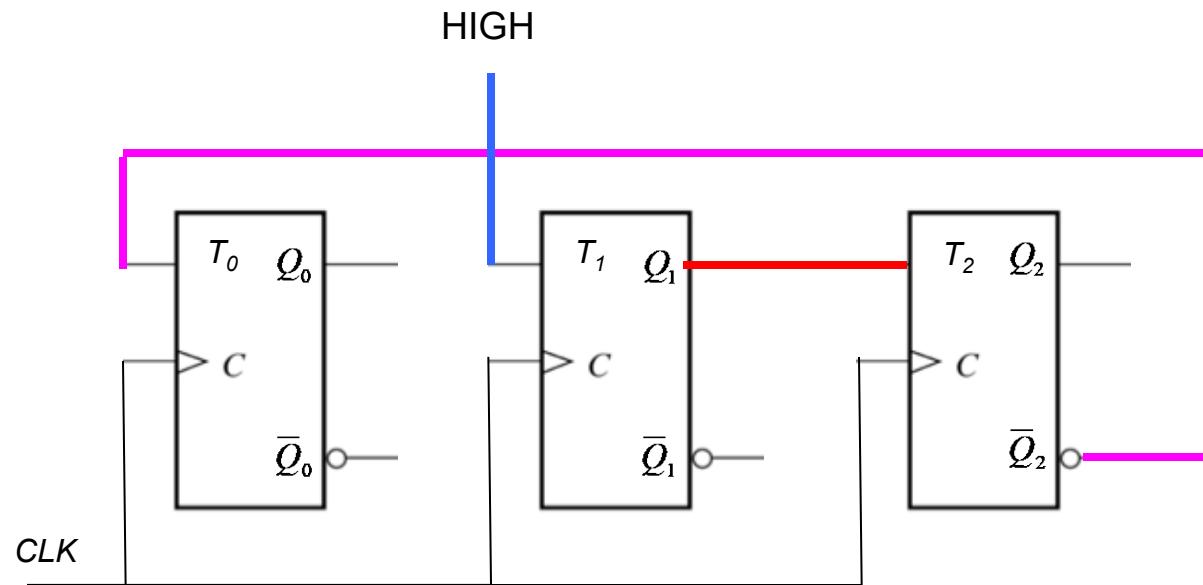



$$T_0 = \bar{Q}_2$$

$$T_1 = 1$$

$$T_2 = Q_1$$

Exercise 8b.14: Design a counter with the **irregular** binary count sequence as shown in the state diagram below using **J-K flip-flop**.

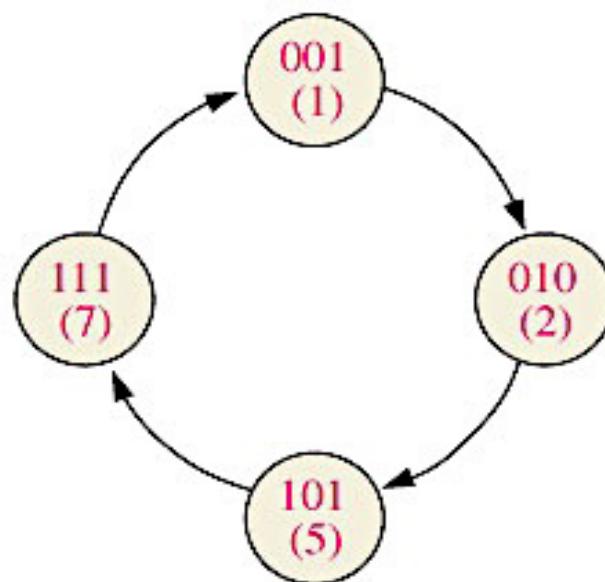

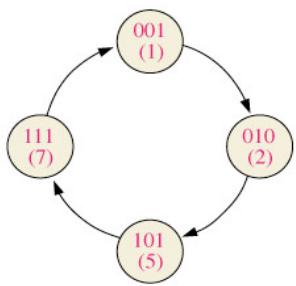


Solution 8b.14:

- Step 3 and 4: Next state table and FF transition table.

**Fill in the next state and T FF transition column

Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0	X	X	X						
0	0	1	0	1	0						
0	1	0	1	0	1						
0	1	1	X	X	X						
1	0	0	X	X	X						
1	0	1	1	1	1						
1	1	0	X	X	X						
1	1	1	0	0	1						

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

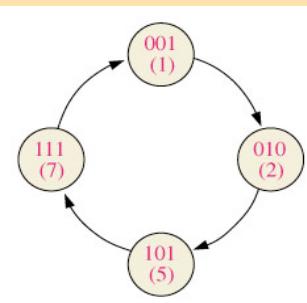

- Step 3 and 4: Next state table and FF transition table.

Present State			Next State			JK Transition Table					
Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_2	K_2	J_1	K_1	J_0	K_0
0	0	0	X	X	X	X	X	X	X	X	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	1	1	X	X	1	1	X
0	1	1	X	X	X	X	X	X	X	X	X
1	0	0	X	X	X	X	X	X	X	X	X
1	0	1	1	1	1	X	0	1	X	X	0
1	1	0	X	X	X	X	X	X	X	X	X
1	1	1	0	0	1	X	1	X	1	X	0

- Step 5:

- Create K-map to determine the Boolean expression

		Q1Q0				
		00	01	11	10	Q2
Q2	0	X	0	X	1	
	1	X	X	X	X	

$$J_2 = \overline{Q}_0$$

		Q1Q0				
		00	01	11	10	Q2
Q2	0	X	1	X	X	
	1	X	1	X	X	

$$J_1 = 1$$

		Q1Q0				
		00	01	11	10	Q2
Q2	0	X	X	X	1	
	1	X	X	X	X	

$$J_0 = 1$$

		Q1Q0				
		00	01	11	10	Q2
Q2	0	X	X	X	X	
	1	X	0	1	X	

$$K_2 = Q_1$$

		Q1Q0				
		00	01	11	10	Q2
Q2	0	X	X	X	1	
	1	X	X	1	X	

$$K_1 = 1$$

		Q1Q0				
		00	01	11	10	Q2
Q2	0	X	1	X	X	
	1	X	0	0	X	

$$K_0 = \overline{Q}_2$$

Step 6: Draw the circuit design

$$J_0 = 1$$


$$J_1 = 1$$

$$J_2 = \bar{Q}_0$$


$$K_0 = \bar{Q}_2$$

$$K_1 = 1$$

$$K_2 = Q_1$$

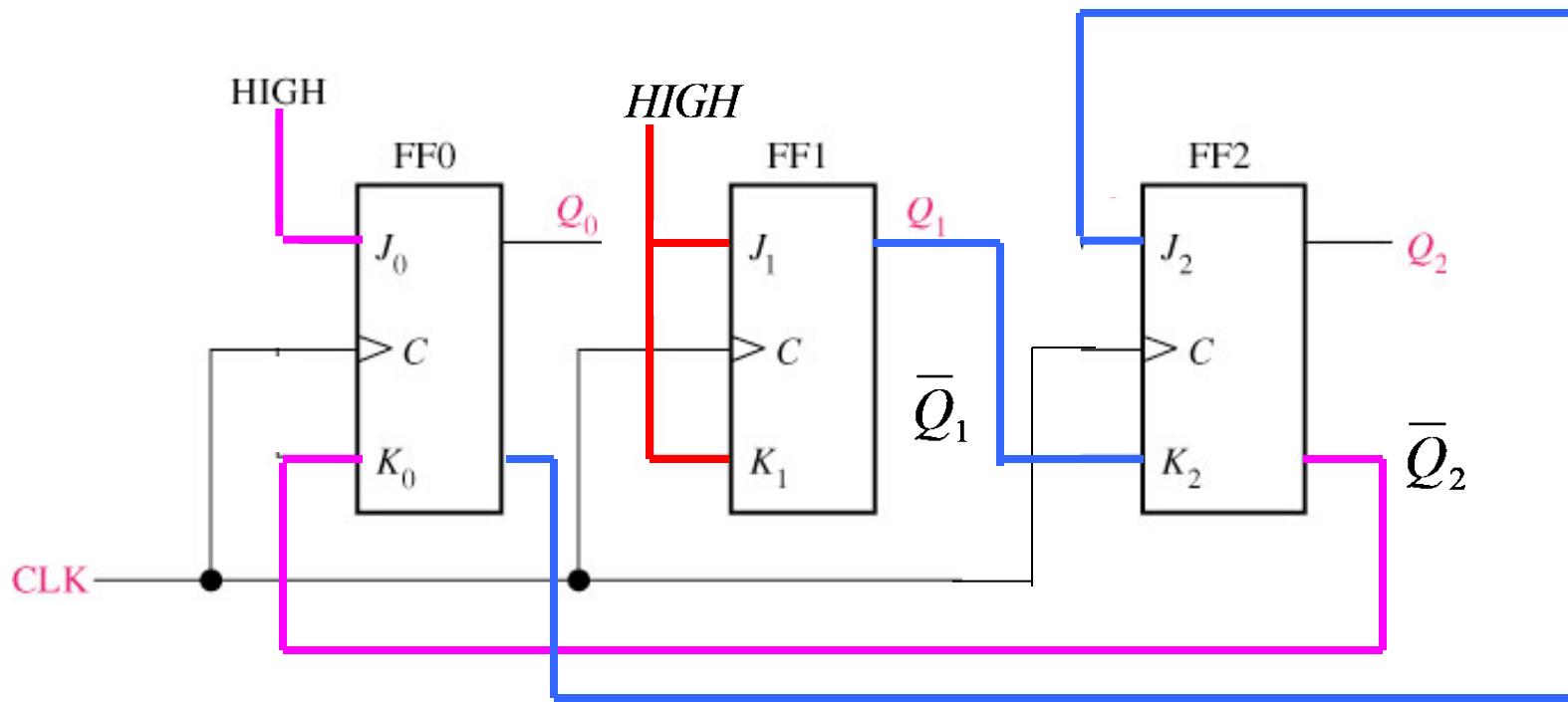

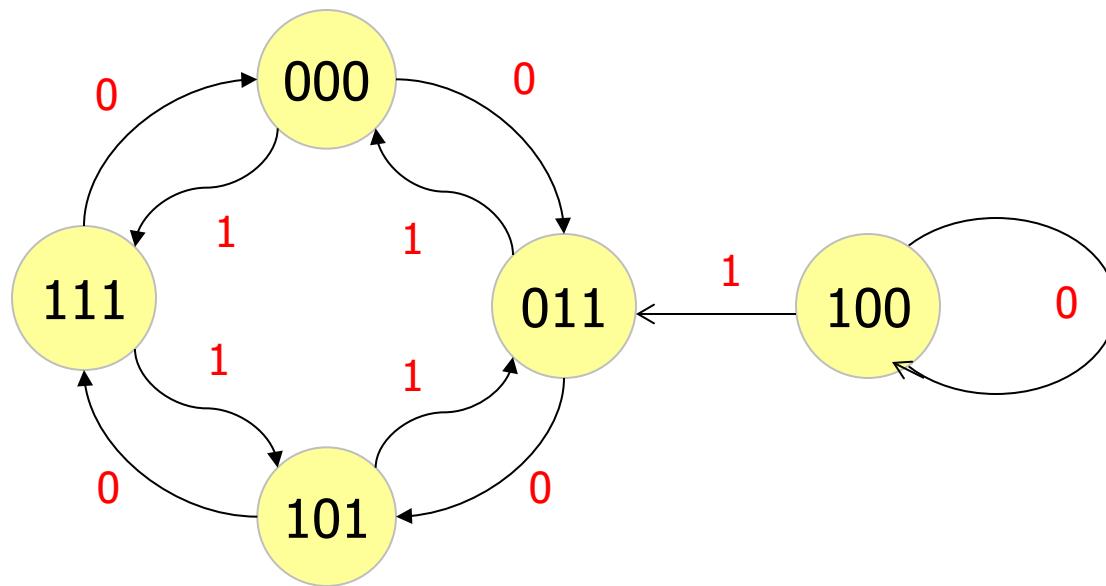
Exercise 8b.16: Design a synchronous counter with the binary count sequence as shown in the state diagram below using J-K flip-flop.



Solutions:


Input, X = 0

Input	Present State			Next State		
X	Q ₂	Q ₁	Q ₀	Q ₂₊	Q ₁₊	Q ₀₊
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			

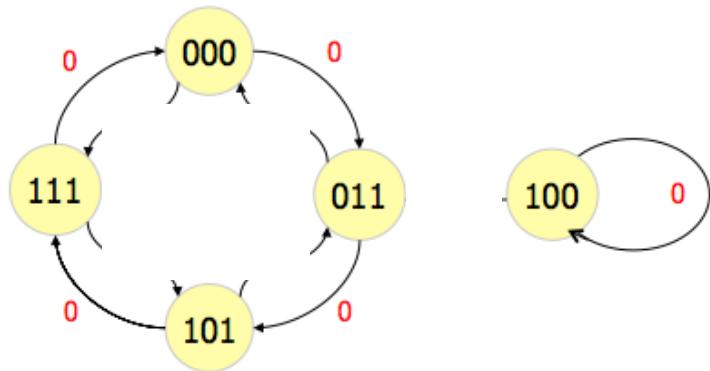

Solutions:


Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

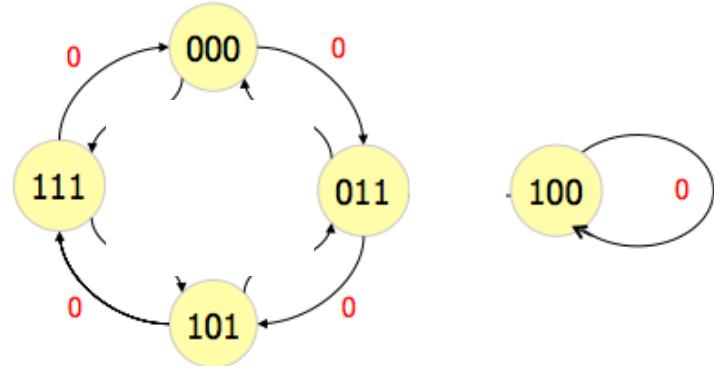

Input, X = 0

Input	Present State			Next State			
	X	Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}
0	0	0	0	0	1	1	
0	0	0	1	X	X	X	
0	0	1	0	X	X	X	
0	0	1	1	1	0	1	
0	1	0	0	1	0	0	
0	1	0	1	1	1	1	
0	1	1	0	X	X	X	
0	1	1	1	0	0	0	


JK Transition Table					
J_2	K_2	J_1	K_1	J_0	K_0
0	X	1	X	1	X
X	X	X	X	X	X
X	X	X	X	X	X
1	X	X	1	X	0
X	0	0	X	0	X
X	0	1	X	X	0
X	X	X	X	X	X
X	1	X	1	X	1

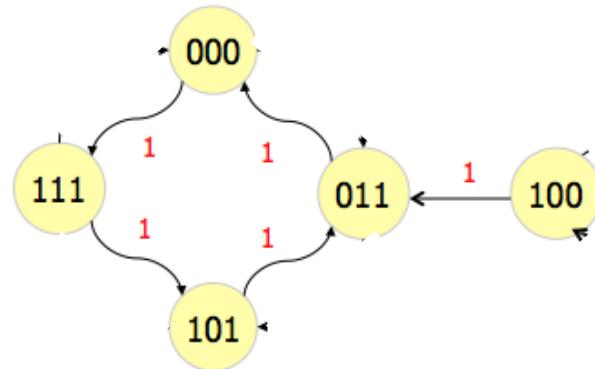

Input, X = 1

Input	Present State			Next State		
X	Q ₂	Q ₁	Q ₀	Q ₂₊	Q ₁₊	Q ₀₊
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

Present State	Next State	FF State	
Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

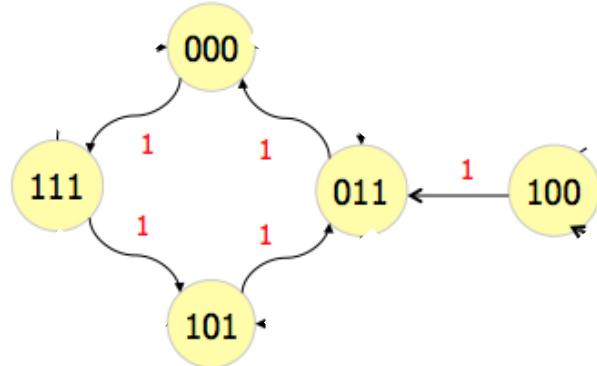

Input, X = 1

Input	Present State			Next State			
	X	Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}
1	0	0	0	0	1	1	1
1	0	0	1	1	X	X	X
1	0	1	0	0	X	X	X
1	0	1	1	1	0	0	0
1	1	0	0	0	0	1	1
1	1	0	1	0	0	1	1
1	1	1	0	1	X	X	X
1	1	1	1	1	1	0	1

JK Transition Table					
J_2	K_2	J_1	K_1	J_0	K_0
1	X	1	X	1	X
X	X	X	X	X	X
X	X	X	X	X	X
0	X	X	0	X	0
X	1	1	X	1	X
X	1	1	X	X	0
X	X	X	X	X	X
X	0	X	1	X	0

Input, $X = 0$

Input	Present State		
X	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1

Use K-maps to derive the logic equations for each J and K.

JK Transition Table					
J_2	K_2	J_1	K_1	J_0	K_0
0	X	1	X	1	X
X	X	X	X	X	X
X	X	X	X	X	X
1	X	X	1	X	0
X	0	0	X	0	X
X	0	1	X	X	0
X	X	X	X	X	X
X	1	X	1	X	1

Input, $X = 1$

Input	Present State		
X	Q_2	Q_1	Q_0
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Use K-maps to derive the logic equations for each J and K.

JK Transition Table					
J_2	K_2	J_1	K_1	J_0	K_0
1	X	1	X	1	X
X	X	X	X	X	X
X	X	X	X	X	X
0	X	X	0	X	0
X	1	1	X	1	X
X	1	1	X	X	0
X	X	X	X	X	X
X	0	X	1	X	0

K-maps:

**Fill in the K-maps

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	0	X	1	X
00	X	X	X	X	X
01	X	X	X	X	X
11	1	X	0	X	X
10	1	X	0	X	X

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	1	X	X	X
01	0	1	X	X	X
11	1	1	X	X	X
10	1	X	X	X	X

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	1	X	X	X
01	0	X	X	X	X
11	1	X	X	X	X
10	1	X	X	X	X

$$J_2 =$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	X	X
01	0	0	1	X	X
11	1	1	0	X	X
10	X	X	X	X	X

$$K_2 =$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	1	X
01	X	X	1	X	X
11	X	X	1	X	X
10	X	X	0	X	X

$$K_1 =$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	0	X
01	X	0	1	X	X
11	X	0	0	X	X
10	X	X	0	X	X

$$K_0 =$$

K-maps:

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	0	X	1	X
	01	X	X	X	X
	11	X	X	X	X
	10	1	X	0	X

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	1	X	X	X
	01	0	1	X	X
	11	1	1	X	X
	10	1	X	X	X

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	1	X	X	X
	01	0	X	X	X
	11	1	X	X	X
	10	1	X	X	X

$$J_2 =$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	X	X
	01	0	0	1	X
	11	1	1	0	X
	10	X	X	X	X

$$K_2 =$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	1	X
	01	X	X	1	X
	11	X	X	1	X
	10	X	X	0	X

$$K_1 =$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	0	X
	01	X	0	1	X
	11	X	0	0	X
	10	X	X	0	X

$$K_0 =$$

K-maps:

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	0	X	1	X
	01	X	X	X	X
	11	X	X	X	X
	10	1	X	0	X

$$J_2 = X \bar{Q}_1 + \bar{X} Q_1$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	X	X
	01	0	0	1	X
	11	1	1	0	X
	10	X	X	X	X

$$K_2 = X \bar{Q}_1 + \bar{X} Q_1$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	1	X	X	X
	01	0	1	X	X
	11	1	1	X	X
	10	1	X	X	X

$$J_1 = X + \bar{Q}_2 + Q_0$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	1	X
	01	X	X	1	X
	11	X	X	1	X
	10	X	X	0	X

$$K_1 = \bar{X} + Q_2$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	1	X	X	X
	01	0	X	X	X
	11	1	X	X	X
	10	1	X	X	X

$$J_0 = X + \bar{Q}_2$$

	$Q_1 Q_0$	00	01	11	10
$X Q_2$	00	X	X	0	X
	01	X	0	1	X
	11	X	0	0	X
	10	X	X	0	X

$$K_0 = \bar{X} Q_2 Q_1$$

Draw the counter design.

FF0

$$J_0 = X + \bar{Q}_2$$
$$K_0 = \bar{X}Q_2Q_1$$

FF1

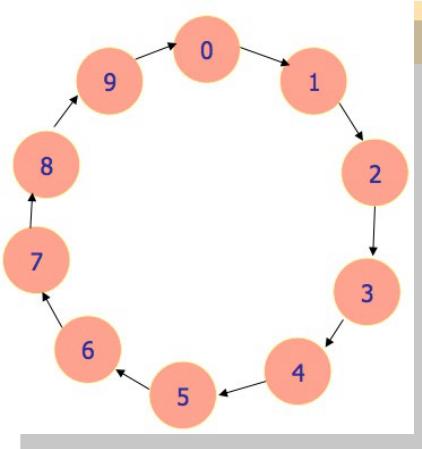
$$J_1 = X + \bar{Q}_2 + Q_0$$
$$K_1 = \bar{X} + Q_2$$

FF2

$$J_2 = X\bar{Q}_1 + \bar{X}Q_1$$
$$K_2 = X\bar{Q}_1 + \bar{X}Q_1$$


$J_2 = K_2 = X \oplus Q_1$

(XOR)

Synchronous BCD Decade Counter

- Synchronous decade counter counts from 0 to 9 and then recycles to 0 again.
- 4 flip-flops are required, and the unused states (**10 to 15**) are taken as **don't care** terms.

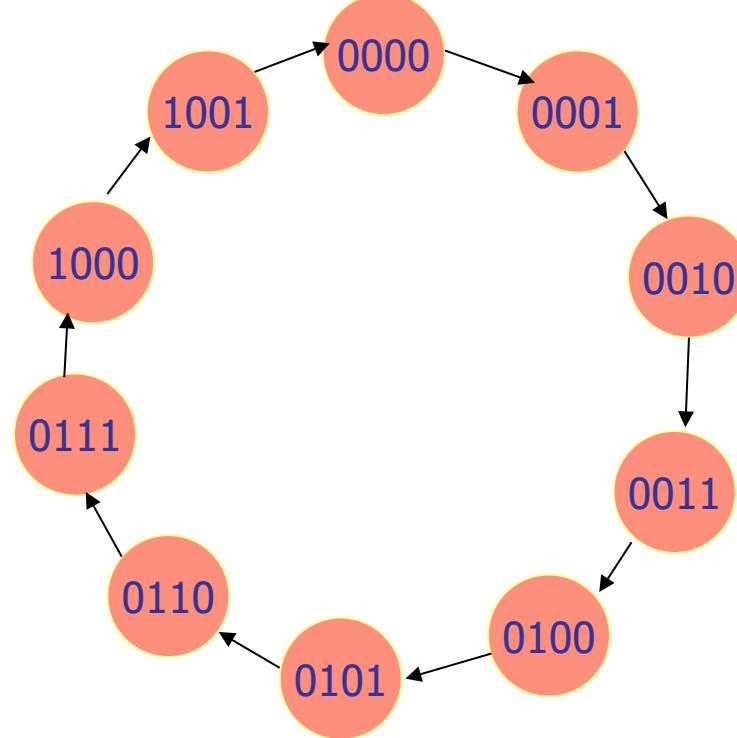

Exercise 8b.17: Draw the design a synchronous BCD decade counter using the T flip-flop.


**Fill in the
T₀ column

Present State				Next State				T FF Transition			
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃₊	Q ₂₊	Q ₁₊	Q ₀₊	T ₃	T ₂	T ₁	T ₀
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1
1	0	1	0	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X


**Fill in the K-maps

Self-Test:

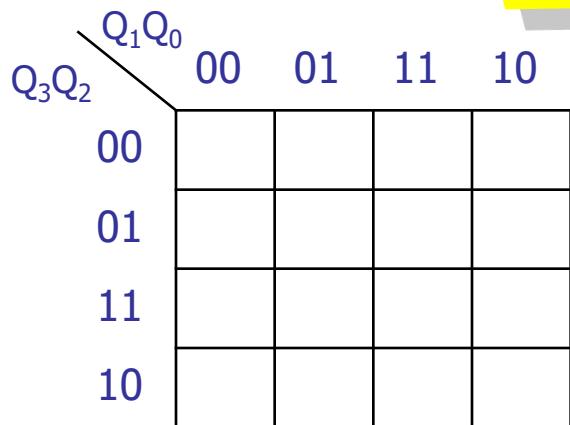
Fill in the K-map
to simplify the
equations.




$$T_3 =$$

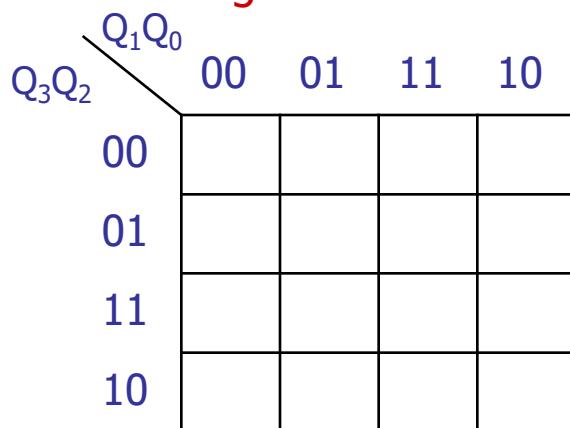

$$T_1 =$$

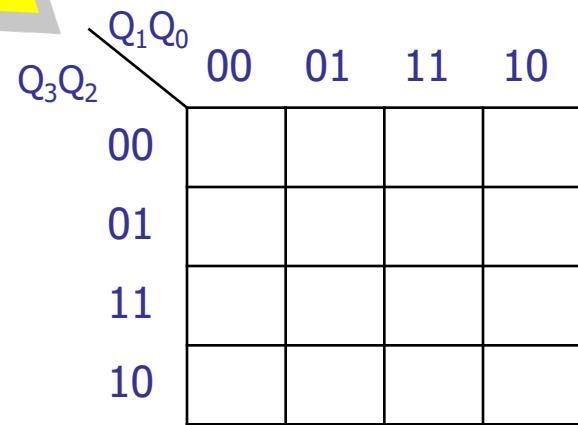

$$T_2 =$$

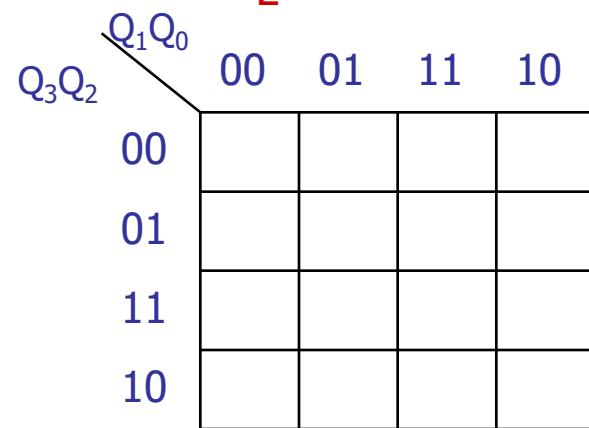

$$T_0 =$$



Home
work

Exercise 8b.18: Design a synchronous BCD decade counter using the D flip-flop.




Cascaded Counter

Cascaded Counter

- Counter can be connected to achieve higher modulus operation.
- Cascading means that the last-stage output of one counter drives the input of the next counter.

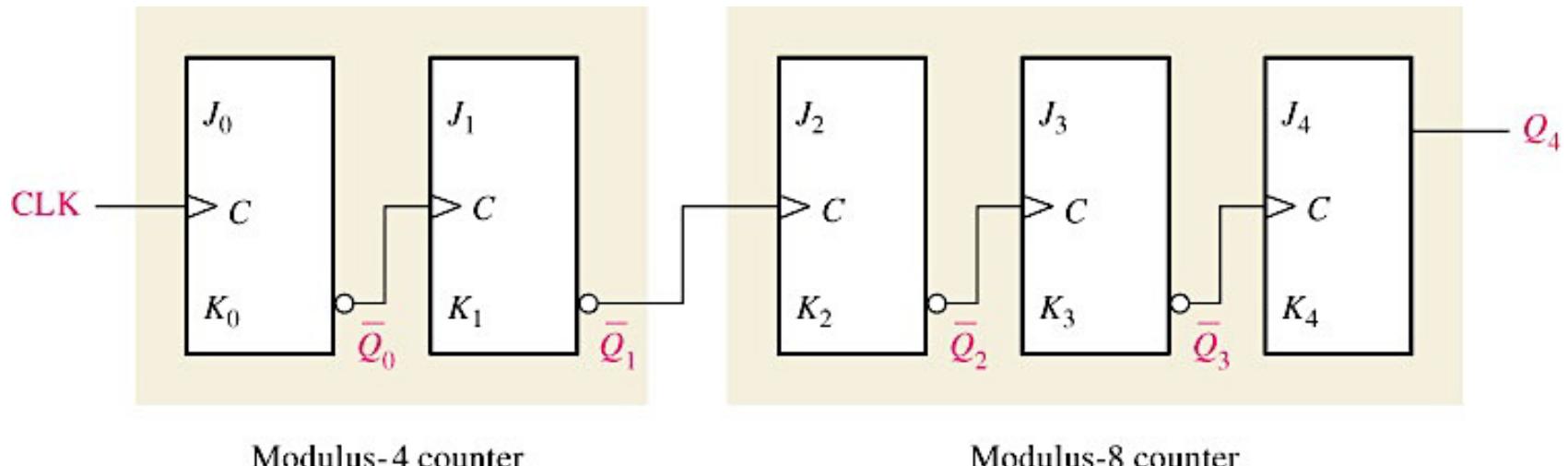Example:

- Two counters, modulus-4 and modulus-8 connected in cascade, can achieve count until 32 CLK (modulus-32). (i.e 4×8)




Recap: Modulus

- The modulus → number of unique states through which the counter will sequence.
- Maximum possible number of states = 2^N ,
 N is the number of flip-flops in the counter.
- Example : Modulus 8 = 2^3 (Need 3 flip flops)
- Counter can be designed to have less number of states in their sequence → Truncated sequence.
 - One common modulus for counters → ten (Modulus 10).
 - It called BCD decade counters (as explained in previous slides).

Cascaded Counter: Modulus-100 Counter

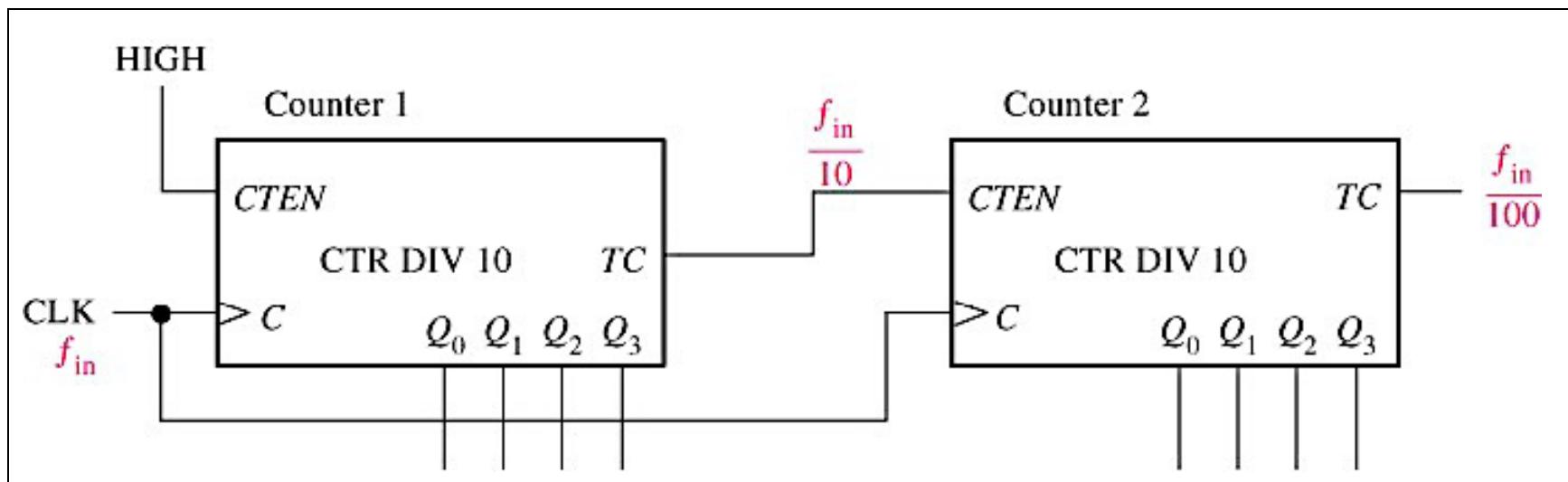- Modulus-100 counter using **2 cascaded decade counters**.
- This counter can be viewed as a **frequency divider**.
- It **divides the input clock frequency by 100**.




CTEN – Count Enable function
TC – Terminal Count function

(Total MOD = $10 \times 10 = 100$)

Cascaded Counter: Modulus-1000 Counter

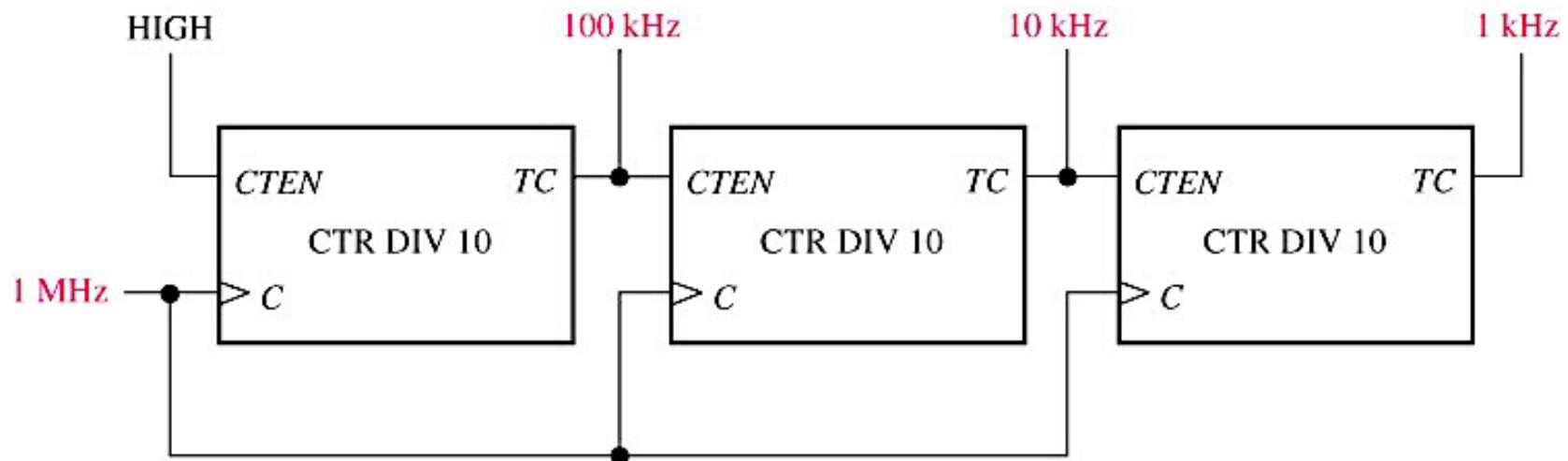- Three cascaded decade counters forming a divide-by-1000 frequency divider.



$$\begin{aligned}\text{Total MOD} &= 10 \times 10 \times 10 \\ &= 1000\end{aligned}$$

Basis clock frequency of 1 MHz and you wish to obtain 100kHz, 10Hz, and 1kHz, a series of cascaded decade counters can be used.

- If 1 MHz signal is divided by 10, the output is 100kHz.
- Then if the 100 kHz signal is divided by 10, the output is 10kHz.
- Further division by 10 gives the 1 kHz frequency.

Exercise 8b.19: Two type of counters, modulus-4 and modulus-8 need to be used to achieve count up to modulus- n (n CLK).

- a) How to cascade the counters to achieve count until 32 CLK (modulus-32)?
- b) What is the frequency produced by each counter given an initial frequency is 800MHz?

Solutions:


a) Modulus-4 x Modulus-8, or

Modulus-8 x Modulus-4.

b)

Modulus-4:
 $= 800\text{MHz} / 4$
 $= 200\text{MHz}$

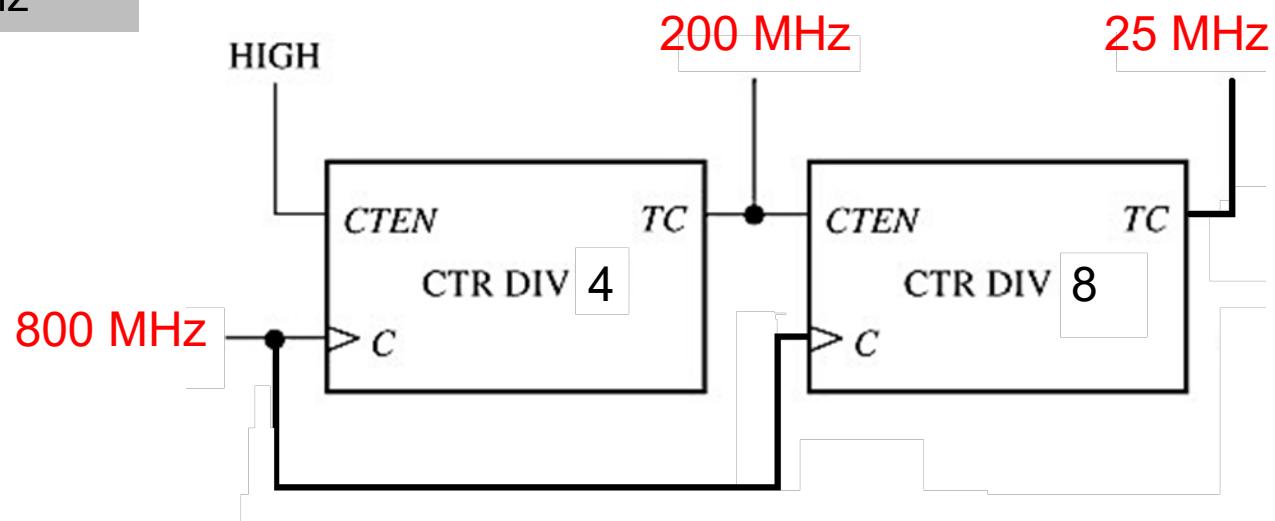
Modulus-8:
 $= 200\text{MHz} / 8$
 $= 25\text{MHz}$



b)

Modulus-8:
 $= 800\text{MHz} / 8$
 $= 100\text{MHz}$

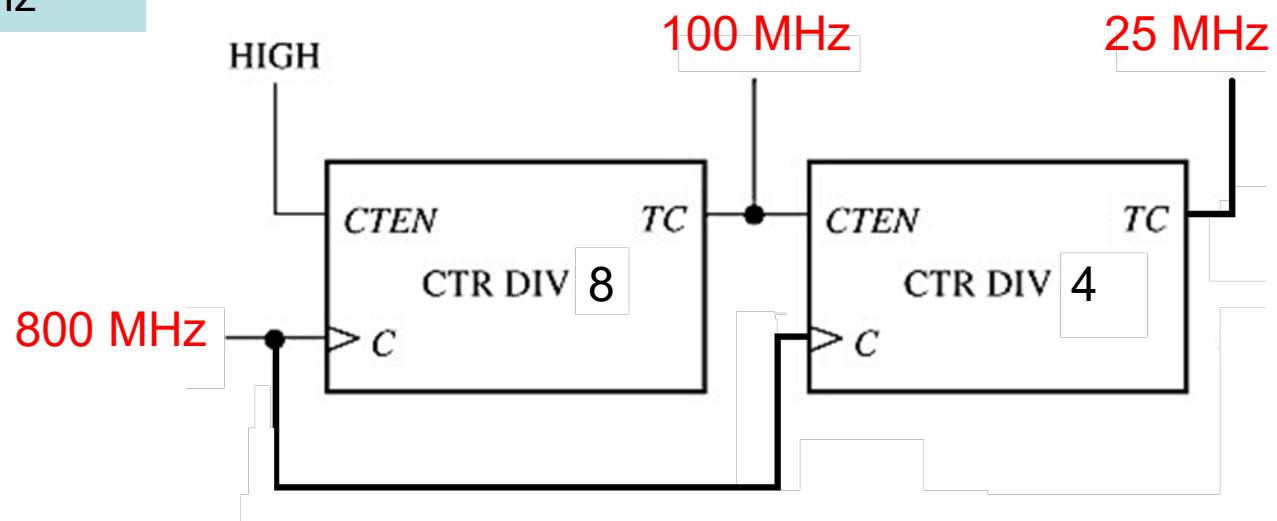Modulus-4:
 $= 100\text{MHz} / 4$
 $= 25\text{MHz}$






Analysis of Sequential Circuits

Analysis of Sequential Circuits

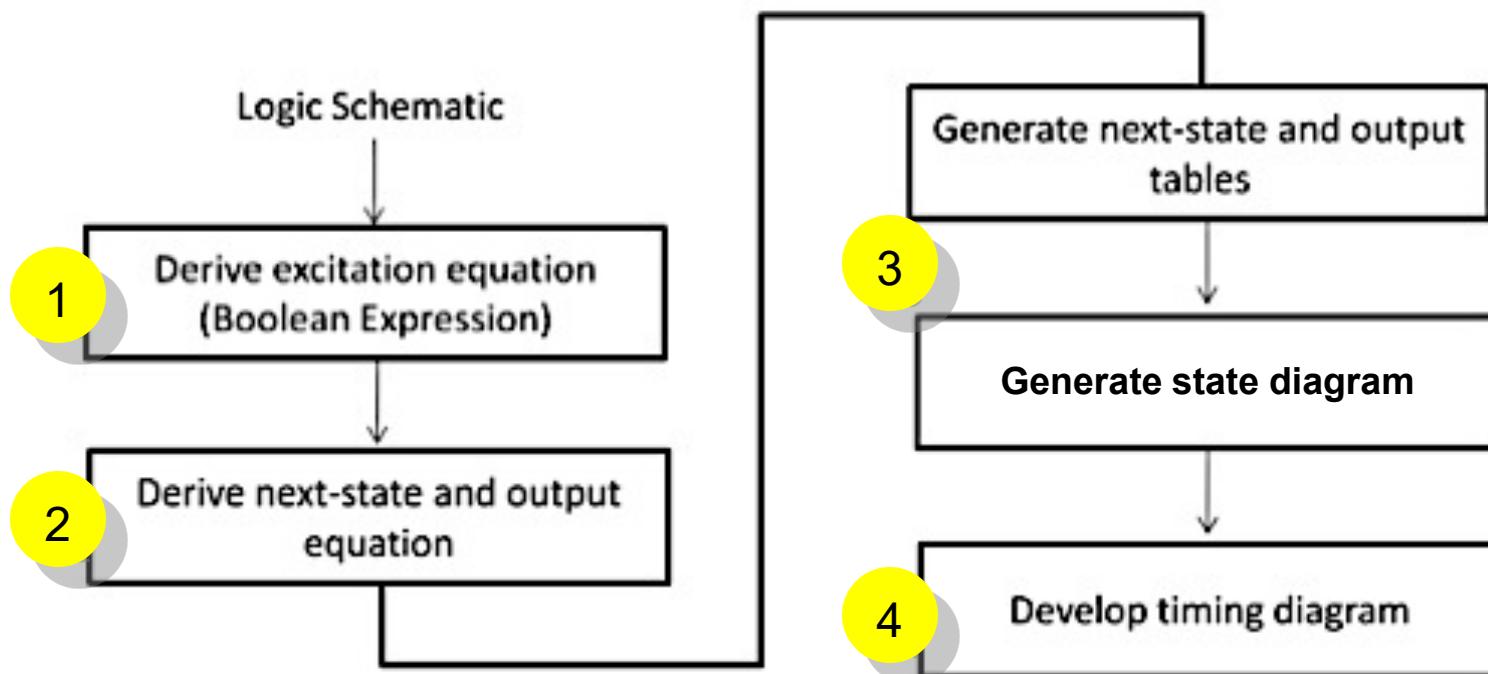- Behavior of a sequential circuit is determined from the **inputs**, the **outputs** and the **states** of its flip-flops.
- Both the **output and the next state** are a function of the **inputs** and the **present state**.



- **Step 1:**
Start with the logic schematic from which we can derive **excitation equations** for each flip-flop input.
- **Step 2:**
To obtain **next-state equations**, we insert the excitation equations into the characteristic equations. The **output equations** can be derived from the schematic:

Flip-flop characteristic equation:

active HIGH

$$JK : Q_{\text{next}} = J\bar{Q} + \bar{K}Q$$

$$D : Q_{\text{next}} = D$$

$$T : Q_{\text{next}} = T\bar{Q} + \bar{T}Q$$

- **Step 3:**

Once we have our output and next-state equations, we can generate the **next-state and output tables** as well as **state diagrams**.


- **Step 4:**

When we reach this stage, we use either the table or the state diagram to develop a **timing diagram** which can be verified through simulation.

Analysis of Sequential Circuits: Modulo-4 Counter

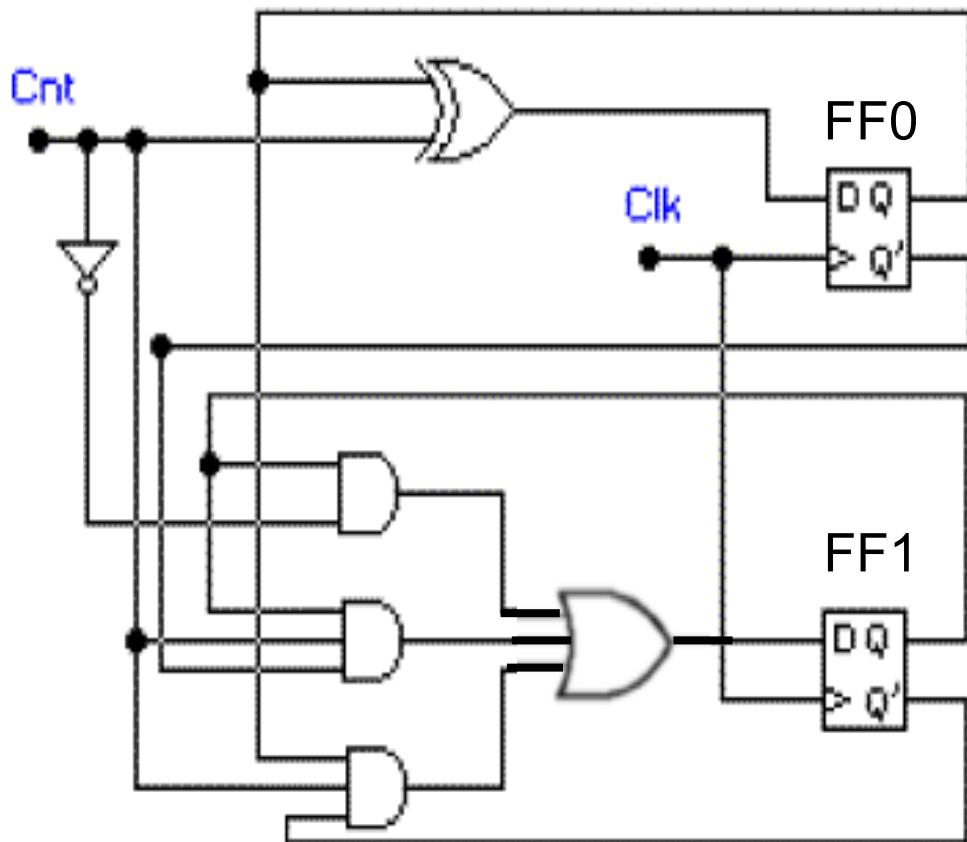Example:


Derive the state table and state diagram for the sequential circuit below.




- Step 1: Boolean expressions for the inputs of each flip-flops in the schematic.

$$D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q_0}$$
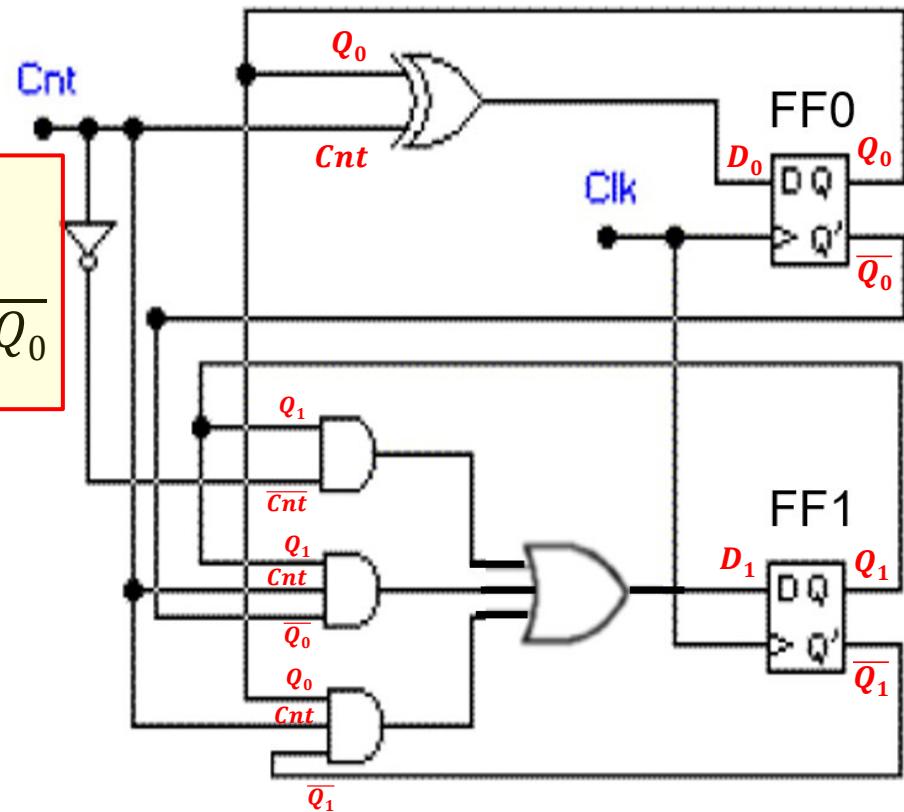
$$D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q_1} \cdot Q_0 + Cnt \cdot Q_1 \cdot \overline{Q_0}$$



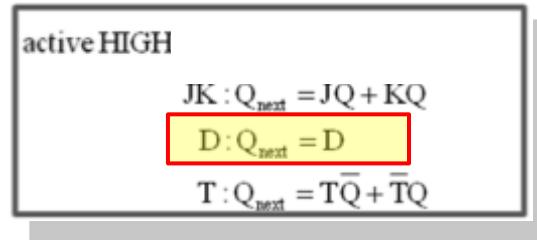

- Step 1: Boolean expressions for the inputs of each flip-flops in the schematic.


$$D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q}_0$$

$$D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q}_1 \cdot Q_0 + Cnt \cdot Q_1 \cdot \overline{Q}_0$$

- Step 2: Derive the next-state equations by converting these excitation equations into flip-flop characteristic equations. In the case of D flip-flops, $Q_+ =$

$$Q_{0+} = D_0$$

$$Q_{1+} = D_1$$

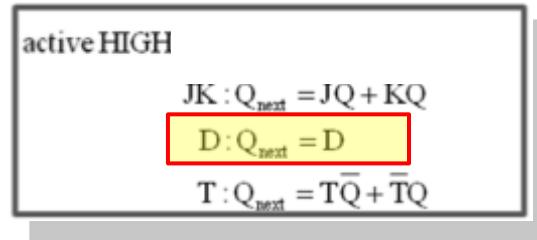

- Step 1: **Boolean expressions** for the inputs of each flip-flops in the schematic.

$$D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q}_0$$

$$D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q}_1 \cdot Q_0 + Cnt \cdot Q_1 \cdot \overline{Q}_0$$

- Step 2: Derive the **next-state equations** by converting these excitation equations into flip-flop characteristic equations. In the case of D flip-flops, $Q_+ =$

$$Q_{0+} = D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q}_0$$

$$Q_{1+} = D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q}_1 \cdot Q_0 + Cnt \cdot Q_1 \cdot \overline{Q}_0$$

$$D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q_0}$$

$$D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q_1} \cdot Q_0 + Cnt \cdot Q_1 \cdot \overline{Q_0}$$

- Step 3:
Construct the
next-state table.

Input, Cnt	Present State		Next State	
	Q ₁	Q ₀	Q ₁₊ = D ₁	Q ₀₊ = D ₀
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		


$$Q_{0+} = D_0 = Cnt \oplus Q_0 = \overline{Cnt} \cdot Q_0 + Cnt \cdot \overline{Q_0}$$

$$Q_{1+} = D_1 = \overline{Cnt} \cdot Q_1 + Cnt \cdot \overline{Q_1} \cdot Q_0 + Cnt \cdot Q_1 \cdot \overline{Q_0}$$

- Step 3:
Construct the
next-state table.



Input, Cnt	Present State		Next State	
	Q ₁	Q ₀	Q ₁₊ = D ₁	Q ₀₊ = D ₀
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

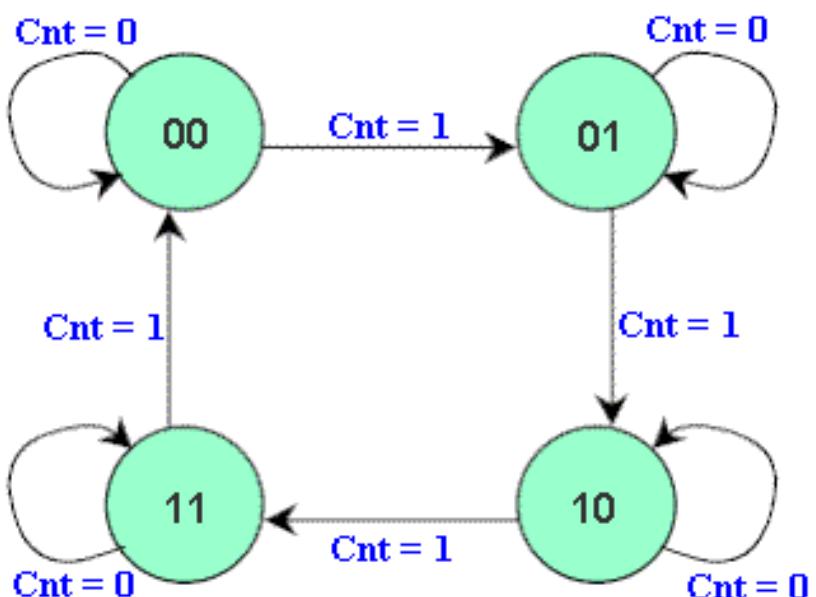- Step 4:
- The **state diagram** is generated directly from the next-state table.



Input, Cnt	Present State		Next State	
	Q_1	Q_0	$Q_{1+} = D_1$	$Q_{0+} = D_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

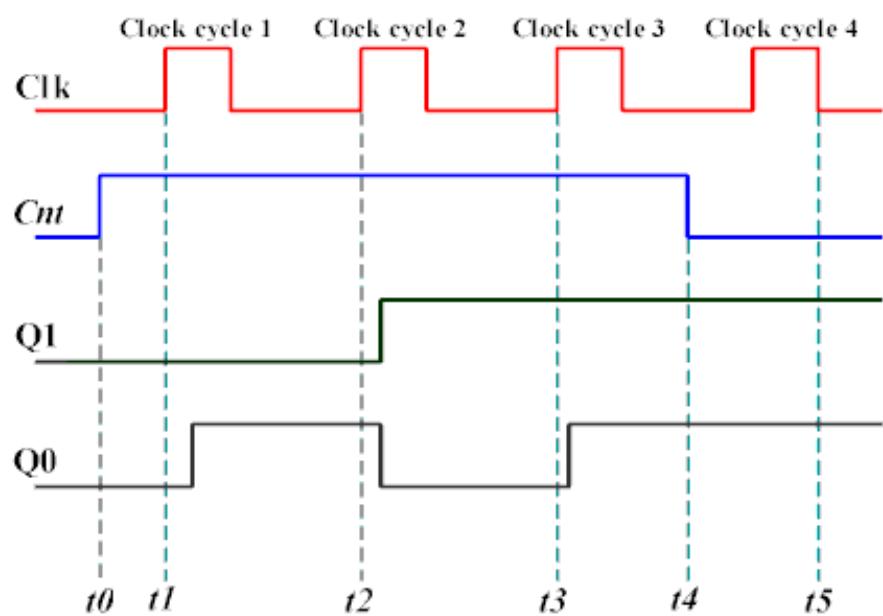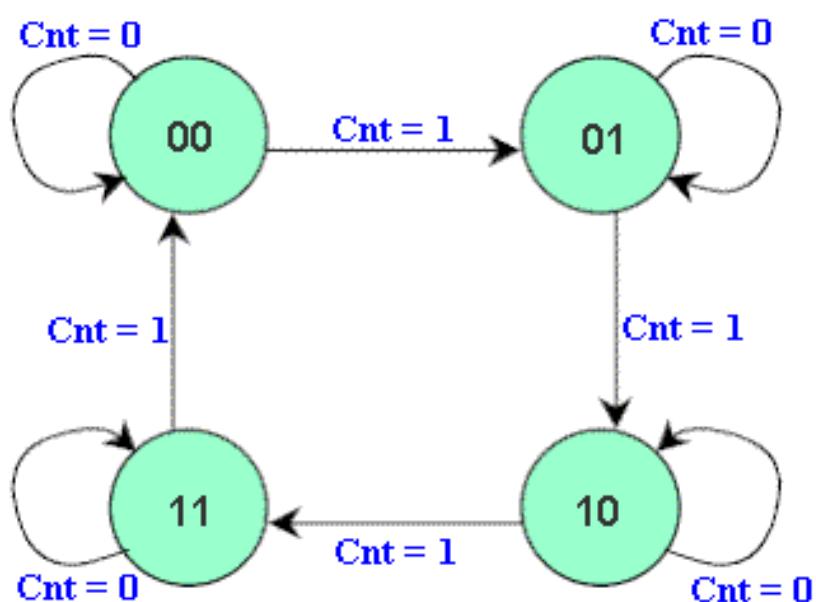- Step 4:
- The **state diagram** is generated directly from the next-state table.
- Next get the **timing diagram**





We can conclude:

a) From the counter circuit:

- 2-bit counter because there are 2 FFs in the design.
- Synchronous counter because the FFs have a common clock.

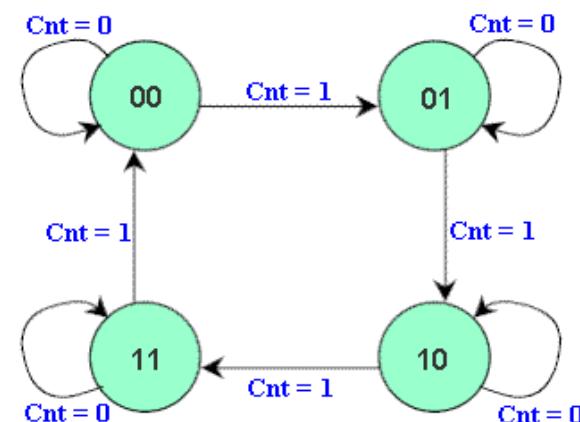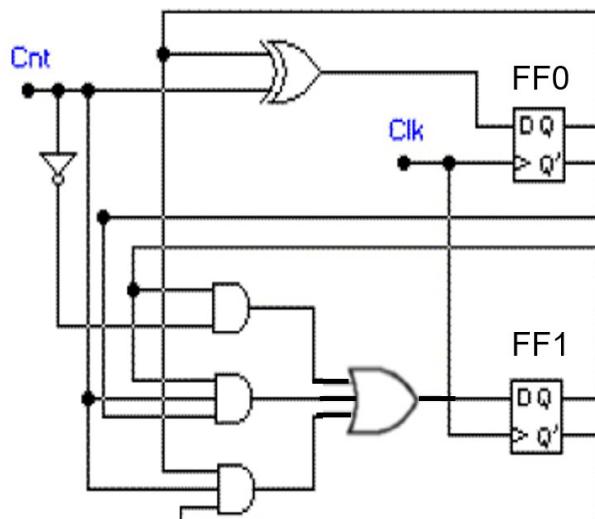b) From the counter state diagram:


- MOD 4 because has 4 state (i.e. $2^2=4$), not a truncated counter.
- Count Up counter when Cnt=1, and stay in the previous state when Cnt=0.



Analysis of Sequential Circuits: JK Circuit Analysis

Assume:

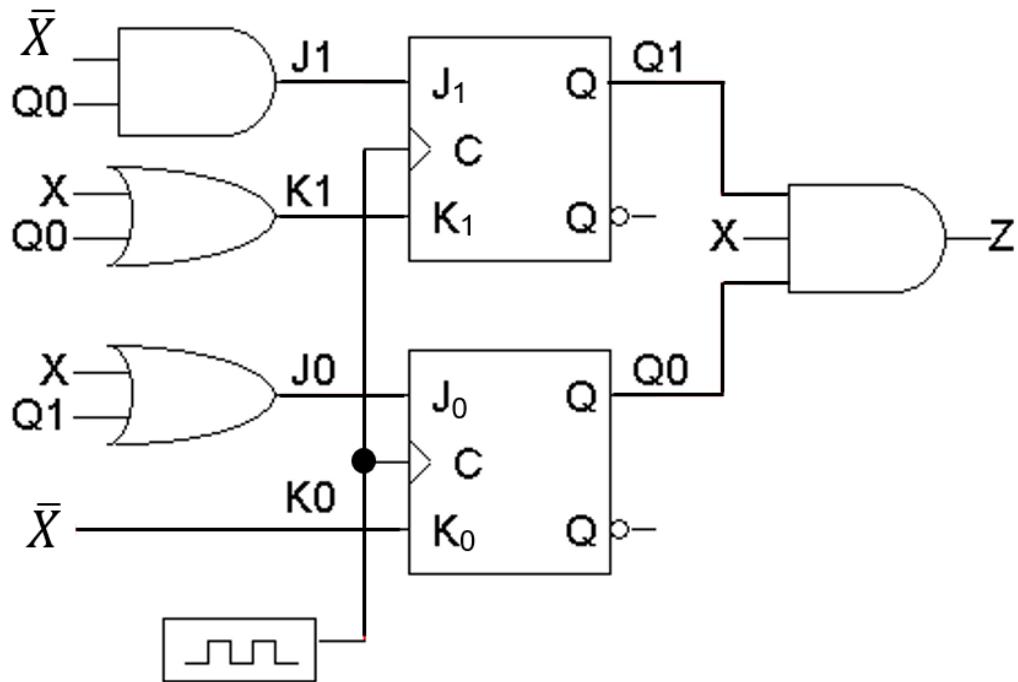- Sequential circuit with two JK flip-flops.
- There is one input, X, and one output, Z.



$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

- Remember that there is one input X, one output Z, and two flip-flops Q_1Q_0 .
- The present state Q_1Q_0 and the input will determine the next state and the output.
- From the diagram, $Z = Q_1Q_0X$

Input, X	Present State		Next State		Output, Z
	Q_1	Q_0	Q_{1+}	Q_{0+}	
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

**Fill in the Z

- Remember that there is one input X, one output Z, and two flip-flops Q_1Q_0 .
- The present state Q_1Q_0 and the input will determine the next state and the output.
- From the diagram, $Z = Q_1Q_0X$

Input, X	Present State		Next State		Output, Z
	Q_1	Q_0	Q_{1+}	Q_{0+}	
0	0	0			0
0	0	1			0
0	1	0			0
0	1	1			0
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

**Fill in the Z

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

active HIGH SR : $Q_{\text{next}} = S + \bar{R}Q, SR = 0$

$$JK : Q_{\text{next}} = J\bar{Q} + \bar{K}Q$$

$$D : Q_{\text{next}} = D$$

$$T : Q_{\text{next}} = T\bar{Q} + \bar{T}Q$$

$$Q_{0+} = J_0\bar{Q}_0 + \bar{K}_0Q_0 = (X + Q_1)\bar{Q}_0 + \bar{\bar{X}}Q_0 = X\bar{Q}_0 + Q_1\bar{Q}_0 + XQ_0$$

$$Q_{1+} = J_1\bar{Q}_1 + \bar{K}_1Q_1 = (\bar{X}Q_0)\bar{Q}_1 + (\bar{X} + \bar{Q}_0)Q_1 = \bar{X}Q_0\bar{Q}_1 + (\bar{X}\bar{Q}_0)Q_1 = \bar{X}Q_0\bar{Q}_1 + \bar{X}\bar{Q}_0Q_1$$

$$= \bar{X}(Q_0\bar{Q}_1 + \bar{Q}_0Q_1)$$

Input, X	Present State		Next State		Output, Z
	Q_1	Q_0	Q_{1+}	Q_{0+}	
0	0	0			0
0	0	1			0
0	1	0			0
0	1	1			0
1	0	0			0
1	0	1			0
1	1	0			0
1	1	1			1

**Fill in the next state column

active HIGH SR : $Q_{\text{next}} = S + \bar{R}Q$, SR = 0

$$JK : Q_{\text{next}} = J\bar{Q} + \bar{K}Q$$

$$D : Q_{\text{next}} = D$$

$$T : Q_{\text{next}} = T\bar{Q} + \bar{T}Q$$

$$Q_{0+} = X\bar{Q}_0 + Q_1\bar{Q}_0 + XQ_0$$

$$Q_{1+} = \bar{X}(Q_0\bar{Q}_1 + \bar{Q}_0 Q_1)$$

Input, X	Present State		Next State		Output, Z
	Q_1	Q_0	Q_{1+}	Q_{0+}	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	0	1	1

**Fill in the next state column

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q_1	Q_0	Q_{1+}	Q_{0+}					
0	0	0							0
0	0	1							0
0	1	0							0
0	1	1							0
1	0	0							0
1	0	1							0
1	1	0							0
1	1	1							1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0			0				0
0	0	1			1				0
0	1	0			0				0
0	1	1			1				0
1	0	0			0				0
1	0	1			0				0
1	1	0			0				0
1	1	1			0				1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0			0	0			0
0	0	1			1	1			0
0	1	0			0	0			0
0	1	1			1	1			0
1	0	0			0	1			0
1	0	1			0	1			0
1	1	0			0	1			0
1	1	1			0	1			1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0			0	0	0		0
0	0	1			1	1	0		0
0	1	0			0	0	1		0
0	1	1			1	1	1		0
1	0	0			0	1	1		0
1	0	1			0	1	1		0
1	1	0			0	1	1		0
1	1	1			0	1	1		1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0			0	0	0	1	0
0	0	1			1	1	0	1	0
0	1	0			0	0	1	1	0
0	1	1			1	1	1	1	0
1	0	0			0	1	1	0	0
1	0	1			0	1	1	0	0
1	1	0			0	1	1	0	0
1	1	1			0	1	1	0	1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0			0	0	0	1	0
0	0	1			1	1	0	1	0
0	1	0			0	0	1	1	0
0	1	1			1	1	1	1	0
1	0	0			0	1	1	0	0
1	0	1			0	1	1	0	0
1	1	0			0	1	1	0	0
1	1	1			0	1	1	0	1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	0	1	0
0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0
1	0	1	0	1	0	1	1	0	0
1	1	0	0	1	0	1	1	0	0
1	1	1	0	1	0	1	1	0	1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	0	1	0
0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0
1	0	1	0	1	0	1	1	0	0
1	1	0	0	1	0	1	1	0	0
1	1	1	0	1	0	1	1	0	1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values

$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	0	1	0
0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0
1	0	1	0	1	0	1	1	0	0
1	1	0	0	1	0	1	1	0	0
1	1	1	0	1	0	1	1	0	1

Method 2 –

- Fill up JK input values based on input equations
- Fill up Next State columns by observing JK input values


$$J_1 = \bar{X}Q_0 \quad J_0 = X + Q_1 \quad Z = Q_1Q_0X$$

$$K_1 = X + Q_0 \quad K_0 = \bar{X}$$

Input, X	Present State		Next State		J1	K1	J0	K0	Output, Z
	Q ₁	Q ₀	Q ₁₊	Q ₀₊					
0	0	0	0	0	0	0	0	1	0
0	0	1	1	0	1	1	0	1	0
0	1	0	1	1	0	0	1	1	0
0	1	1	0	0	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0
1	0	1	0	1	0	1	1	0	0
1	1	0	0	1	0	1	1	0	0
1	1	1	0	1	0	1	1	0	1

Exercise 8b.20: Draw the state diagram for the example in previous slide.

Present state

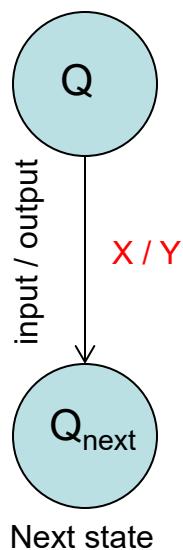


Next state

Input, X	Present State		Next State		Output, Z
	Q_1	Q_0	Q_{1+}	Q_{0+}	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	0	1	1


Solution :

Draw the state diagram for the example in previous slide.


Present state

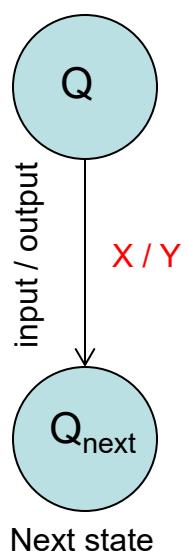

Next state

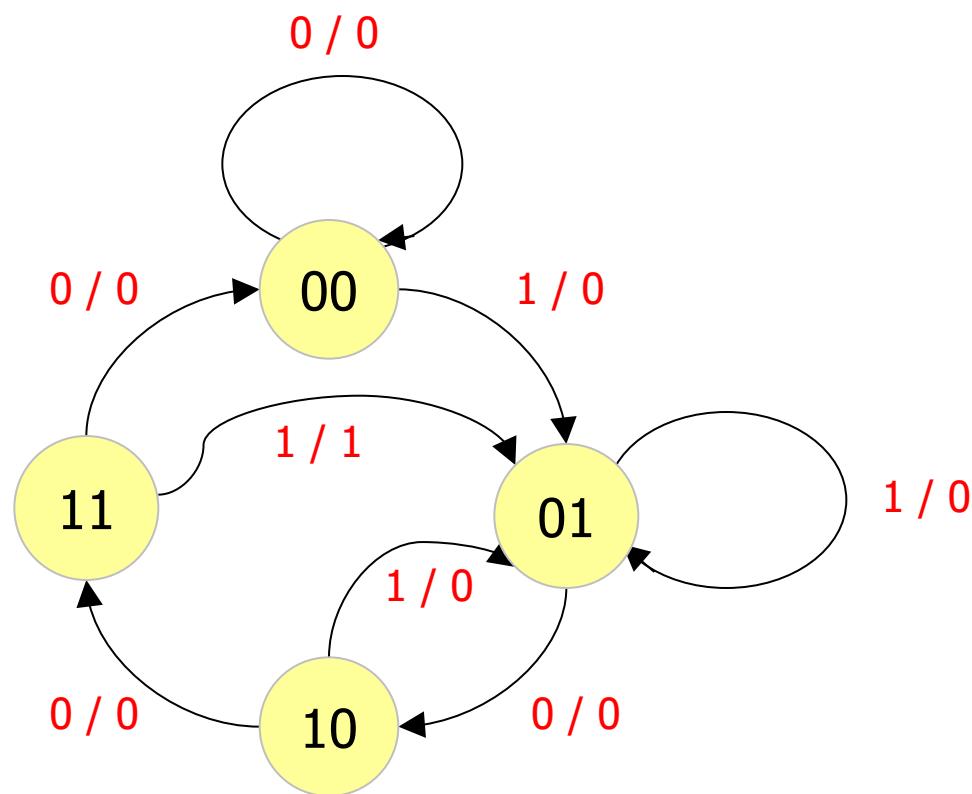

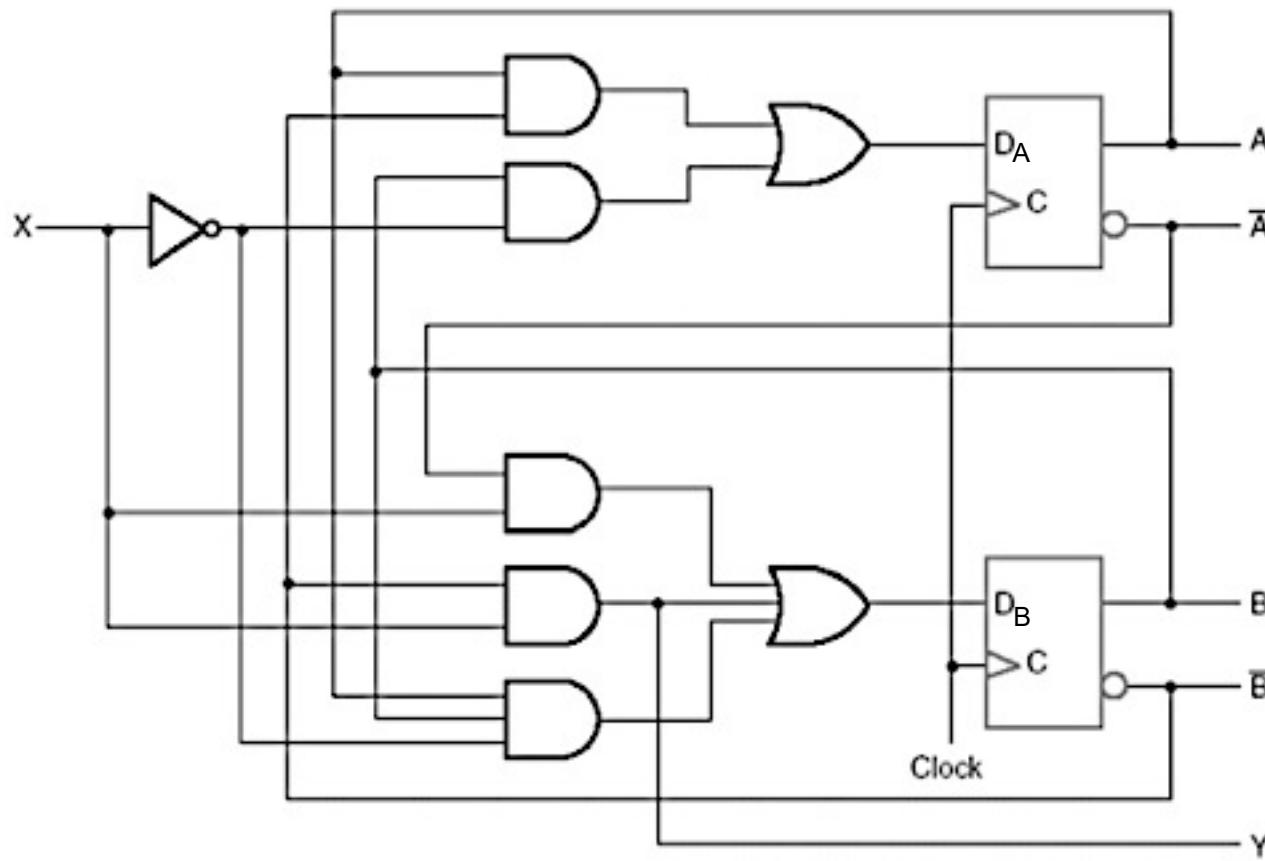Exercise 8b.21: Analysis for the following sequential circuit.



Solution:

Step 1: The equation of each FF and output, Y

$$D_A = \overline{X}B + A\overline{B}$$


$$D_B = \overline{A}X + \overline{B}X + AB\overline{X}$$

$$Y = \overline{B}X$$

Step 2: Derive the next state equations by converting these excitation equation into FF characteristic equations.

$$D_{A+} = D_A$$

$$D_{B+} = D_B$$

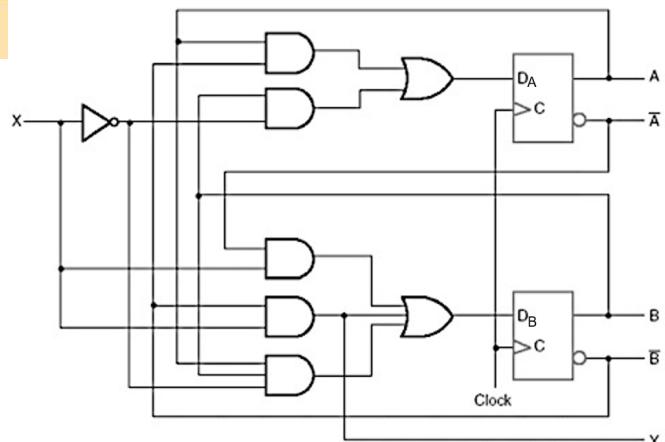

$$\text{active HIGH SR : } Q_{\text{next}} = S + \overline{R}Q, SR = 0$$

$$\text{JK : } Q_{\text{next}} = J\overline{Q} + \overline{K}Q$$

$$\boxed{\text{D : } Q_{\text{next}} = D}$$

$$\text{T : } Q_{\text{next}} = T\overline{Q} + \overline{T}Q$$

Solution:

Step 1: The equation of each FF and output, Y

$$D_A = \overline{X}B + A\overline{B}$$


$$D_B = \overline{A}X + \overline{B}X + AB\overline{X}$$

$$Y = \overline{B}X$$

Step 2: Derive the next state equations by converting these excitation equation into FF characteristic equations.

$$D_{A+} = D_A = \overline{X}B + A\overline{B}$$
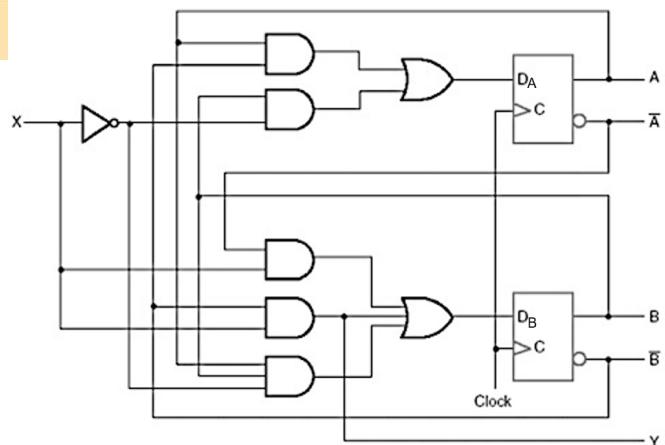
$$D_{B+} = D_B = \overline{A}X + \overline{B}X + AB\overline{X}$$



$$\text{active HIGH SR : } Q_{\text{next}} = S + \overline{R}Q, SR = 0$$

$$\text{JK : } Q_{\text{next}} = J\overline{Q} + \overline{K}Q$$

$$\boxed{\text{D : } Q_{\text{next}} = D}$$

$$\text{T : } Q_{\text{next}} = T\overline{Q} + \overline{T}Q$$

$$D_{A+} = D_A = \overline{X}B + A\overline{B}$$


$$\begin{aligned} D_{B+} &= D_B = \overline{A}X + \overline{B}X + AB\overline{X} \\ Y &= \overline{B}X \end{aligned}$$

Step 3: Produce a Next State Table.

Input, X	Present State		Next State		Output, Y
	A	B	A ₊	B ₊	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Exercise 8b.22: Draw the state diagram for the example in previous slide.

Present state

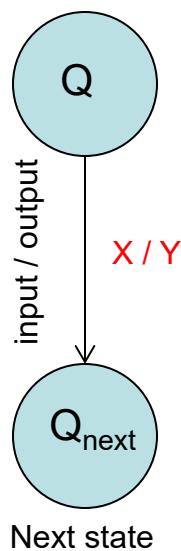



Next state

Input, X	Present State		Next State		Output, Y
	A	B	A ₊	B ₊	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Solution :

Draw the state diagram for the example in previous slide.

Present state

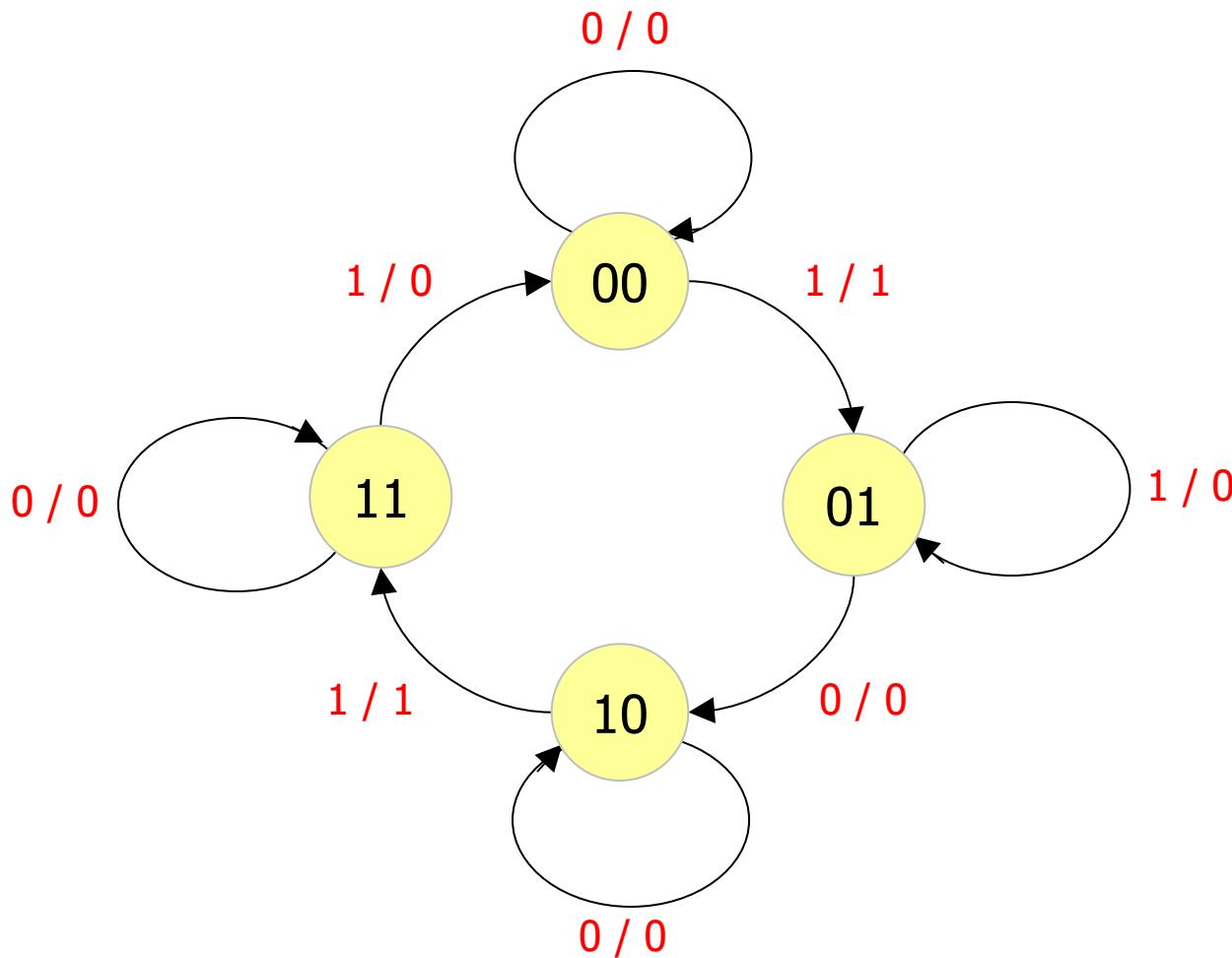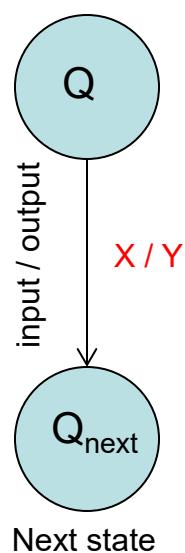


Next state

End of Module 8

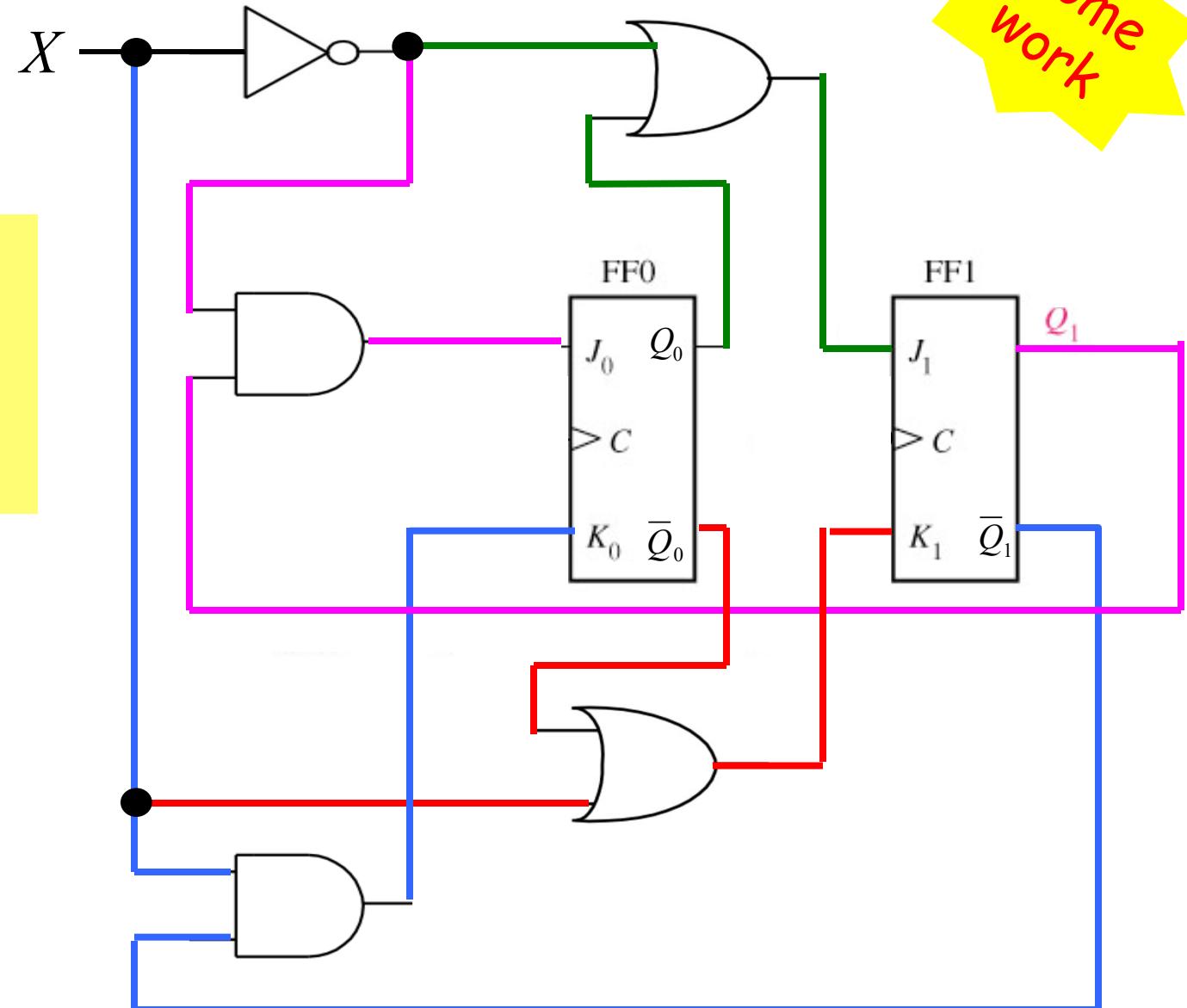Exercise 8b.23:


Derive the state table and state diagram for the sequential circuit below.



Home
work

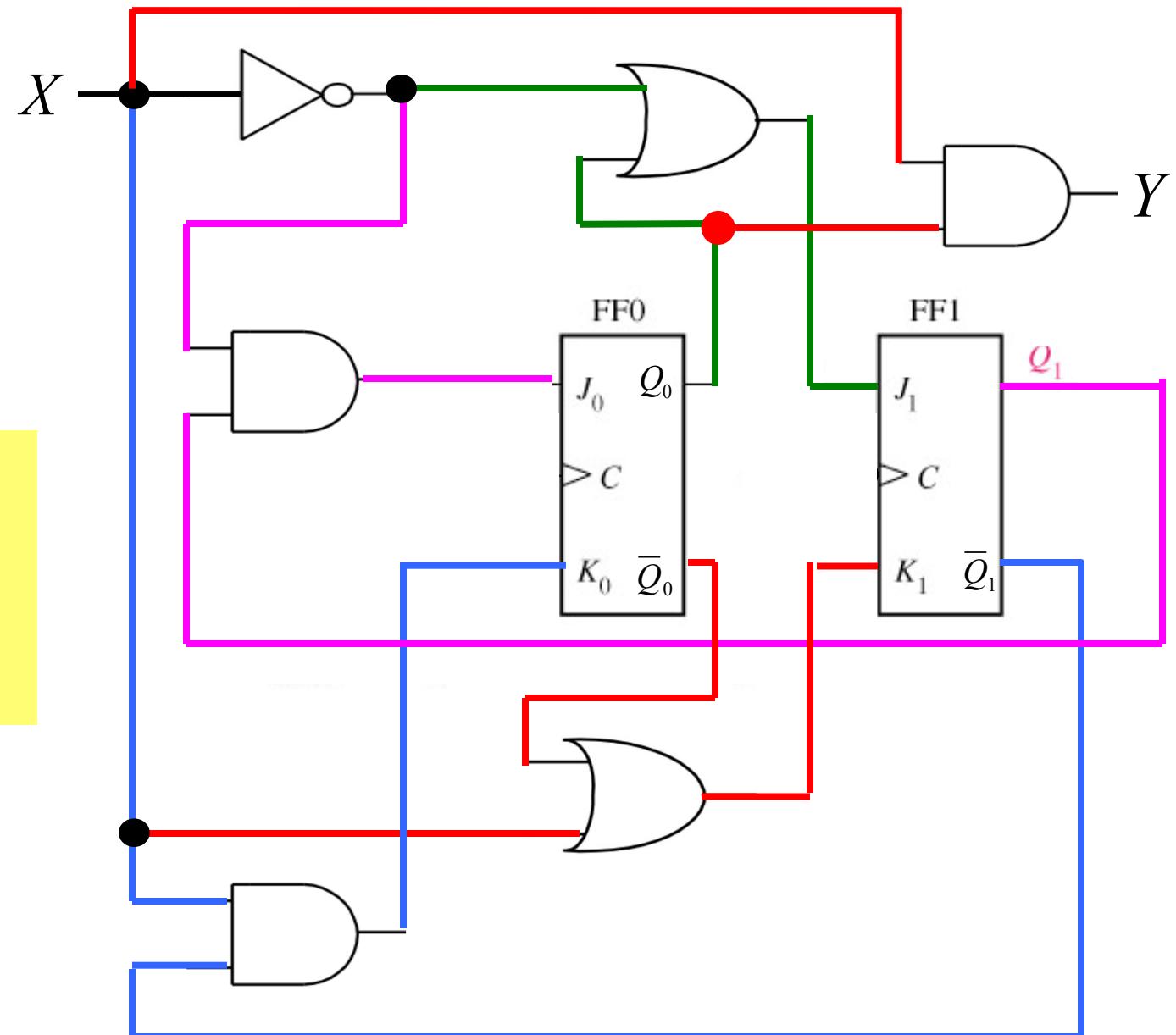Exercise 8b.24:


Derive the state table and state diagram for the sequential circuit below.



Home
work

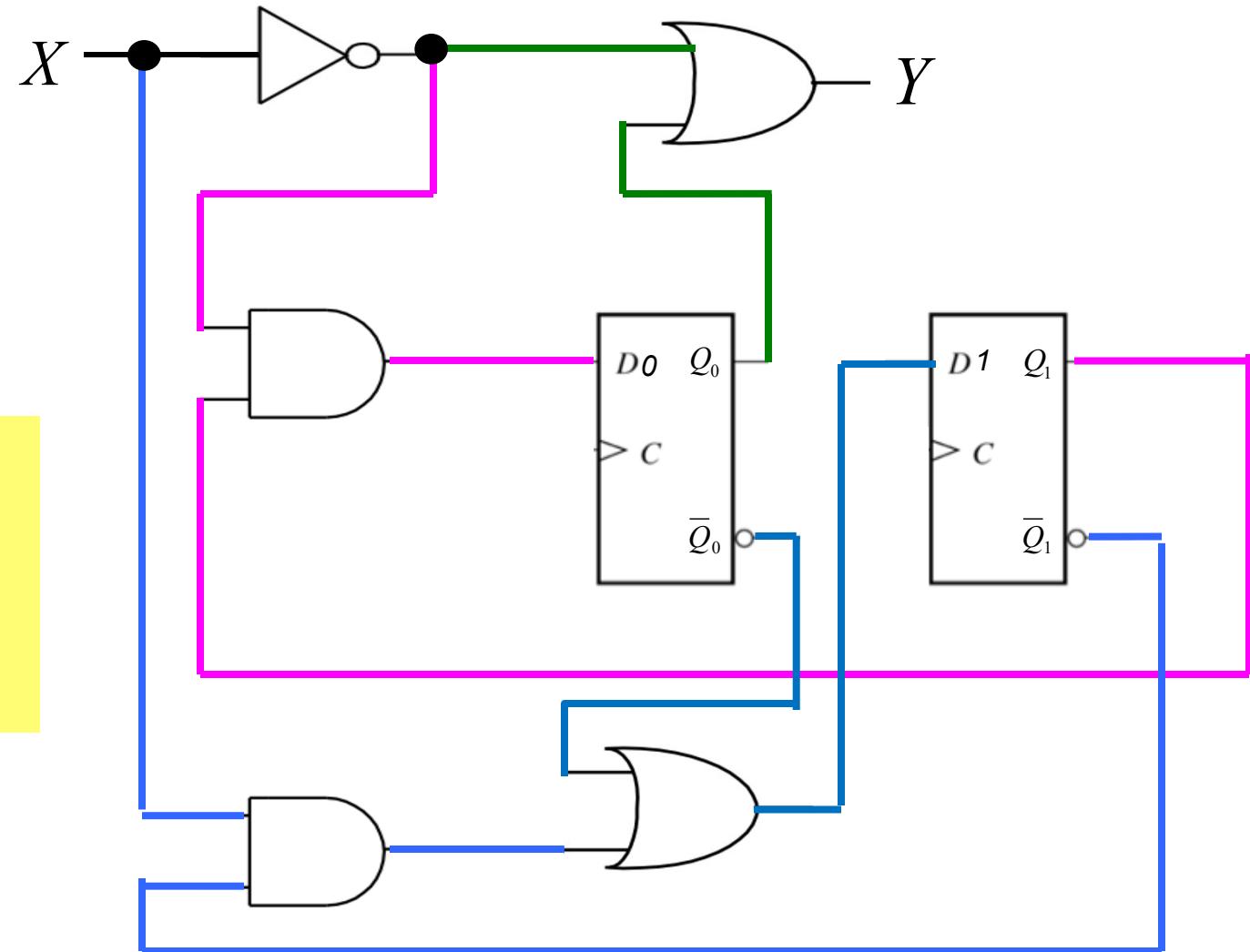Exercise 8b.25:

Derive the state table and state diagram for the sequential circuit below.



Home
work

Exercise 8b.27:

Derive the state table and state diagram for the sequential circuit below.

